
UNIVERSITI SAINS MALAYSIA

Semester I Examination
Academic Session 2008/2009

November 2008

EEE 510 – ANALOG CIRCUIT DESIGN

Time : 3 hours

INSTRUCTION TO CANDIDATE:

Please ensure that this examination paper contains **NINE (9)** printed pages and **SIX (6)** questions before answering.

Answer **FIVE (5)** questions.

Distribution of marks for each question is given accordingly.

All questions must be answered in English.

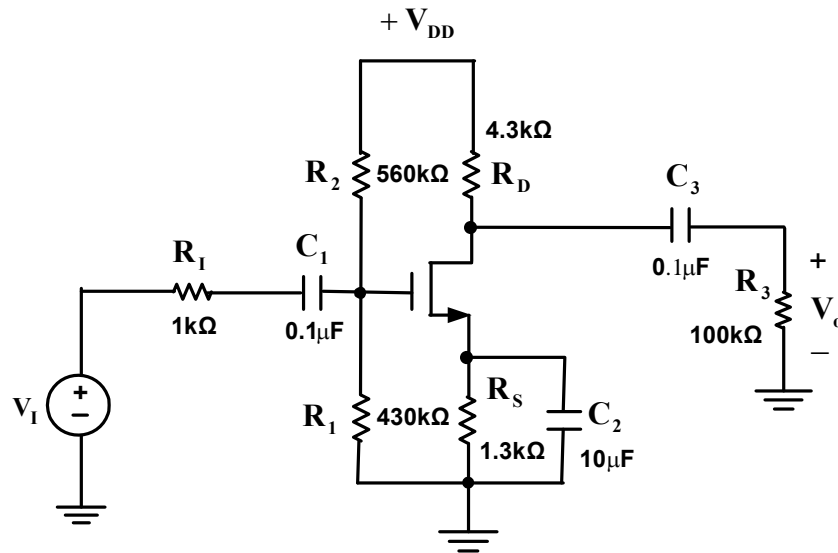


Figure 1

1. Given in Figure 1 a common source amplifier with source degeneration. Assuming negligible output impedance, r_o , ignoring the gate-to-drain capacitance, and occurring at low enough frequency that you can ignore gate-to-source capacitance C_{gs} ,
 - (a) draw the equivalent small signal model (5 marks)
 - (b) derive the gain to yield the following expression.

$$A_v(s) = \frac{V_o(s)}{V_I(s)} = A_{mid} F_L(s)$$

$$= \left[-g_m (R_3 \parallel R_D) \frac{R_G}{R_I + R_G} \right] \frac{s^2 \left[s + \frac{1}{C_2 R_S} \right]}{\left[s + \frac{1}{C_1 (R_1 + R_G)} \right] \left[s + \frac{1}{C_2 \left(\frac{1}{g_m} \parallel R_S \right)} \right] \left[s + \frac{1}{C_3 (R_D + R_3)} \right]}$$

(15 marks)

2. Given a BJT circuit as shown in Figure 2 and it has the following I-V characteristic:

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left(1 + \frac{V_{CE}}{V_A}\right)$$

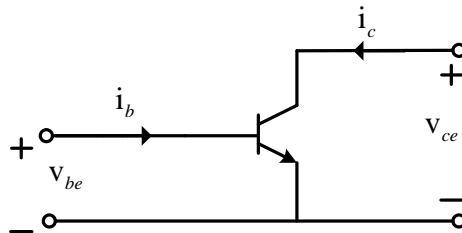


Figure 2 : BJT Circuit

Using a 2-port y-network, we also have the following relation:

$$i_b = y_{11} V_{be} + y_{12} V_{ce} \quad (1)$$

$$i_c = y_{21} V_{be} + y_{22} V_{ce} \quad (2)$$

The hybrid-pi model is as shown in Figure 3 below:

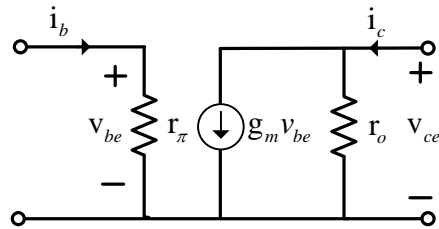


Figure 3 : Hybrid-pi model for BJT circuit

- (a) Convert equations (1) and (2) to the h-parameter network. Draw the corresponding h-parameter hybrid-pi model. (5 marks)
 - (b) Find the input resistance using h-parameter that we have defined in part (a). (5 marks)
 - (c) Find the output resistance using h-parameter that we have defined in part (a). (5 marks)
 - (d) Find the forward current gain using h-parameter that we have defined in part (a). (5 marks)
3. Given a common-source circuit as shown in Figure 4 and it has the following I-V characteristic:

$$I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

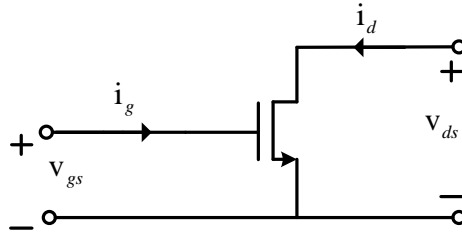


Figure 4 : MOSFET Circuit

Using a 2-port y-network, we also have the following relation:

$$i_g = y_{11}v_{gs} + y_{12}v_{ds}$$

$$i_d = y_{21}v_{gs} + y_{22}v_{ds}$$

The solutions for the above equalities are as follows:

$$y_{11} = \left. \frac{i_g}{v_{gs}} \right|_{v_{ds}=0} = 0$$

$$y_{12} = \left. \frac{i_g}{v_{ds}} \right|_{v_{gs}=0} = 0$$

$$y_{21} = \left. \frac{i_d}{v_{gs}} \right|_{v_{ds}=0} = \frac{2I_D}{V_{GS} - V_{TN}}$$

$$y_{22} = \left. \frac{i_d}{v_{ds}} \right|_{v_{gs}=0} = \frac{I_D}{\frac{1}{\lambda} + V_{DS}}$$

- (a) From the above expression, convert the small signal hybrid-pi model showing g-parameter.

(5 marks)

- (b) Derive the forward current gain from the g-parameter as in part (a).

(5 marks)

- (c) Derive the forward voltage gain from the g-parameter as in part (a).
(5 marks)
- (d) Derive the output resistance from the g-parameter as in part (a).
(5 marks)
4. Given a class A emitter-follower as shown in Figure 5. Transistor Q_1 is the emitter follower with Q_2, R_1, R_2 , and R_3 set up the biasing. Find the efficiency of the class A circuit using the following methodologies:

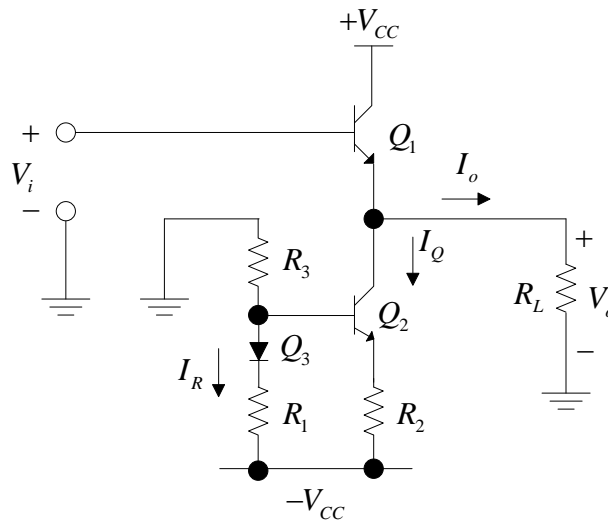


Figure 5 : Emitter-Follower Class A Output Stage

- (a) Using the Kirchoff's voltage law (KVL), find the voltage transfer characteristic (VTC) relating between the output voltage, V_o to the input voltage, V_i .

(5 marks)

...7/-

- (b) Draw the voltage transfer characteristics (VTC) with proper labelling. (5 marks)
- (c) Express the load power, P_L and the power due to DC power supply, P_{DC} . (5 marks)
- (d) Find the efficiency, η which is the ratio between the load power to the power due to DC supply. Show that the maximum efficiency is approximately 25%. (5 marks)

5.

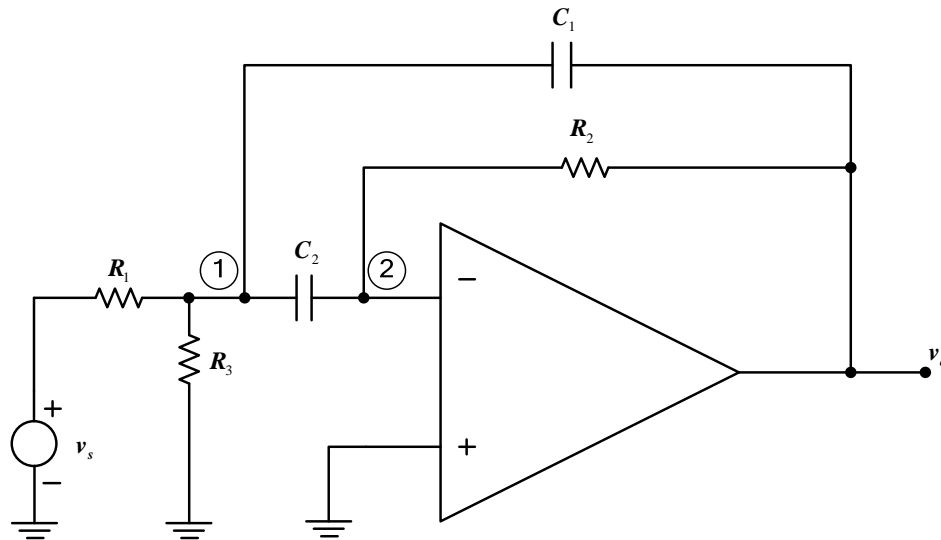


Figure 6 : Inverting Amplifier as a Bandpass Filter

Figure 6 shows the diagram of a bandpass filter built from an inverting op-amp. Prove that the following expression holds true:

$$A_{BP}(s) = - \left(\frac{2Q}{1 + \frac{R_1}{R_3}} \right) \left(\frac{s\omega_0}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2} \right)$$

Prove the above expression by the following methodology:

- (a) Express V_Q , R_1 , and R_3 as a function of Thevenin's voltage, V_{TH} and Thevenin's resistor, R_{TH} . Then, write Kirchoff's current law (KCL) at both nodes 1 and 2. Prove that the ratio of V_Q to V_{TH} is

$$\frac{V_Q}{V_{TH}} = \frac{\frac{-s}{R_{TH}C_1}}{s^2 + \frac{s}{R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + \frac{1}{R_2R_{TH}C_1C_2}}$$

(10 marks)

- (b) Using $R_{TH} = R_1 || R_2$, and $V_{TH} = \frac{R_2}{R_1 + R_2} V_S$, prove that $\frac{V_Q}{V_S}$ is given by

$$\frac{V_Q}{V_S} = \frac{\frac{-s}{R_1C_1}}{s^2 + \frac{s}{R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + \frac{R_1 + R_2}{R_2C_1C_2R_1R_3}}$$

(5 marks)

- (c) From the following relation

$$\frac{V_Q}{V_S} = K \frac{s\omega_0}{s^2 + s\frac{\omega_0}{Q} + \omega_0^2}$$

Find K, ω_0 and Q.

(5 marks)

...9/-

6. Estimate ω_L for the common-collector (CC) and the common-drain amplifier as shown in Figure 7 and 8.

(20 marks)

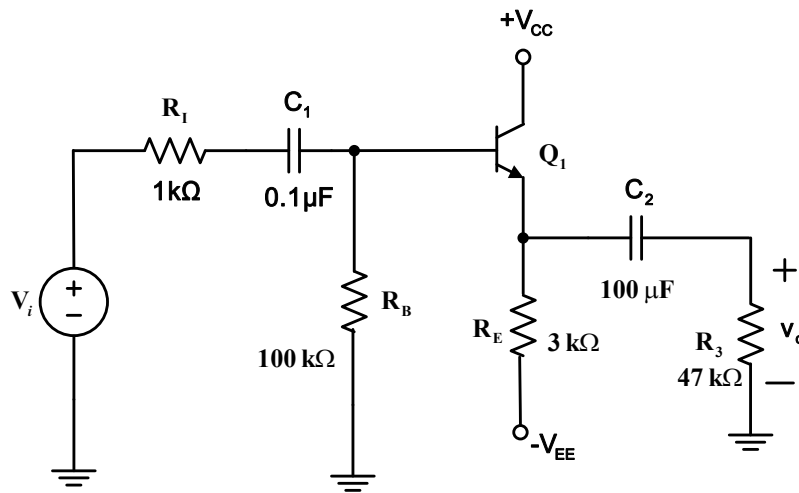


Figure 7 : Common-collector (CC) amplifier

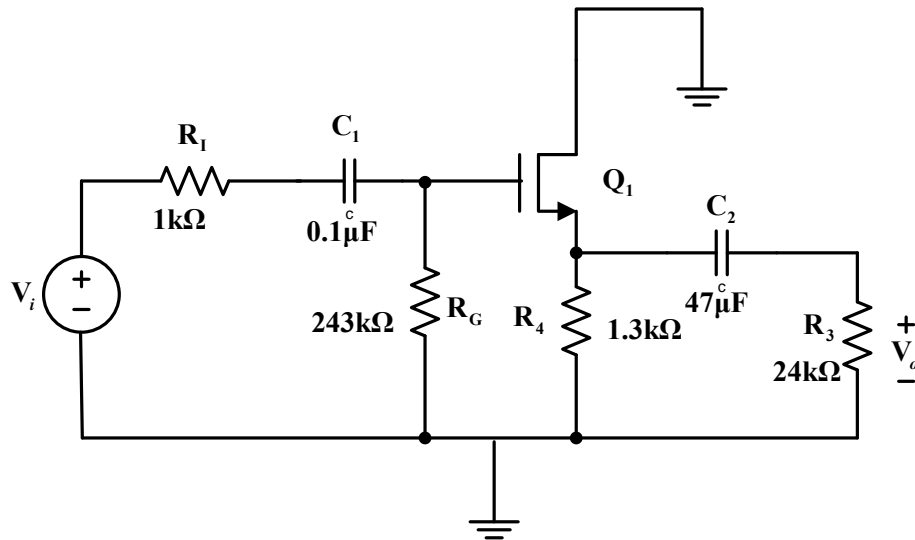


Figure 8 : Common-drain (CD) amplifier

ooo0ooo