

$$t_f = \frac{2 C_L}{\beta_m} F_m$$


com

$$F_m = \frac{V_{Tm}}{(V_{DD} - V_{Tm})^2} + \frac{1}{2(V_{DD} - V_{Tm})} \quad \text{lm} \quad \frac{2(V_{DD} - V_{Tm}) < V_{OL}}{V_{OL}}$$

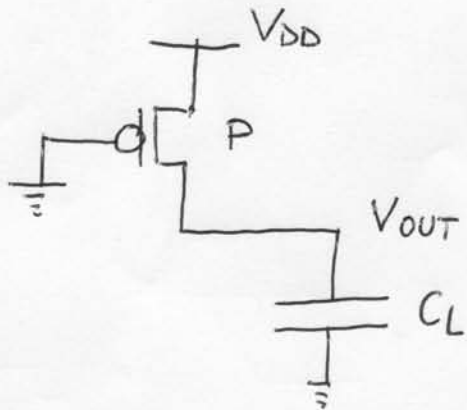
B) TRANSITORIO DI ~~INVERSIONE~~ SALITA t_r

Per $t < 0$ $V_{IN} = V_{DD} \longrightarrow V_{OUT} = 0$

Per $t = 0$ $V_{IN}: V_{DD} \longrightarrow 0$ quindi: N_{OFF} C_L si carica
 P_{ON}



$$V_{OUT}(0) = 0$$

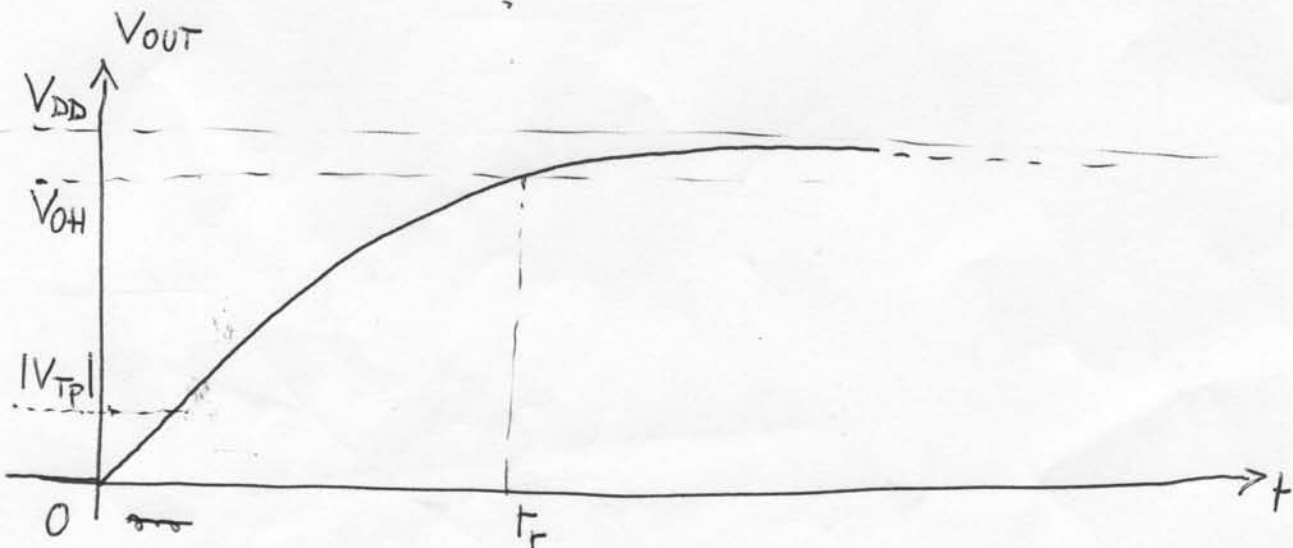

$$t_r = \frac{2 C_L}{\beta_P} F_P$$

com

$$F_P = \frac{|V_{TP}|}{(V_{DD} - |V_{TP}|)^2} + \frac{1}{2(V_{DD} - |V_{TP}|)} \ell_m \frac{2(V_{DD} - |V_{TP}|) - (V_{DD} - V_{OH})}{V_{DD} - V_{OH}}$$

● TECNOLOGIA A

$$V_{DD} = 3,3V \quad V_{Tm} = |V_{TP}| = 0,7V \quad \beta'_m = 100 \mu A/V^2 \quad \beta'_p = 50 \mu A/V^2$$

$$L_{min} = 0,35 \mu m \quad C_{ox} = 3,45 fF/\mu m^2$$

- TEMPI DI TRANSITO AL 90%

$$V_{OL} = \frac{V_{DD}}{10} = 0,33V$$

$$V_{OH} = \frac{9}{10} V_{DD} = 2,97V$$

$$V_{DD} - V_{OH} = 0,33V$$

$$F_{m_{90\%}} = F_{P_{90\%}} = \frac{0,7}{6,76} + \frac{1}{5,2} \ell_m \frac{5,2 - 0,33}{0,33} =$$

$$= 0,10355 + 0,51764 = 0,6212 \quad V^{-1}$$

- TEMPI DI TRANSITO AL 50% $V_{OL} = \frac{V_{DD}}{2} = 1,65V = V_{OH}$

$$F_{m_{50\%}} = F_{P_{50\%}} = \frac{0,7}{6,76} + \frac{1}{5,2} \ell_m \frac{5,2 - 1,65}{1,65} =$$

$$= 0,10355 + 0,14734 = 0,2509 \quad V^{-1}$$

$$C_L = m C_{im_gate} = m (W_P L_P + C_{ox}) = m L_{min}^2 (S_m + S_p) C_{ox}$$

Sia $C_L = 120 \text{ fF}$

$$m (S_m + S_p) = \frac{C_L}{L_{min}^2 C_{ox}} = \frac{120 \cdot 10^{-15}}{0,1225 \cdot 10^{-12} \cdot 3,45 \cdot 10^{-15}} = \frac{120}{0,4226} \approx 284$$

- $S_m = 2 \quad S_p = 2 S_m = 4$

$$\beta_m = \beta'_m \cdot S_m = 200 \frac{\mu A}{V^2}$$

$$\beta_p = \beta'_p S_p = 200 \frac{\mu A}{V^2}$$

$$t_{f90\%} = t_{r90\%} = \frac{2 \cdot 120 \cdot 10^{-15}}{200 \cdot 10^{-6}} \cdot 0,6212 = 0,7454 \cdot 10^{-9} = 745,4 \text{ ps}$$

$$t_{f50\%} = t_{r50\%} = \frac{2 \cdot 120 \cdot 10^{-15}}{200 \cdot 10^{-6}} \cdot 0,2509 = 0,301 \cdot 10^{-9} = 301 \text{ ps}$$

- $S_m = 1 \quad S_p = 4$

$$\beta'_m = \beta'_m S_m = 100 \mu A/V^2$$

$$\beta_p = \beta'_p S_p = 200 \frac{\mu A}{V^2}$$

$$t_{r90\%} = 745,4 \text{ ps}$$

$$t_{f90\%} = 2 t_{r90\%} = 1490,8 \text{ ps} \approx 1,49 \text{ ns}$$

$$t_{r50\%} = 301 \text{ ps}$$

$$t_{f50\%} = 2 t_{r50\%} = 602 \text{ ps}$$

- $S_m = 2 \quad S_p = 2$

$$\beta_m = \beta'_m S_m = 200 \frac{\mu A}{V^2}$$

$$\beta_p = \beta'_p S_p = 100 \frac{\mu A}{V^2}$$

$$t_{f90\%} = 745,4 \text{ ps}$$

$$t_{r90\%} = 2 t_{f90\%} = 1490,8 \text{ ps} \approx 1,49 \text{ ns}$$

$$t_{f50\%} = 301 \text{ ps}$$

$$t_{r50\%} = 2 t_{f50\%} = 602 \text{ ps}$$

● TECNOLOGIA B

$$V_{DD} = 1V \quad \beta'_m = 200 \frac{\mu A}{V^2} \quad \beta'_p = 100 \frac{\mu A}{V^2} \quad V_{Tm} = |V_{Tp}| = 0,25V$$

$$L_{min} = 0,09 \mu m = 90 nm \quad C_{ox} = \frac{23 fF}{\mu m^2}$$

- TEMPI DI TRANSITO AL 90%

$$V_{OL} = \frac{V_{DD}}{10} = 0,1V$$

$$V_{OH} = 0,9V \quad V_{DD} - V_{OH} = 0,1V$$

$$F_{m90\%} = F_{p90\%} = \frac{0,25}{0,5625} + \frac{1}{1,5} \ln \frac{1,5 - 0,1}{0,1} =$$

$$= 0,4444 + 1,7593 = 2,203 V^{-1}$$

- TEMPI DI TRANSITO AL 50%

$$V_{OL} = V_{OH} = \frac{V_{DD}}{2} = 0,5V$$

$$F_{m50\%} = F_{p50\%} = \frac{0,25}{0,5625} + \frac{1}{1,5} \ln \frac{1,5 - 0,5}{0,5} =$$

$$= 0,4444 + 0,4621 = 0,906 V^{-1}$$

$$\frac{F_{m90\%B}}{F_{m90\%A}} = \frac{F_{p90\%B}}{F_{p90\%A}} = 3,546$$

$$\frac{F_{m50\%B}}{F_{m50\%A}} = \frac{F_{p50\%B}}{F_{p50\%A}} = 3,611$$

$$C_L = m L_{mim}^2 (S_m + S_p) C_{ox} = 284 \cdot 8,1 \cdot 10^{-3} \cdot \cancel{10^{-12}} \cdot 23 \cdot \frac{10^{-15}}{\cancel{10^{-12}}} = 52,9 \text{ fF}$$

- $S_m = 2$ $S_p = 4$

$$\beta_m = \beta'_m S_m = 400 \frac{\mu A}{V^2} \quad \beta_p = \beta'_p S_p = 400 \frac{\mu A}{V^2}$$

$$t_{f90\%} = t_{r90\%} = \frac{2 \cdot 52,9 \cdot 10^{-15}}{400 \cdot 10^{-6}} \cdot 2,203 = 0,5827 \text{ ns} = 582,7 \text{ ps}$$

$$t_{f50\%} = t_{r50\%} = \frac{2 \cdot 52,9 \cdot 10^{-15}}{400 \cdot 10^{-6}} \cdot 0,906 = 239,6 \text{ ps}$$

- $S_m = 1$ $S_p = 4$

$$\beta_m = \beta'_m S_m = 200 \frac{\mu A}{V^2} \quad \beta_p = \beta'_p S_p = 400 \frac{\mu A}{V^2}$$

$$t_{r90\%} = 582,7 \text{ ps} \quad t_{f90\%} = 2 t_{r90\%} = 1165,4 \text{ ps} = 1,165 \text{ ns}$$

$$t_{r50\%} = 239,6 \text{ ps} \quad t_{f50\%} = 2 t_{r50\%} = 479,2 \text{ ps}$$


- $S_m = 2$ $S_p = 2$

$$\beta_m = \beta'_m S_m = 400 \frac{\mu A}{V^2} \quad \beta_p = \beta'_p S_p = 200 \frac{\mu A}{V^2}$$

$$t_{f90\%} = 582,7 \text{ ps} \quad t_{r90\%} = 2 t_{f90\%} = 1165,4 \text{ ps} = 1,165 \text{ ns}$$

$$t_{f50\%} = 239,6 \text{ ps} \quad t_{r50\%} = 2 t_{f50\%} = 479,2 \text{ ps}$$

• MODELLO RESISTENZA EQUIVALENTE

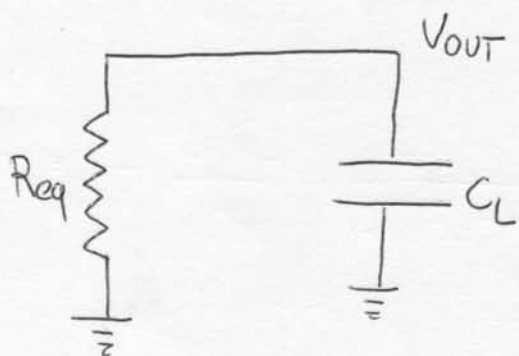

$$V_{OUT}(0) = V_{DD}$$

$$\frac{V_{OUT}}{R_{eq}} = - C_L \frac{dV_{OUT}}{dt}$$

$$\frac{dV_{OUT}}{V_{OUT}} = - \frac{dt}{R_{eq} C_L}$$

$$R_{eq} = \frac{2}{\beta_m} \cdot F_m \cdot \frac{1}{l_m \frac{V_{DD}}{V_{OL}}}$$

$$= \left(\frac{2}{\beta_m} F_m \cdot \frac{1}{l_m \frac{V_{DD}}{V_{OL}}} \right) \cdot \frac{1}{S_m}$$


$$\left[l_m V_{OUT} \right]_{V_{DD}}^{V_{OL}} = - \frac{t_f}{R_{eq} C_L}$$

$$t_f = R_{eq} C_L l_m \frac{V_{DD}}{V_{OL}}$$

$$t_{f_{sox}} = R_{eq} C_L l_m (10)$$

$$t_{f_{sox}} = R_{eq} C_L l_m (2)$$
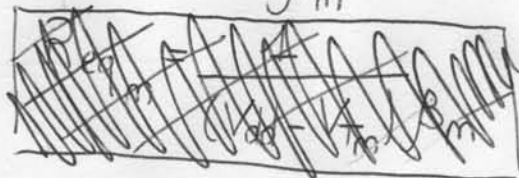
$$R_{eq} \propto \frac{1}{\beta_m} \quad R_{eq} t_{tr, S_m} = 1$$



$$V_{OUT}(0) = 0$$

$$\frac{V_{DD} - V_{OUT}}{R_{eq}} = C_L \frac{dV_{OUT}}{dt}$$


$$\frac{dV_{OUT}}{V_{DD} - V_{OUT}} = \frac{dt}{R_{eq} C_L}$$

$$- l_m \left(\frac{V_{DD} - V_{OH}}{V_{DD}} \right) = \frac{t_r}{R_{eq} C_L}$$

$$t_r = R_{eq} C_L l_m \left(\frac{V_{DD}}{V_{DD} - V_{OH}} \right)$$

$$t_{r_{sox}} = R_{eq} C_L l_m (10)$$

$$t_{r_{sox}} = R_{eq} C_L l_m (2)$$

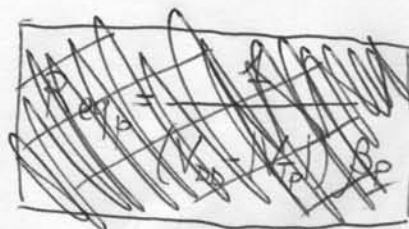

~~VDD - VOH~~

$$t_{f_{sox}} = \frac{2 C_L}{\beta_m} F_{m_{sox}} = \frac{2 C_L}{\beta'_m S_m} F_{m_{sox}} = \frac{1}{S_m} \left(\frac{2 F_{m_{sox}}}{\beta'_m} \right) C_L$$

$$t_{f_{sox}} = R_{m_{eq_{sox}}} C_L \ln(10)$$

$$R_{m_{eq_{sox}}} \ln(10) = \frac{1}{S_m} \left(\frac{2 F_{m_{sox}}}{\beta'_m} \right)$$

$$R_{m_{eq_{sox}}} = \frac{1}{S_m} \left(\frac{2 F_{m_{sox}}}{\beta'_m \ln(10)} \right) = \frac{R_{m_{eq_{sox}, s=1}}}{S_m}$$

Quindi:

$$R_{m_{eq_{sox}, s=1}} = \frac{2 F_{m_{sox}}}{\beta'_m \ln(10)}$$

$$R_{p_{eq_{sox}, s=1}} = \frac{2 F_{p_{sox}}}{\beta'_p \ln(10)}$$

$$R_{m_{eq_{sox}, s=1}} = \frac{2 F_{m_{sox}}}{\beta'_m \ln(2)}$$

$$R_{p_{eq_{sox}, s=1}} = \frac{2 F_{p_{sox}}}{\beta'_p \ln(2)}$$

• TECNOLOGIA A

$$R_{m \text{ eq } 90\%, s=1} = \frac{2 \cdot 0,6212}{100 \cdot 10^{-6} \cdot 2,3026} = 5,395 \text{ k}\Omega$$

$$R_{p \text{ eq } 90\%, s=1} = 10,79 \text{ k}\Omega$$

$$R_{m \text{ eq } 50\%, s=1} = \frac{2 \cdot 0,2509}{100 \cdot 10^{-6} \cdot 0,6931} = 7,24 \text{ k}\Omega$$

$$R_{p \text{ eq } 50\%, s=1} = 14,48 \text{ k}\Omega$$

• TECNOLOGIA B

$$R_{m \text{ eq } 90\%, s=1} = \frac{2 \cdot 2,203}{200 \cdot 10^{-6} \cdot 2,3026} = 9,567 \text{ k}\Omega$$

$$R_{p \text{ eq } 90\%, s=1} = 19,134 \text{ k}\Omega$$

$$R_{m \text{ eq } 50\%, s=1} = \frac{2 \cdot 0,906}{200 \cdot 10^{-6} \cdot 0,6931} = 13,071 \text{ k}\Omega$$

$$R_{p \text{ eq } 50\%, s=1} = 26,142 \text{ k}\Omega$$


Se TECNOLOGIA (A) $S_p = 4$

$$t_{r_{sox}} = \frac{14,48 \cdot 10^3}{4} \cdot 120 \cdot 10^{-15} \cdot 0,6931 = 301 \text{ ps}$$

Se TECNOLOGIA (B) $S_m = 2$

$$t_{f_{sox}} = \frac{9,567 \cdot 10^3}{2} \cdot 52,9 \cdot 10^{-15} \cdot 2,3026 = 582,6 \text{ ps}$$

NOR CMOS

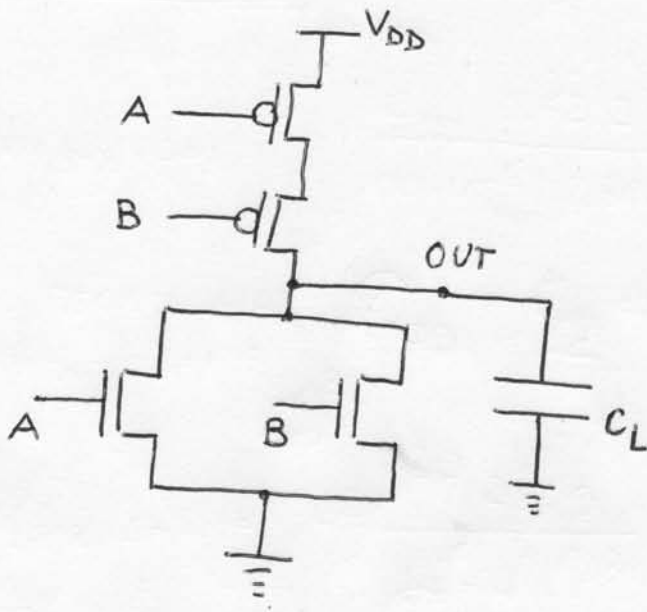

| A | B | OUT |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

mMOS com fattore di forma S_m
 pMOS com fattore di forma S_p

- tempo di salita t_r

$$S_{PU} = \frac{S_p}{2}$$

$$t_r = \frac{2 C_L}{\beta'_p S_{PU}} F_p = \frac{2 C_L}{\beta'_p \frac{S_p}{2}} F_p = \frac{4 C_L}{\beta'_p S_p} F_p$$

- tempo di discesa t_f

(a) A B : 00 \longrightarrow 01
 10

$$S_{PD} = S_m \quad \left(\begin{array}{l} \text{CASO} \\ \text{PEGGIORE} \end{array} \right)$$

$$t_f = \frac{2 C_L}{\beta'_m S_N} F_m$$

(b) A B : 00 \longrightarrow 11

$$S_{PD} = 2 S_N$$

$$t_f = \frac{2 C_L}{\beta'_m 2 S_N} F_m = \frac{C_L}{\beta'_m S_N} F_m$$

Se vogliamo $t_r = t_f$ (caso peggiore)

$$\frac{4 C_L}{\beta'_p S_p} F_p = \frac{2 C_L}{\beta'_m S_m} F_m$$

$$\frac{S_p}{S_m} = 2 \frac{F_p}{F_m} \cdot \frac{\beta'_m}{\beta'_p} = 2 \cdot \frac{1}{1} = 2 = 4$$

• TECNOLOGIA A ($C_L = 120 \text{ fF}$)

- $S_m = 2$ $S_p = 4 S_m = 8$

$$t_{r_{90\%}} = \frac{4 C_L F_m}{\beta'_p S_p} = \frac{4 \cdot 120 \cdot 10^{-15}}{50 \cdot 10^{-6} \cdot 8} = 1,2 \text{ ns} = 1200 \text{ ps}$$

$$t_{f_{90\%} \text{ peggiore}} = 745,44 \text{ ps}$$

$$t_{r_{50\%}} = t_{f_{90\%} \text{ peggiore}} = \frac{4 \cdot 120 \cdot 10^{-15}}{50 \cdot 10^{-6} \cdot 8} \cdot 0,2509 = 301 \text{ ps}$$

- $S_m = 2$ $S_p = 2$

$$t_{f_{90\%} \text{ peggiore}} = 745,44 \text{ ps}$$

$$t_{r_{90\%}} = 2,98 \text{ ns} = 4 \cdot t_{f_{90\%} \text{ peggiore}}$$

$$t_{f_{50\%} \text{ peggiore}} = 301 \text{ ps}$$

$$t_{r_{50\%}} = 4 t_{f_{50\%} \text{ peggiore}} = 1,204 \text{ ns}$$

- $S_m = 8$ $S_p = 8$

$$t_{r_{90\%}} = 745,44 \text{ ps}$$

$$t_{f_{90\%} \text{ peggiore}} = \frac{t_{r_{90\%}}}{4} = 186,36 \text{ ps}$$

$$t_{r_{50\%}} = 301 \text{ ps}$$

$$t_{f_{50\%} \text{ peggiore}} = \frac{t_{r_{50\%}}}{4} = 75,25 \text{ ps}$$

• TECNOLOGIA B ($C_L = 52,9 \text{ fF}$)

- $S_m = 2$ $S_p = 4 S_m = 8$

$$t_{r_{90\%}} = \frac{4 C_L}{\beta'_p S_p} F_{p_{90\%}} = \frac{4 \cdot 52,9 \cdot 10^{-15}}{100 \cdot 10^{-6} \cdot 8} \cdot 2,203 = 582,7 \text{ ps} = t_{f_{90\%} \text{ peggiore}}$$

$$t_{r_{50\%}} = \frac{4 \cdot 52,9 \cdot 10^{-15}}{100 \cdot 10^{-6} \cdot 8} \cdot 0,906 = 239,6 \text{ ps} = t_{f_{50\%} \text{ peggiore}}$$

- $S_m = 2$ $S_p = 2$

$$t_{f_{90\%} \text{ peggiore}} = 582,7 \text{ ps}$$

$$t_{r_{90\%}} = 4 \cdot t_{f_{90\%} \text{ peggiore}} = 2,33 \text{ ns}$$

$$t_{f_{50\%} \text{ peggiore}} = 239,6 \text{ ps}$$

$$t_{r_{50\%}} = 4 \cdot t_{f_{50\%} \text{ peggiore}} = 958,4 \text{ ps}$$

- $S_m = 8$ $S_p = 8$

$$t_{r_{90\%}} = 582,7 \text{ ps}$$

$$t_{f_{90\%} \text{ peggiore}} = \frac{t_{r_{90\%}}}{4} = 145,67 \text{ ps}$$

$$t_{r_{50\%}} = 239,6 \text{ ps}$$

$$t_{f_{50\%} \text{ peggiore}} = \frac{t_{r_{50\%}}}{4} = 59,9 \text{ ps}$$

METODO DELLA RESISTENZA EQUIVALENTE

• TECNOLOGIA A $C_L = 120 \text{ fF}$ $S_m = 8$ $t_{f_{90\%}} = ?$

$$S_{PD \text{ peggiore}} = S_m = 8$$

$$R_{PD \text{ eq } 90\%} = \frac{R_{meq \ 90\%, \ s=1}}{8} = 674,37 \ \Omega$$

$$t_{f_{90\%}} = R_{PD \text{ eq } 90\%} \cdot C_L \cdot \ln(10) = 674,37 \cdot 120 \cdot 10^{-15} \cdot 2,3025 = 186,32 \text{ ps}$$


• TECNOLOGIA B $C_L = 52,9 \text{ fF}$ $S_P = 2$ $t_{r_{50\%}} = ?$

$$S_{PU} = \frac{S_P}{2} = 1$$

$$R_{eq_{PU, 50\%}} = R_{eq_{p, 50\%, S=1}} = 26,142 \text{ k}\Omega$$

$$t_{r_{50\%}} = R_{eq_{PU, 50\%}} \cdot C_L \cdot \ln(2) = 26,142 \cdot 10^3 \cdot 52,9 \cdot 10^{-15} \cdot 0,6931 =$$
$$= 958,49 \text{ ps}$$

NAND CMOS

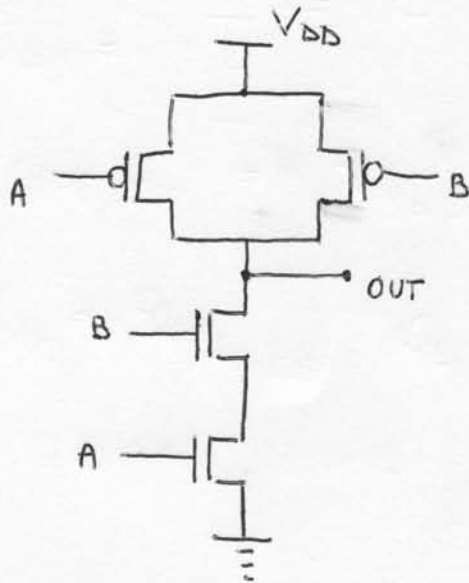

| A | B | OUT |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

$$S_{PD} = \frac{S_N}{2}$$

$$t_f = \frac{2 C_L}{\beta'_m S_{PD}} \cdot F_m = \frac{4 C_L}{\beta'_m S_m} \cdot F_m$$

- tempo di salita:

(a) A, B: ~~11~~ \rightarrow $\begin{matrix} 01 \\ 10 \end{matrix}$

$$t_r = \frac{2 C_L F_P}{\beta'_p S_P} \quad (\text{caso peggiore})$$

A, B: $11 \rightarrow 00$ entrambi i pMOS accesi
 $S_{PU} = 2 S_P$

$$t_r = \frac{2 C_L}{\beta'_p 2 S_P} F_P = \frac{C_L}{\beta'_p S_P} F_P$$

Se vogliamo $t_f = t_r$ peggiore

$$\frac{4 C_L}{\beta'_m S_m} F_m = \frac{2 C_L}{\beta'_p S_p} F_p$$

$$\frac{S_m}{S_p} = 2 \frac{\beta'_p}{\beta'_m} \cdot \frac{F_m}{F_p} = 2 \cdot \frac{1}{2} \cdot 1 = 1$$

● TECNOLOGIA A $C_L = 120 \text{ fF}$

- $S_m = 4$ $S_p = 4$

$$t_{f90\%} = \frac{C_L}{\beta'_m} F_{m90\%} = \frac{120 \cdot 10^{-15}}{100 \cdot 10^{-6}} \cdot 0,6212 = 745,44 \text{ ps}$$

$$t_{r90\% \text{ peggiore}} = 745,44 \text{ ps}$$

→ $t_{f50\%} = \frac{120 \cdot 10^{-15}}{100 \cdot 10^{-6}} \cdot 0,2509 = 301 \text{ ps}$

$$t_{r50\% \text{ peggiore}} = 301 \text{ ps}$$

- $S_m = 1$ $S_p = 4$

$$t_{r90\% \text{ peggiore}} = 745,44 \text{ ps}$$

$$t_{f90\%} = 4 \cdot t_{r90\% \text{ peggiore}} = 2,98 \text{ ms}$$

$$t_{r50\% \text{ peggiore}} = 301 \text{ ps}$$

$$t_{f50\%} = 4 \cdot t_{r50\% \text{ peggiore}} = 1,204 \text{ ms}$$

$$S_m = 4 \quad S_p = 1$$

$$t_{f_{sox}} = 745,44 \text{ ps}$$

$$t_{r_{sox}} \text{ peggiore} = 4 \cdot t_{f_{sox}} = 2,98 \text{ ns}$$

$$t_{f_{sox}} = 301 \text{ ps}$$

$$t_{r_{sox}} \text{ peggiore} = 4 \cdot t_{f_{sox}} = 1,204 \text{ ns}$$

• TECNOLOGIA B $C_L = 52,9 \text{ fF}$

- $S_m = 4$ $S_p = 4$

$$t_{fsox} = \frac{4 \cdot 52,9 \cdot 10^{-15}}{200 \cdot 10^{-6} \cdot 4} \cdot 2,203 = 582,7 \text{ ps}$$

$$t_{rsox} \text{ peggiore} = 582,7 \text{ ps}$$

$$t_{fsox} = \frac{4 \cdot 52,9 \cdot 10^{-15}}{200 \cdot 10^{-6} \cdot 4} \cdot 0,906 = 239,6 \text{ ps}$$

$$t_{rsox} \text{ peggiore} = 239,6 \text{ ps}$$

- $S_m = 1$ $S_p = 4$

$$t_{rsox} \text{ peggiore} = 582,7 \text{ ps}$$

$$t_{fsox} = 4 \cdot t_{rsox} \text{ peggiore} = 2,33 \text{ ms}$$

$$t_{rsox} \text{ peggiore} = 239,6 \text{ ps}$$

$$t_{fsox} = 4 \cdot t_{rsox} \text{ peggiore} = 958,4 \text{ ps}$$

- $S_m = 4$ $S_p = 1$

$$t_{fsox} = 582,7 \text{ ps}$$

$$t_{rsox} \text{ peggiore} = 4 \cdot t_{fsox} = 2,33 \text{ ms}$$

$$t_{fsox} = 239,6 \text{ ps}$$

$$t_{rsox} \text{ peggiore} = 4 \cdot t_{fsox} = 958,4 \text{ ps}$$

METODO DELLA RESISTENZA EQUIVALENTE

A) TECNOLOGIA A $C_L = 120 \text{ fF}$ $S_m = 1$ $t_{f, \text{sox}} = ?$

$$S_{PD} = \frac{S_m}{2} = 0,5$$

$$R_{\text{eq}_{\text{sox}} \text{ PD}} = \frac{R_{\text{meq}_{\text{sox}} \text{ , } S=1}}{S_{PD}} = 10,79 \text{ k}\Omega$$

$$t_{f, \text{sox}} = R_{\text{eq}_{\text{sox}} \text{ PD}} \cdot C_L \ln(10) = 10,79 \cdot 10^3 \cdot 120 \cdot 10^{-15} \cdot 2,3025 = 2,98 \text{ ns}$$

B) TECNOLOGIA B $C_L = 52,9 \text{ fF}$ $S_p = 4$ $t_{r, \text{sox. peggiore}} = ?$

$$S_{PU} = S_p = 4$$

$$R_{\text{eq}_{\text{sox}} \text{ PU}} = \frac{R_{\text{p eq}_{\text{sox}} \text{ , } S=1}}{S_{PU}} = 6,5355 \text{ k}\Omega$$

$$t_{r, \text{sox. peggiore}} = R_{\text{eq}_{\text{sox}} \text{ PU}} \cdot C_L \cdot \ln(2) = 6,5355 \cdot 10^3 \cdot 52,9 \cdot 10^{-15} \cdot 0,6931 = 239,6 \text{ ps}$$