

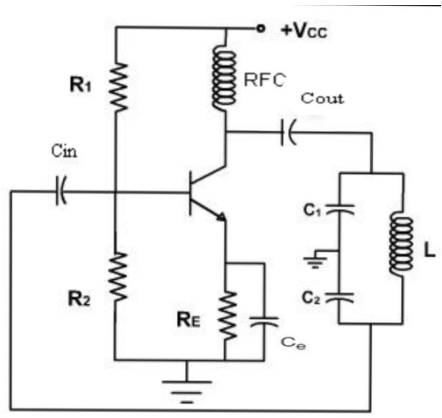
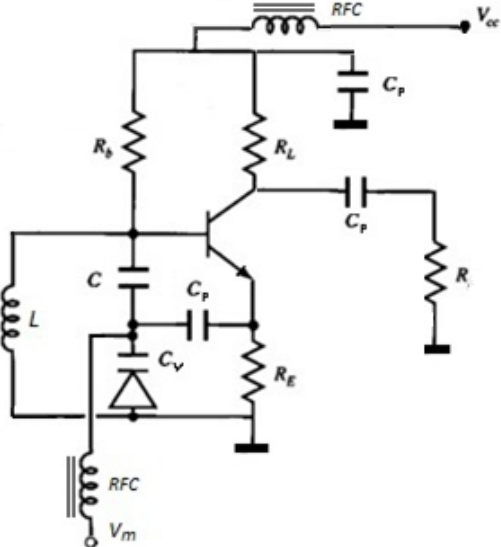
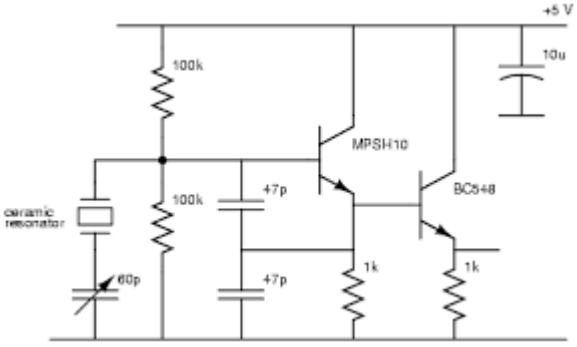
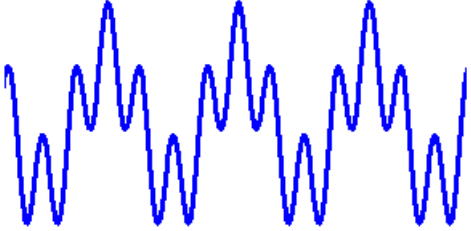


RF OSCILLATORS

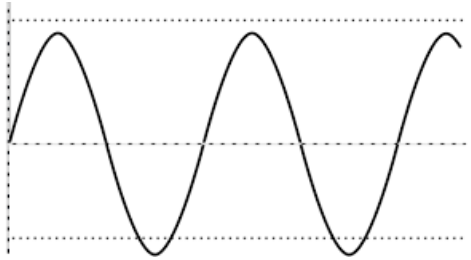






RF OSCILLATORS

Problem motivation





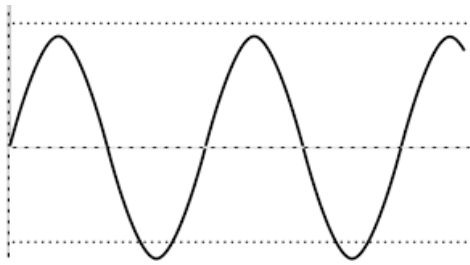


IDEALLY ...


BUT...

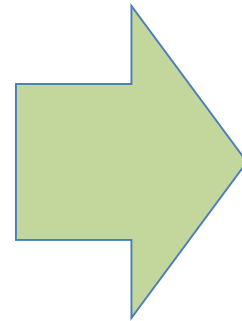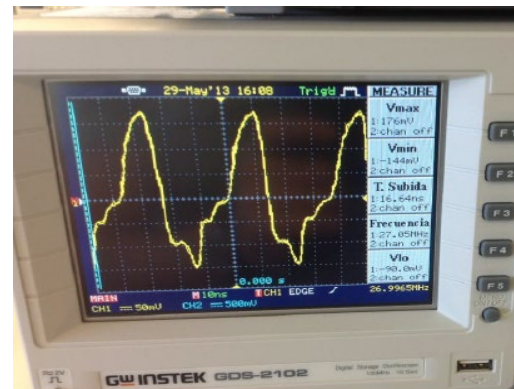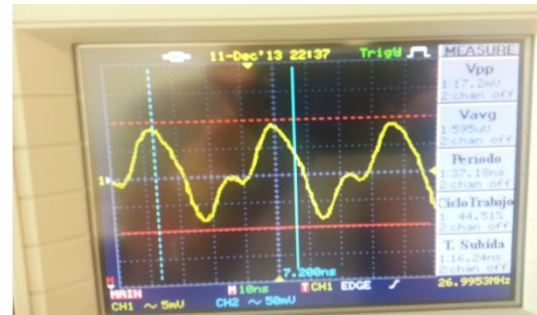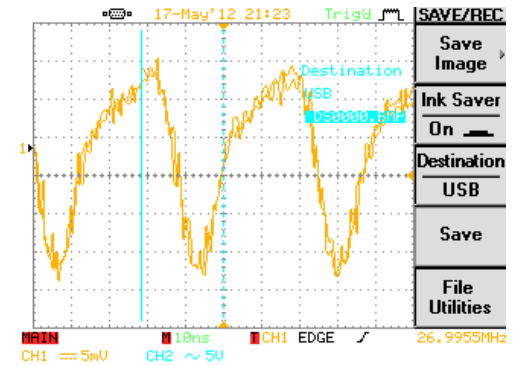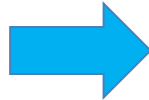

RF OSCILLATORS

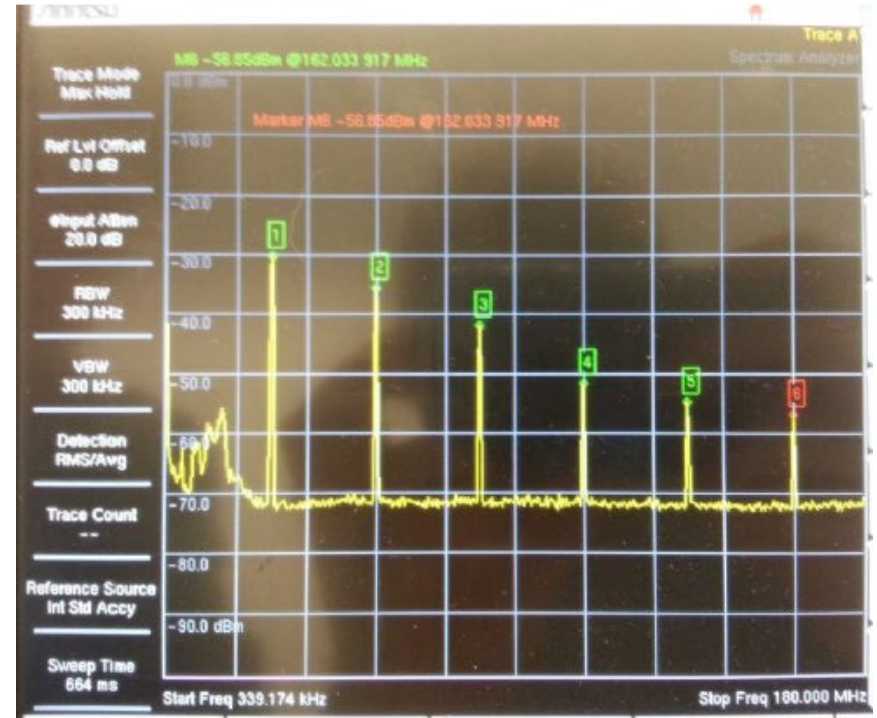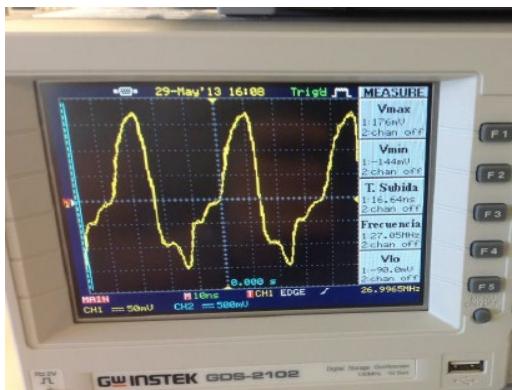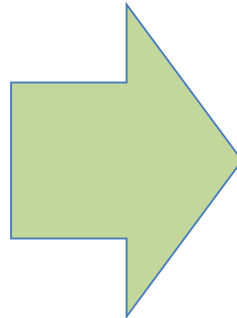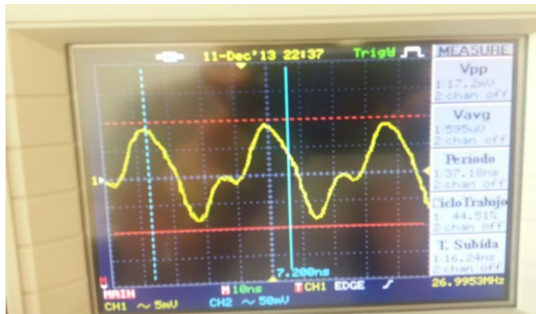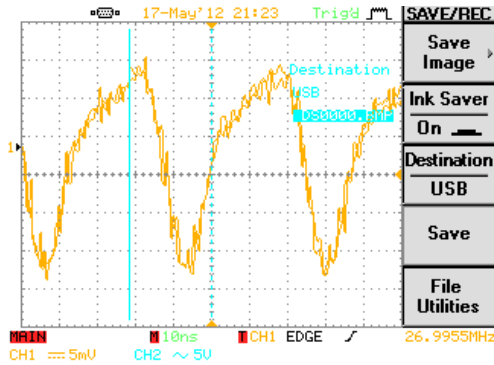


BASIC RF OSCILLATORS

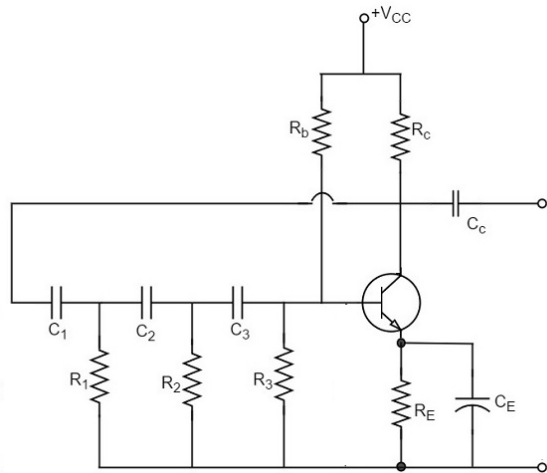


RC oscillators (phase shift) :

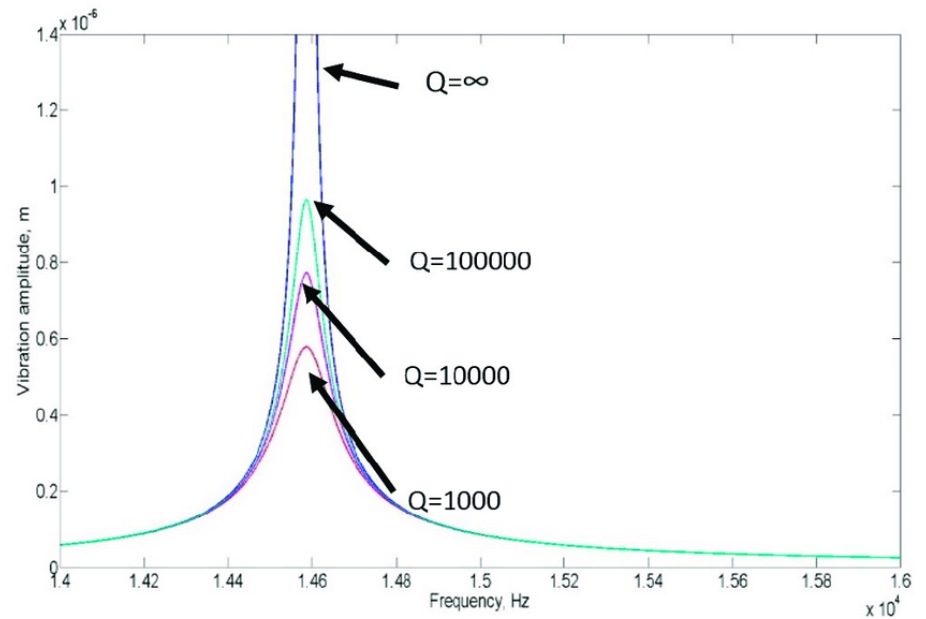- Poor frequency selectivity.
- Low Q .
- Low frequency stability.
- Not too suitable for RF communication circuits.



BASIC RF OSCILLATORS


COLPITTS

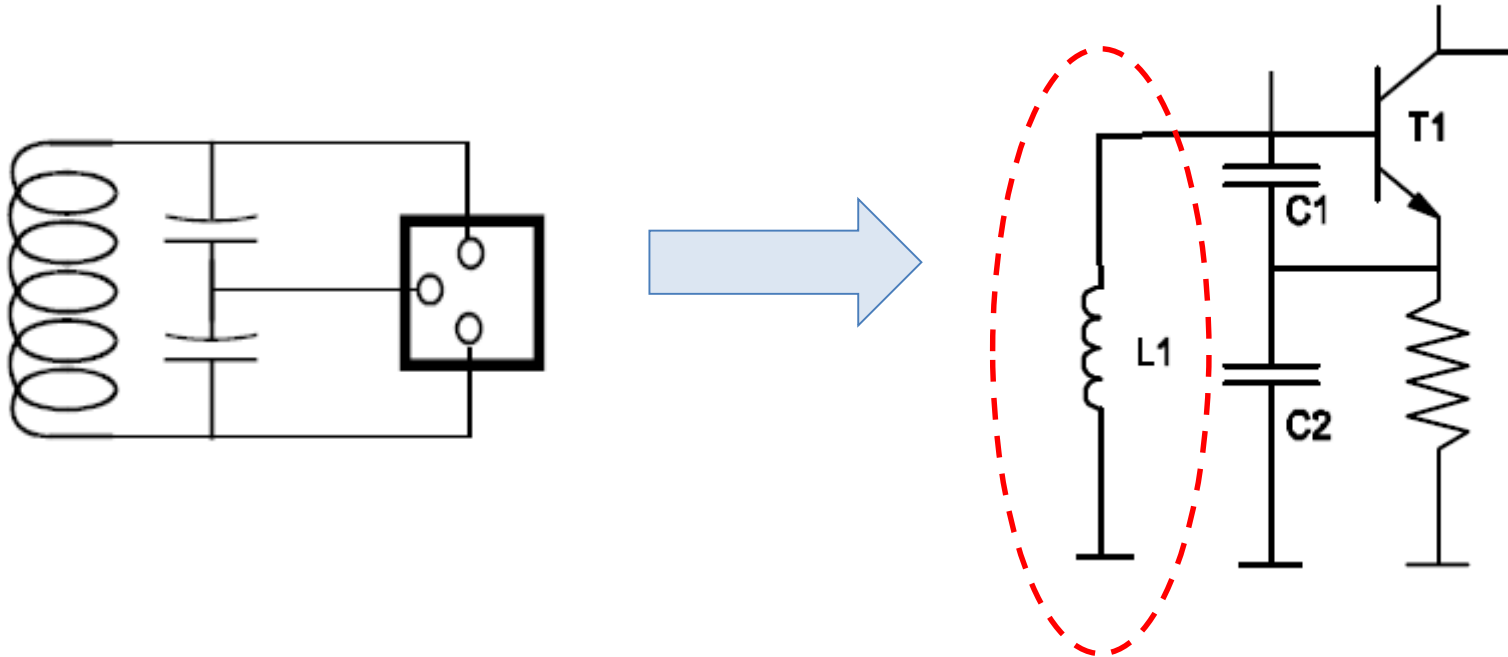

“artistic plot” : This inductor destroys the DC biasing of the transistor



BASIC RF OSCILLATORS

COLPITTS

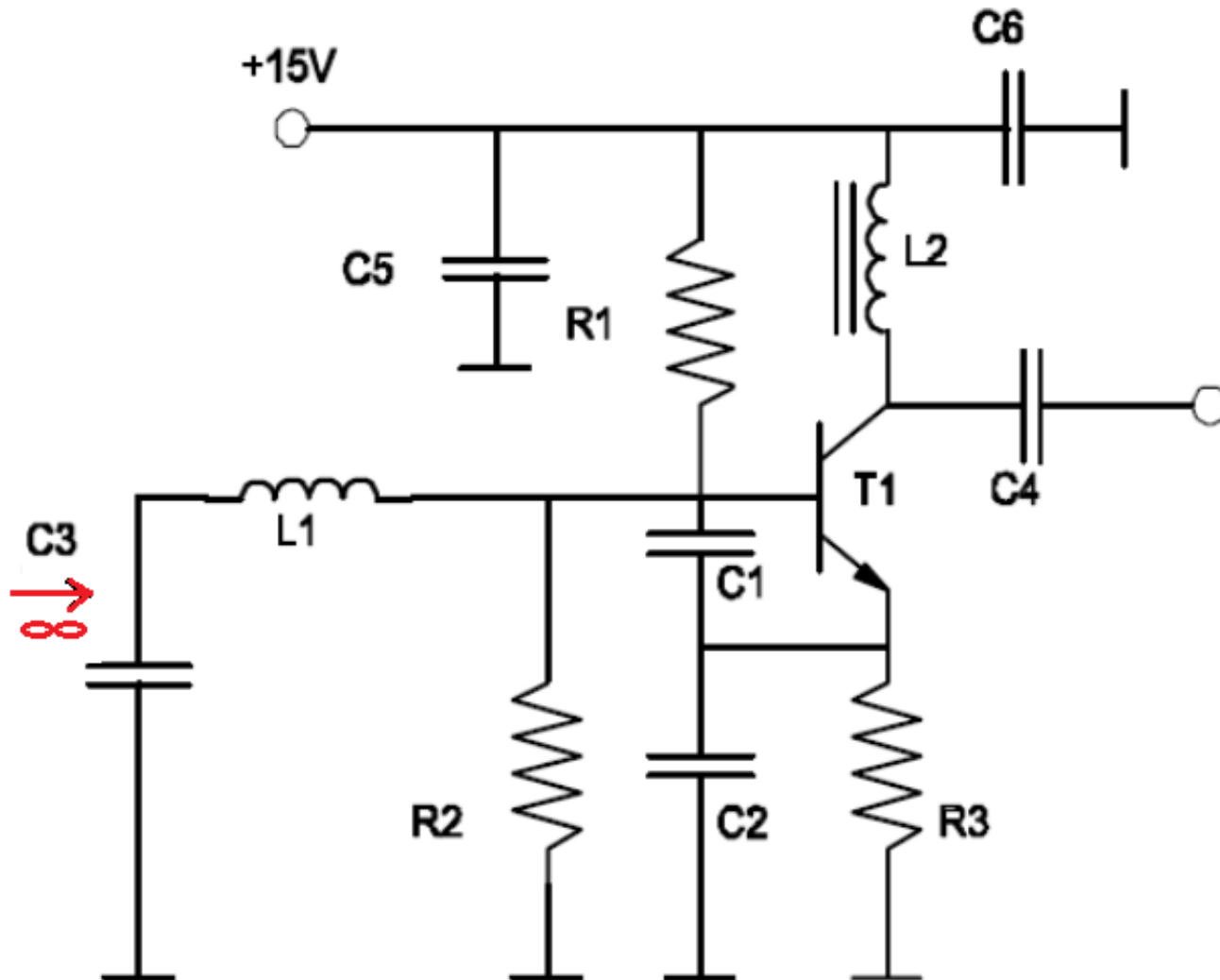

OSCILLATORS

CAVITY OSCILLATORS

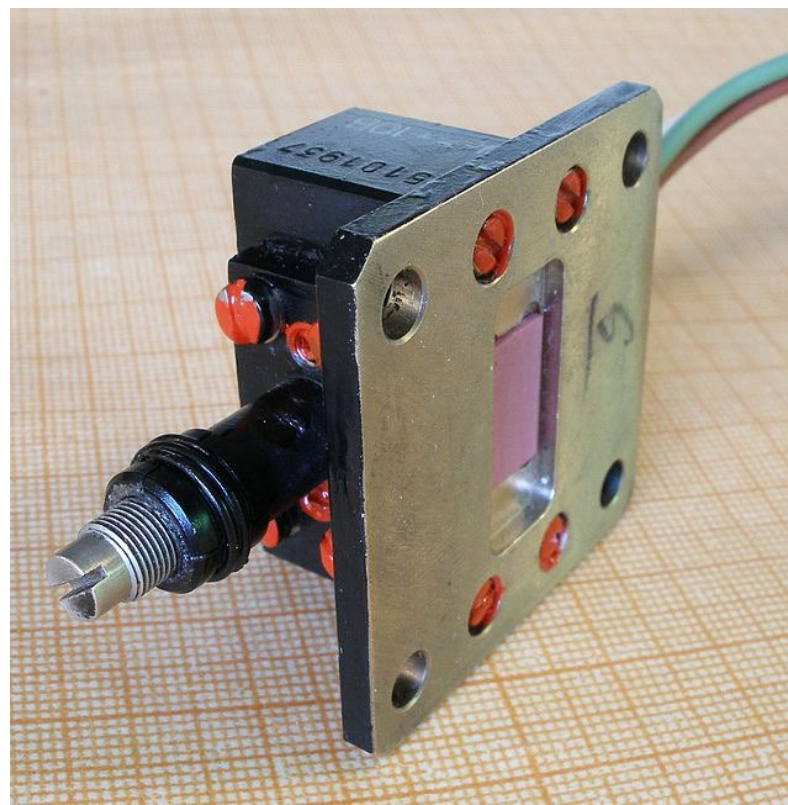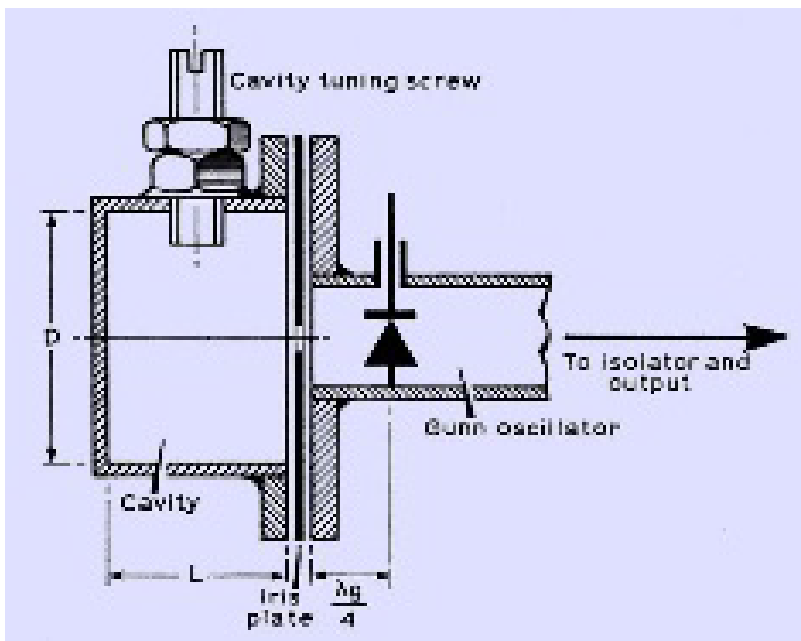

RF OSCILLATORS




VARICAPS

VOLTAGE CONTROLLED OSCILLATORS (VCO)

VARICAP (VARACTOR)

VARIABLE CAPACITANCE

(DO NOT CONFUSS with VARISTOR) !!

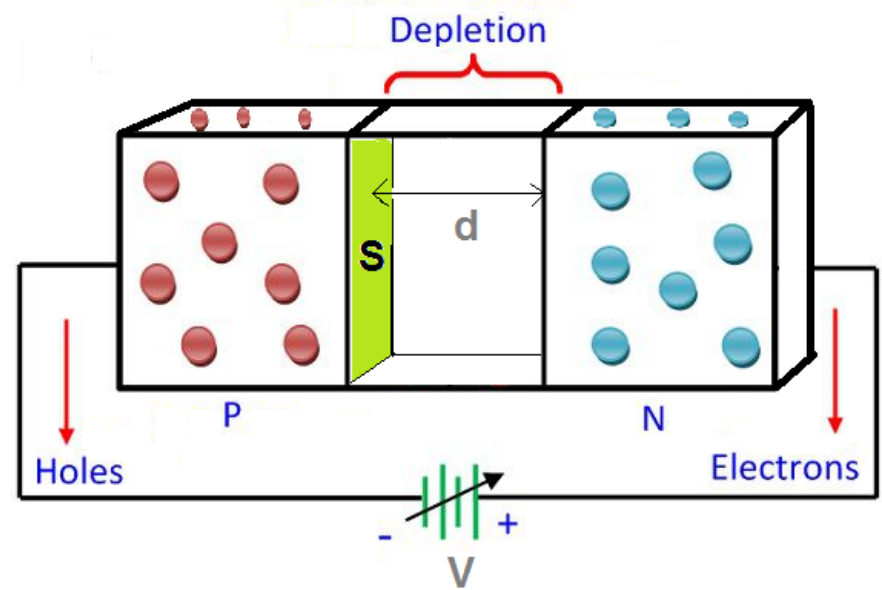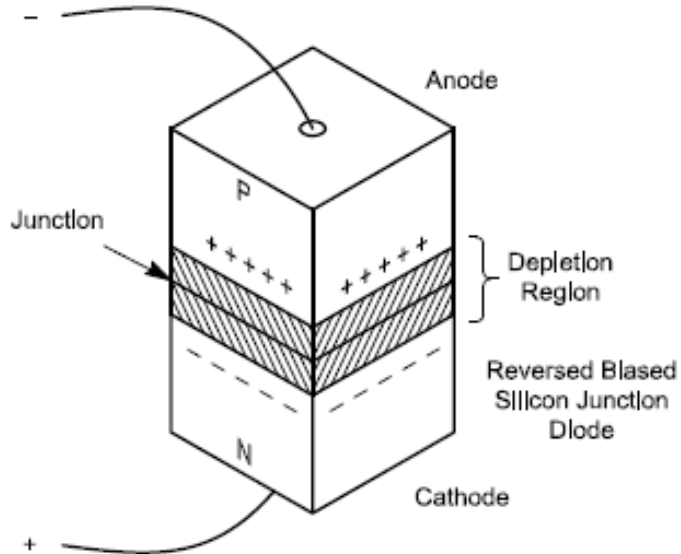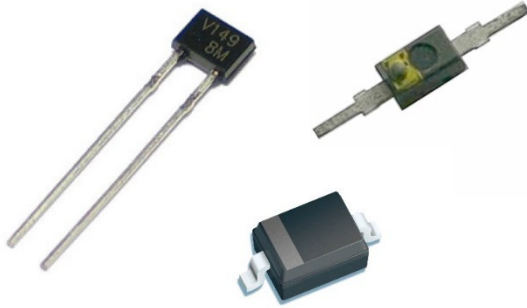


$$d \sim f(V)$$

$$C \sim \epsilon \frac{S}{d} \rightarrow C \sim f(V)$$

V reverse !





VARICAP (VARACTOR)

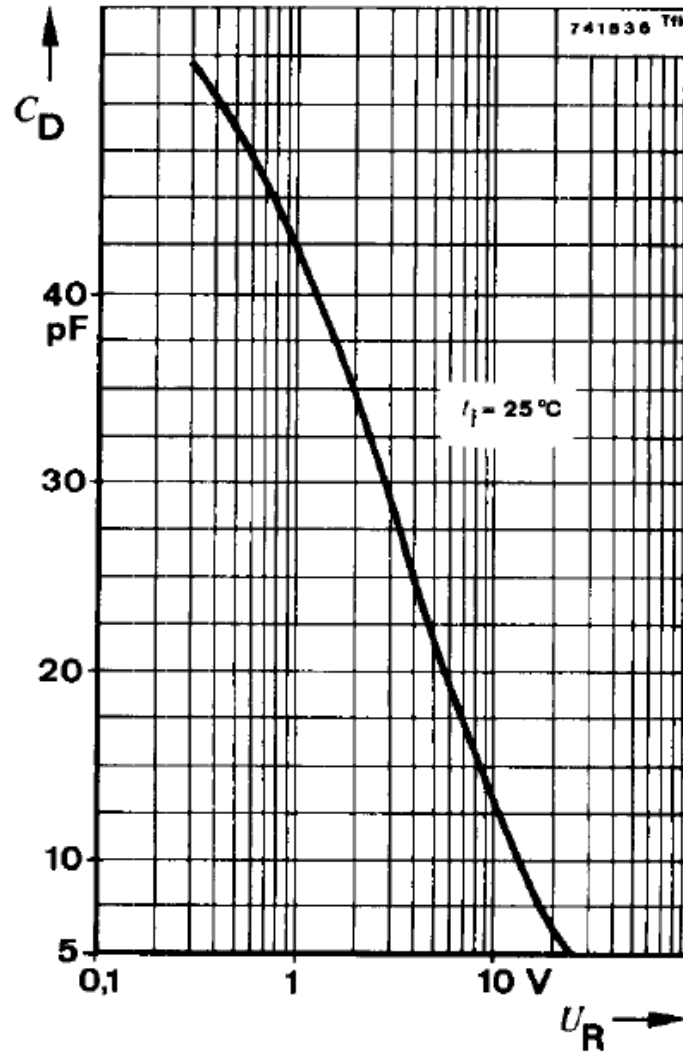

VCO


Voltage-Controlled Oscillator

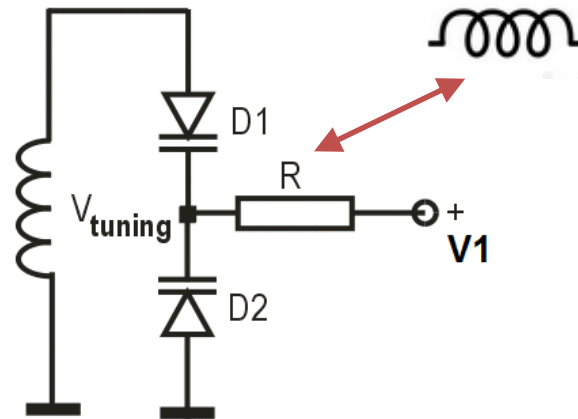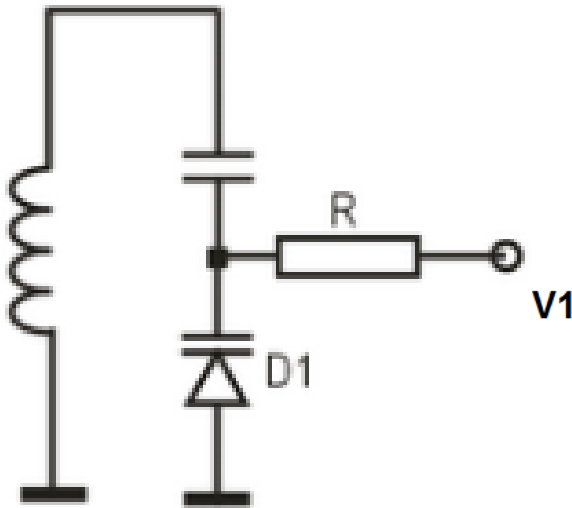(not necessarily with a Varicap, but usual at RF frequencies)




$V1 = V_{\text{tuning}}$ (independently or R)

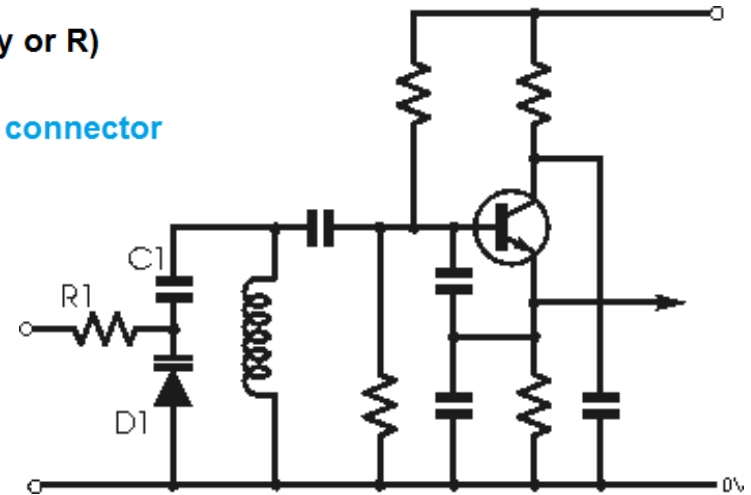if R \uparrow , no signal loss through the tuning connector



VARICAP (VARACTOR)

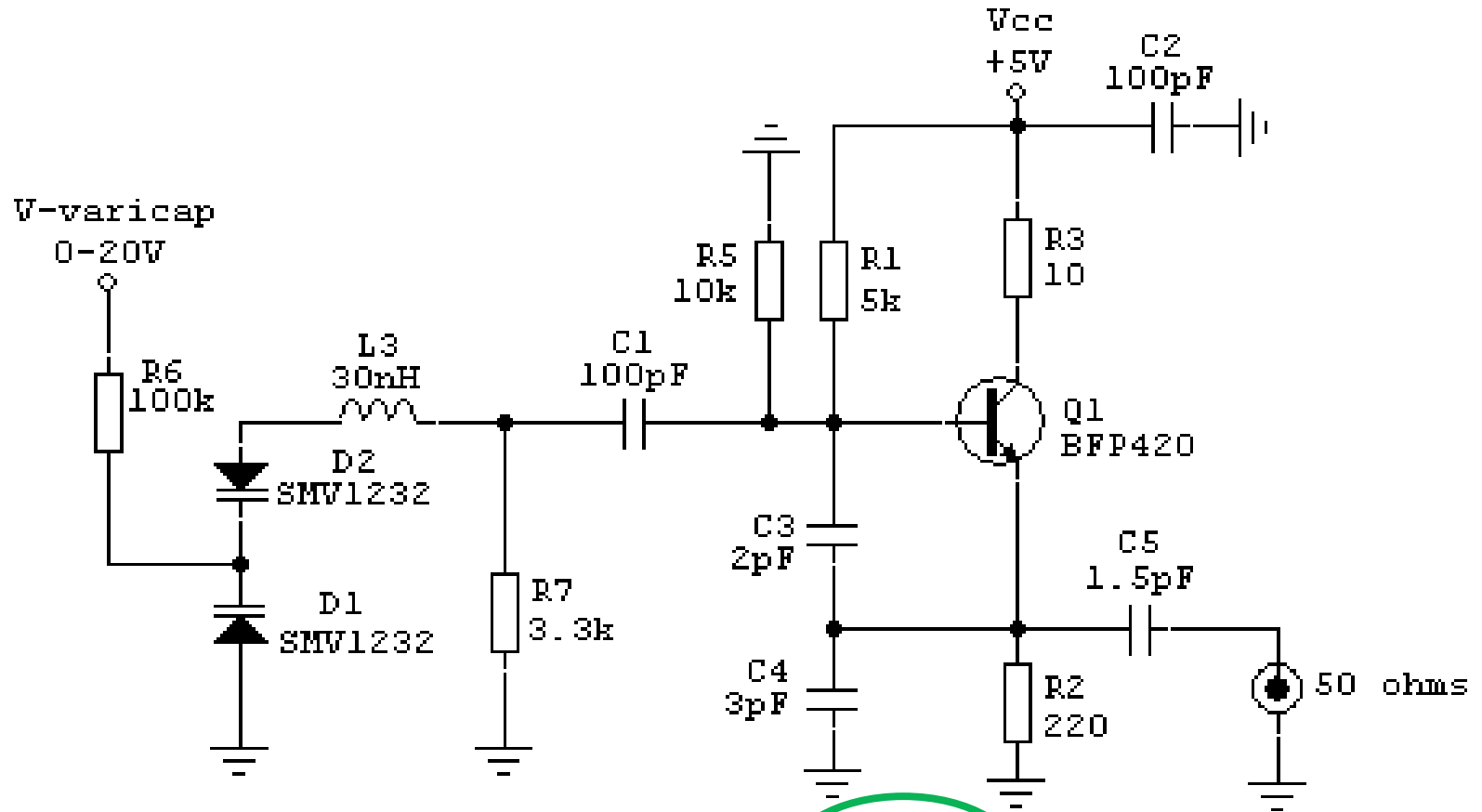





950MHz-2200MHz Colpitts VCO

???




CRYSTAL OSCILLATOR

(Quartz Crystals)

QUARTZ CRYSTAL OSCILLATOR

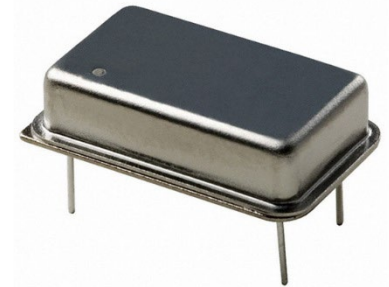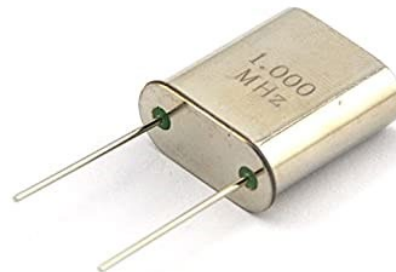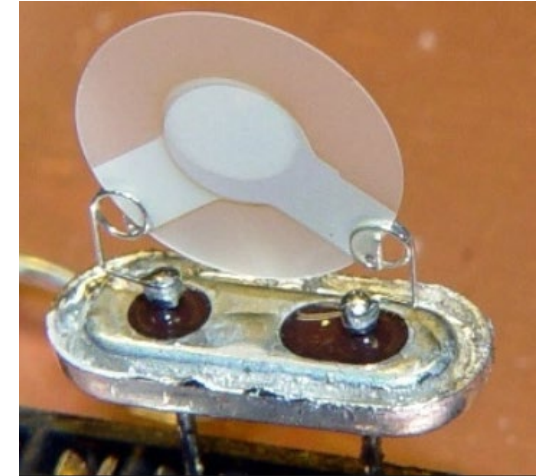
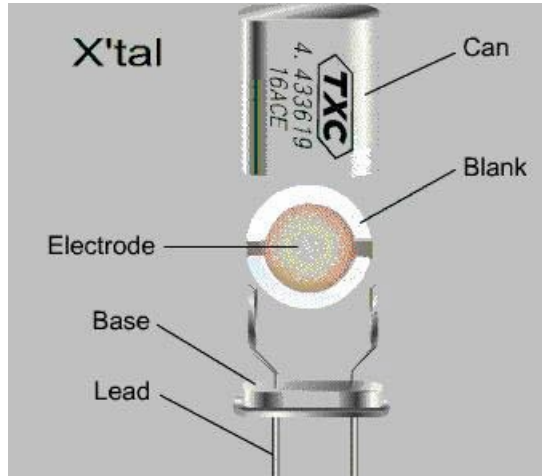


QUARTZ CRYSTAL OSCILLATOR

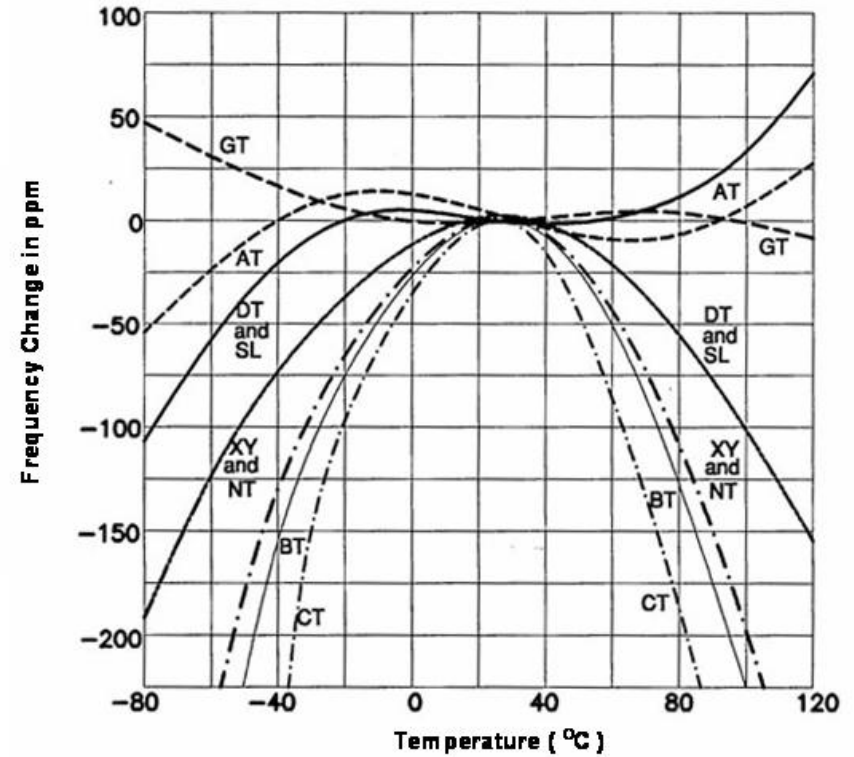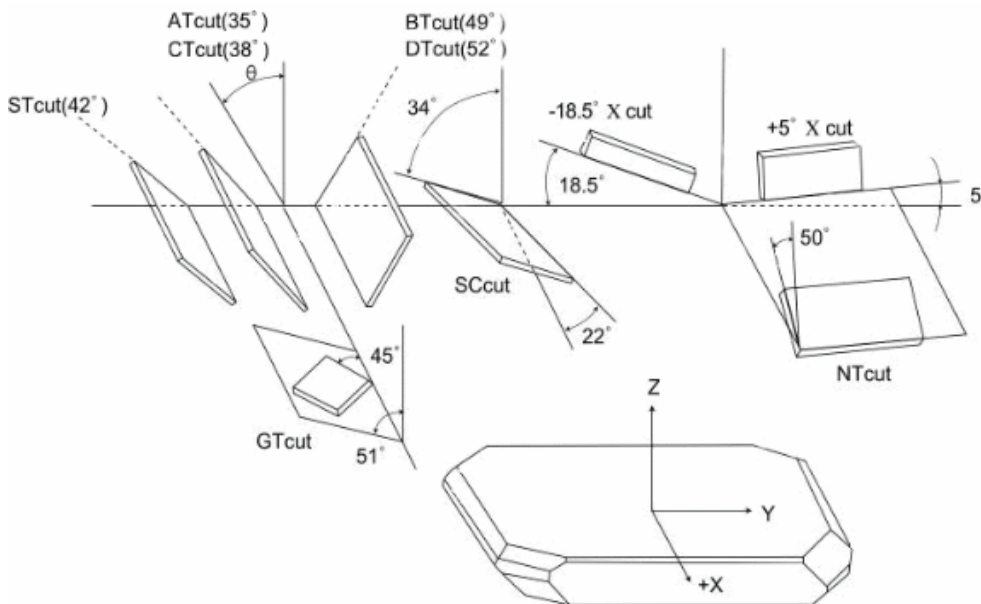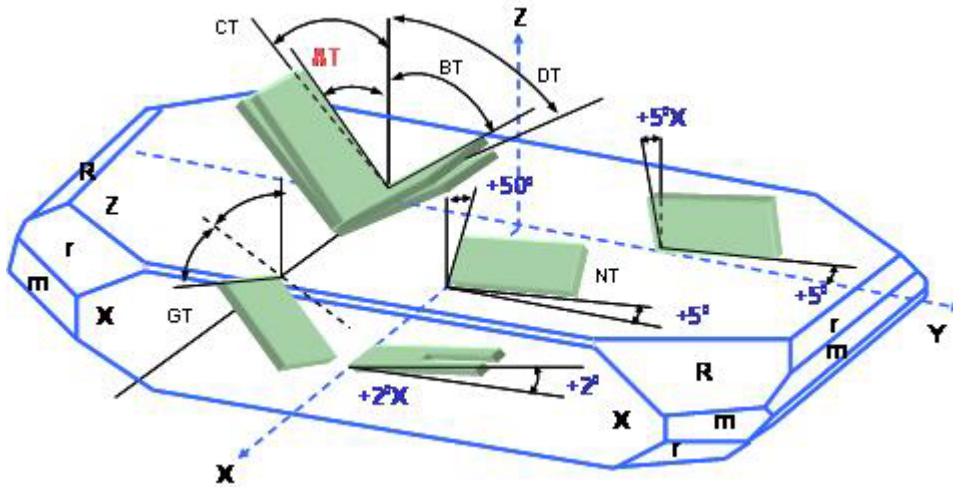


VARICAP (VARACTOR)


Colpitts Crystal Oscillators

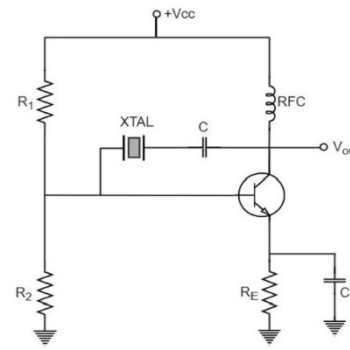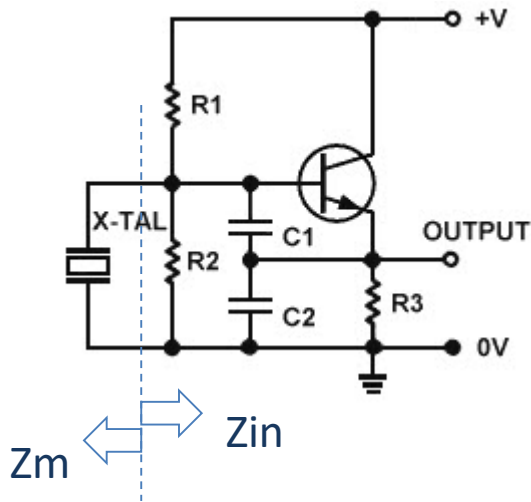

Series resonance

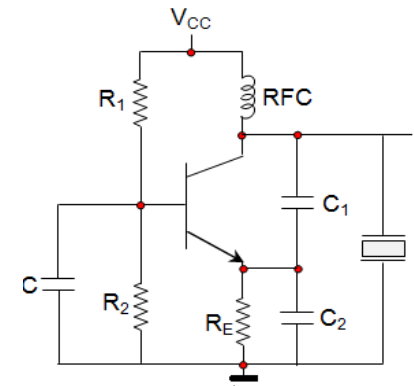

Parallel resonance

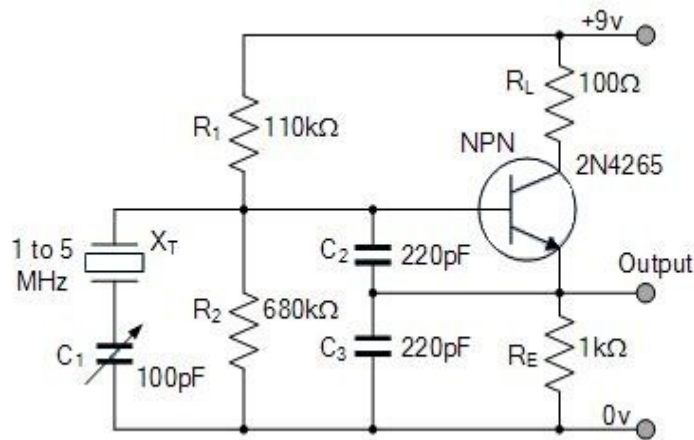

On supplying the power to the oscillator, the amplitude of the oscillations increases until a point where the **NONLINEAR** amplifier sets the loop gain to unity (Barkhausen gain requirement). The frequency will self-adjust (series or parallel resonance) so as to facilitate the crystal to present a reactance to the circuit to fulfill the Barkhausen phase requirement (so, not all the circuits with two poles in the imaginary axis are oscillators in practice).

The desired operating frequency of the **parallel resonant crystal is often set 100 ppm or so above the series resonant frequency**; if the oscillator stability is better than 100 ppm the resonance can be tuned with a capacitance.

FREQUENCY STABILITY

FREQUENCY STABILITY


CONTROLLED CRYSTAL OSCILLATORS

Oven Controlled Crystal Oscillators (OCXO)

Typical Temperature Stability: $\pm 1 \times 10^{-7}$ to $\pm 1 \times 10^{-9}$

Typical aging rate: $\pm 2 \times 10^{-7}$ /year to $\pm 2 \times 10^{-8}$ /year

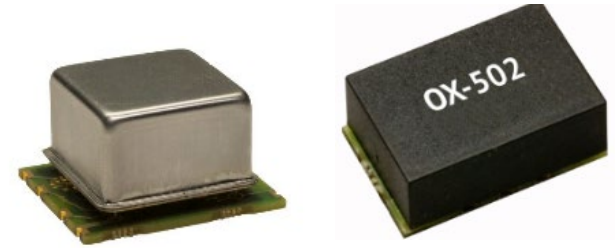Typical Power Consumption: 1.5 Watts to 2.0 Watts



Temperature Controlled Crystal Oscillators (TCXO)

Typical Temperature Stability: ± 0.20 ppm to ± 2.0 ppm

Typical aging rate: ± 0.50 ppm/year to ± 2 ppm/year





Voltage Controlled Crystal Oscillators (VCXO)

Typical deviation ranges: ± 10 ppm to as much as ± 2000 ppm.


Typical aging rate: ± 1 ppm/year to ± 5 pp/year

	Clock Oscillator	TCXO	OCXO
0°C to 70°C	± 10 ppm	± 0.5 ppm	± 0.003 ppm
-20°C to 70°C	± 25 ppm	± 0.5 ppm	± 0.003 ppm
-40°C to 85°C	± 30 ppm	± 1 ppm	± 0.02 ppm
-55°C to 125°C	± 50 ppm	N/A	N/A

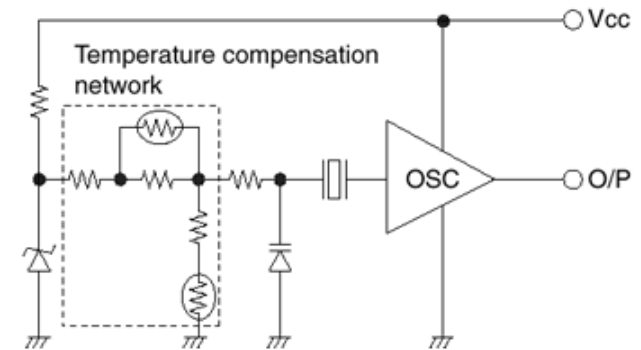

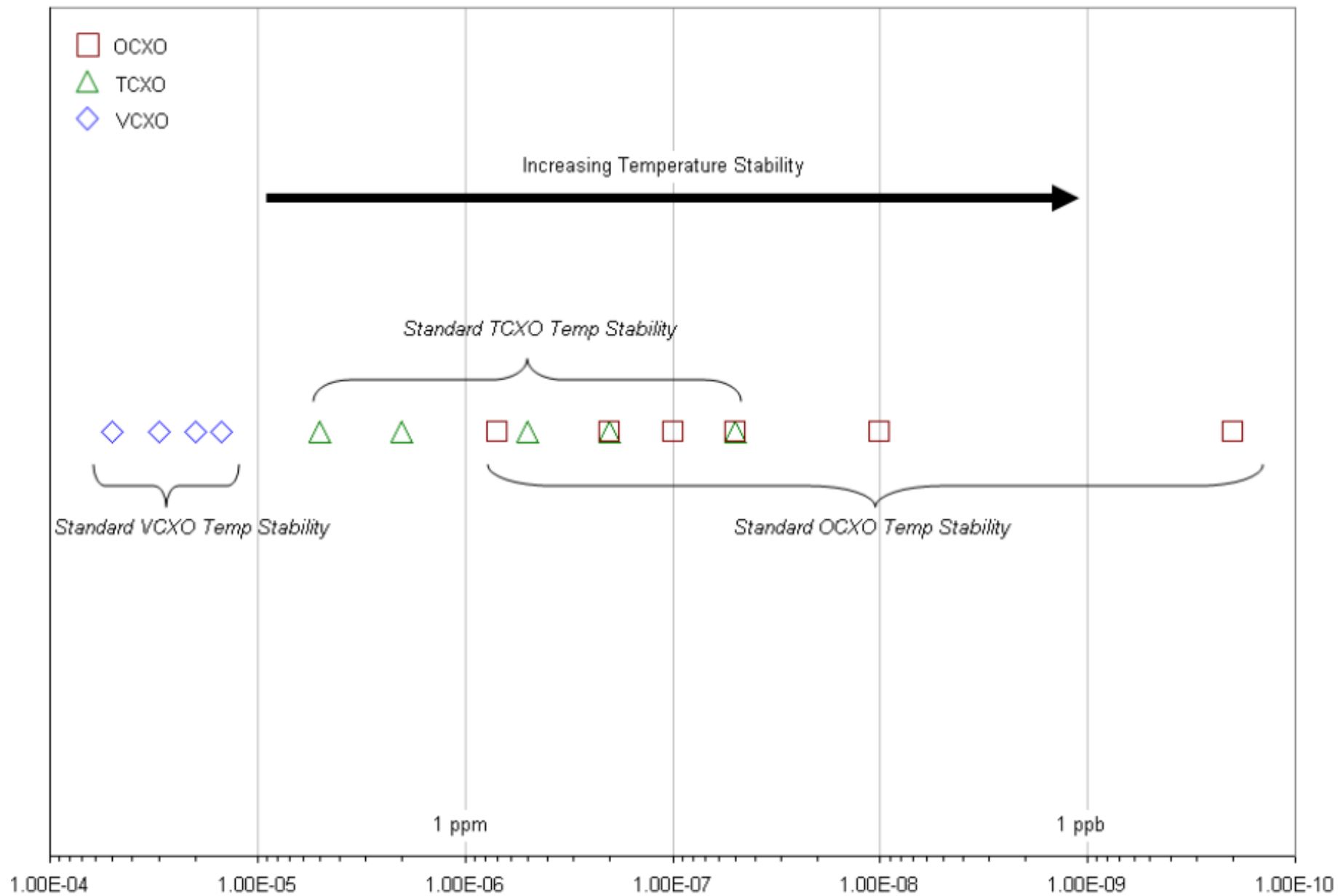

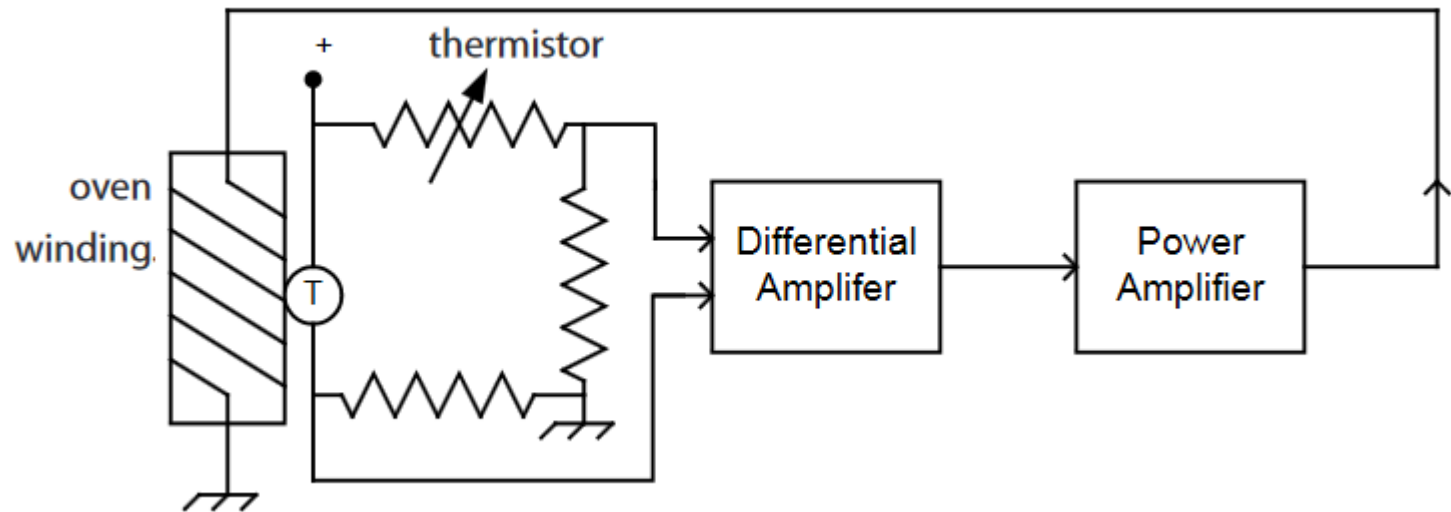Oven Controlled Crystal Oscillator (OCXO)



FREQUENCY STABILITY

TEMPERATURE COEFFICIENT

parts per million (ppm)

.01 % = 100 PPM

.005% = 50 PPM

.001 % = 10 PPM

ppm/°C

$$\Delta f = k (f_o \cdot \Delta T) , \quad k = \text{ppm}/^{\circ}\text{C} , \quad T = \text{temp in } ^{\circ}\text{C}$$

example:

DATA:

nominal frequency = 20 MHz,


k= 32 ppm /°C

$\Delta T = +10 ^{\circ}\text{C}$ (+ = temperature increment)

$$\Delta f = 32 \cdot 20 \cdot 10 = 6400 \text{ Hz}$$

FREQUENCY STABILITY

PUSHING and PULLING

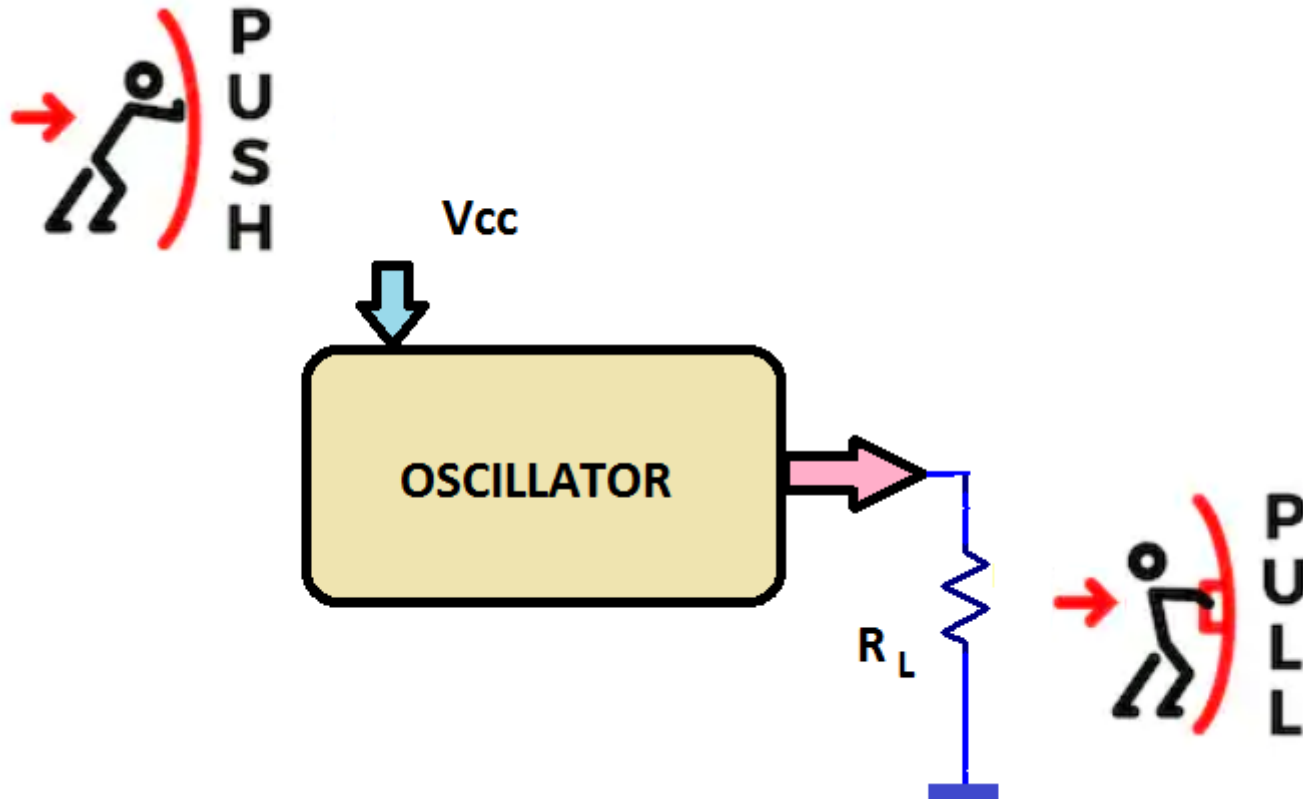

FREQUENCY STABILITY


PUSHING and PULLING

PUSHING: Sensitivity of the output frequency to **SUPPLY VOLTAGE** changes.
Hz/V or Hz/mV. May a positive or negative value.
Specially relevant in mobile equipment, battery operated




PULLING: Sensitivity of the output frequency to the **OUTPUT IMPEDANCE**.
Not often specified in ohms (!). Instead, it more used a parameter related
with the separation between the actual impedance and the ideal one (matching
impedance).

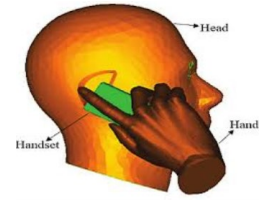“ less than X Hz at **VSWR** = Y”
“no more than X kHz at Y dB **return loss**”






Specially relevant in mobile equipment, specially regarding the antenna impedance
which depends on the mobile terminal environment

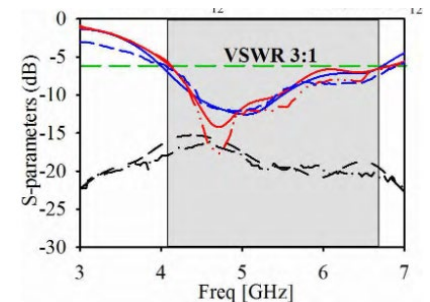(VSWR , return loss... are concepts seen in the parallel course of OESC.)




FREQUENCY STABILITY

PHASE NOISE

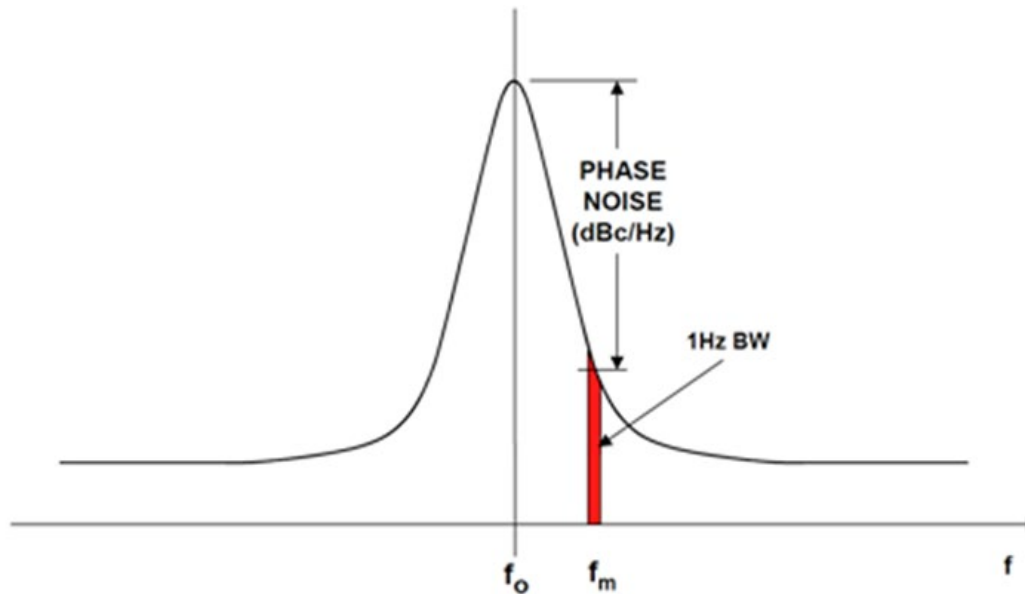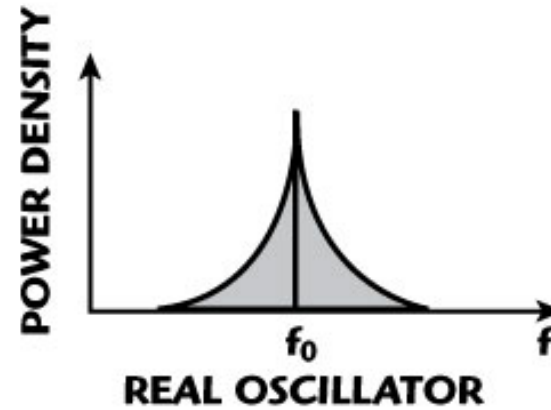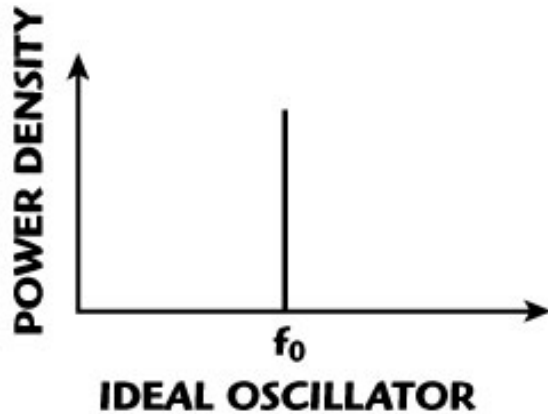

FREQUENCY STABILITY


PHASE NOISE EFFECTS

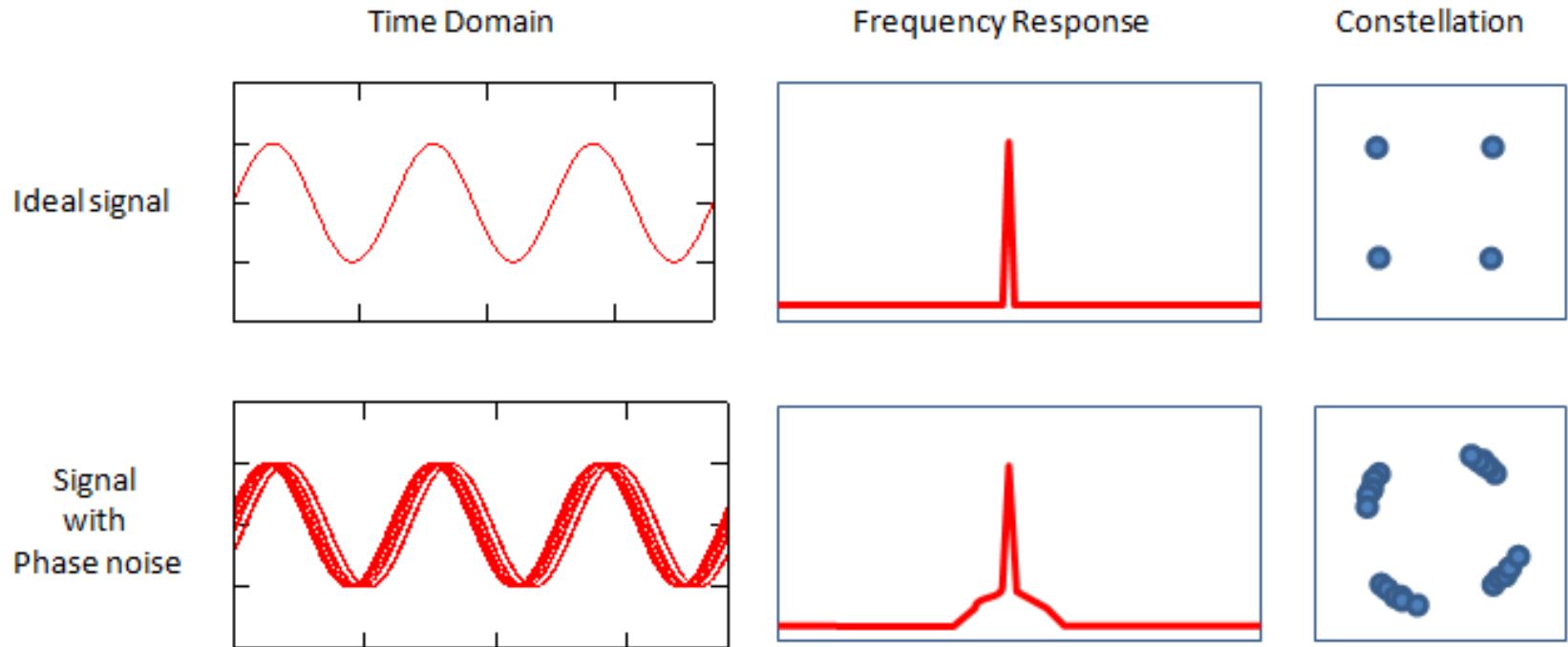


FREQUENCY STABILITY

NOISE EFFECTS

16-QAM and 64-QAM

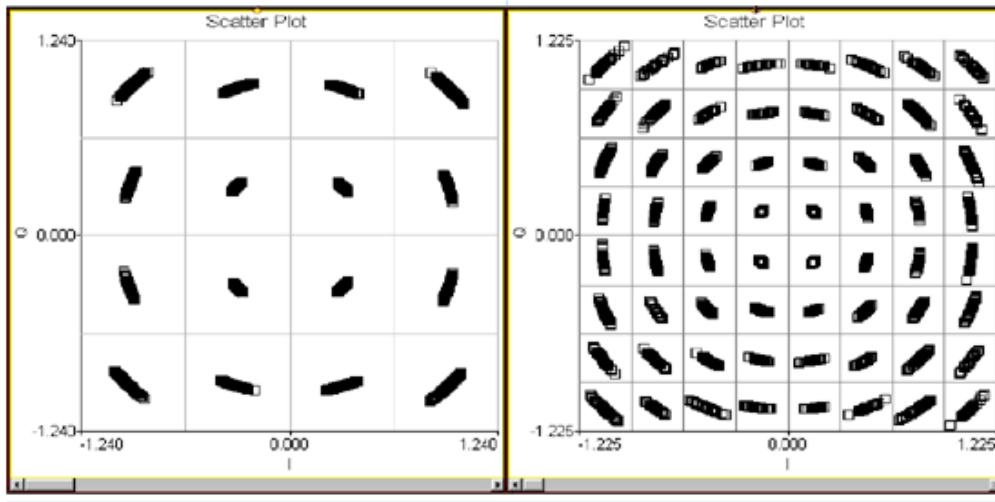


256-QAM

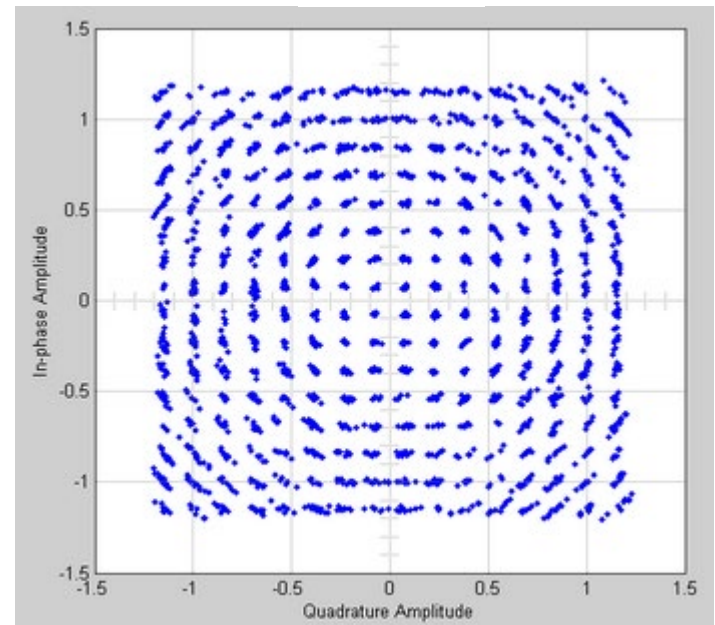

FREQUENCY STABILITY

PHASE NOISE EFFECTS

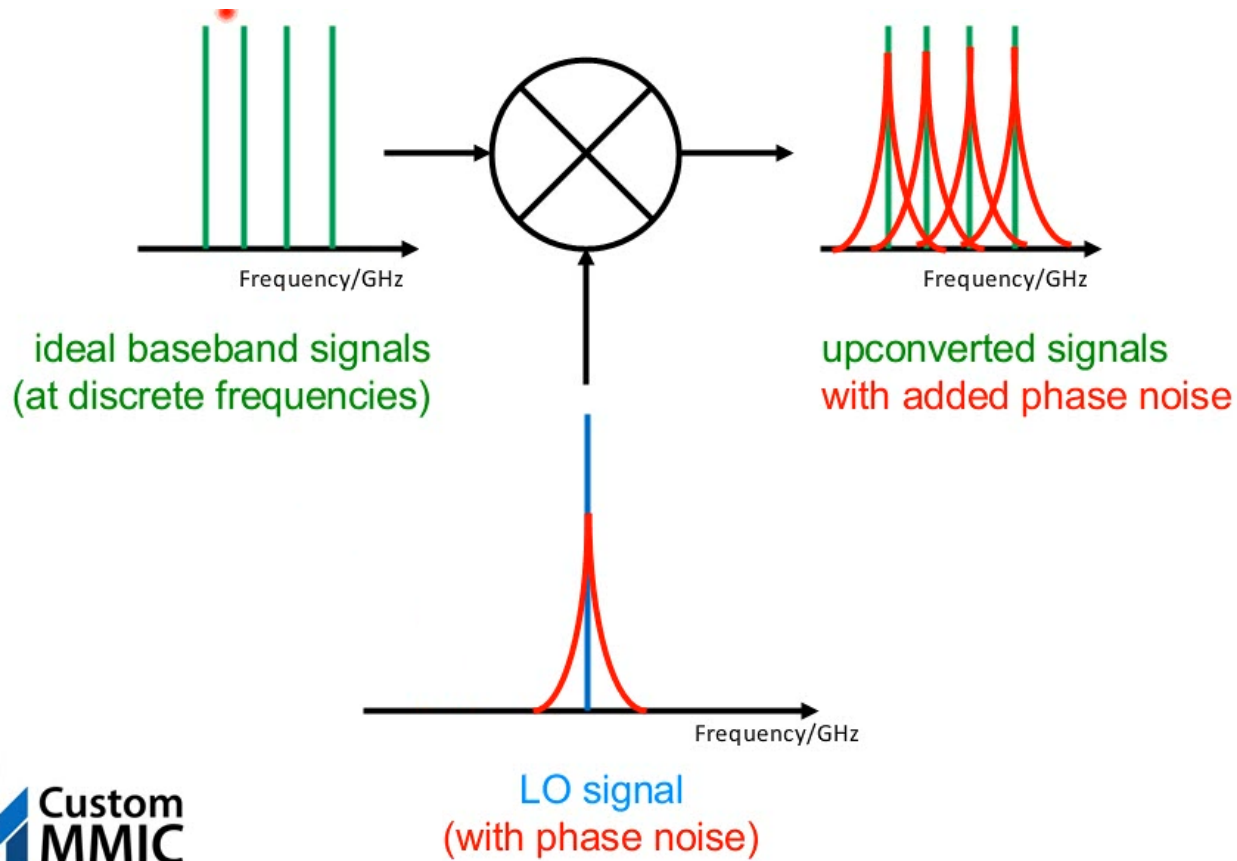

FREQUENCY STABILITY

PHASE NOISE EFFECTS

