July 1966


Brief 66-10292

NASA TECH BRIEF



NASA Tech Briefs are issued to summarize specific innovations derived from the U. S. space program and to encourage their commercial application. Copies are available to the public from the Clearinghouse for Federal Scientific and Technical Information, Springfield, Virginia 22151.

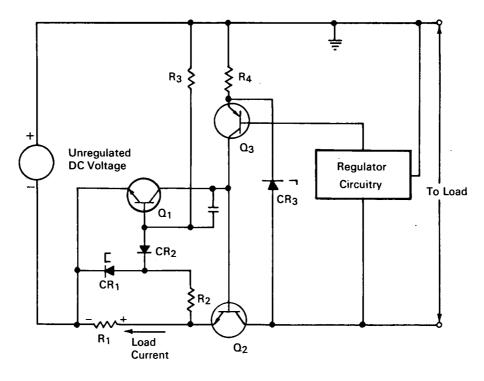Circuit Protects Regulated Power Supply Against Overload Current



The problem:

To protect a low voltage transistorized dc regulator from damage by excessive load currents. In some applications, a single load fault can disable an entire system by disabling the regulators. Current threshold detectors have employed zener diodes and the voltage characteristics of transistor base-emitter junctions but these have not achieved sharp detection and current limiting.

The solution:

A sensing circuit in which a tunnel diode controls a series regulator transistor. When a fault occurs, the faulty circuit is limited to a preset percentage of the current when limiting first occurs.

How it's done:

 R_4 , Q_3 , and CR_3 form the regulator series stage driver and Q_2 is the regulator series element. The overload circuit is composed of R_1 , R_2 , R_3 , CR_1 , CR_2 , and Q_1 , and functions by shunting the base current of Q_2 through Q_1 in case of overload, thereby shutting off Q_2 and limiting the fault current. The volt-ampere characteristics of CR_1 are used to provide the voltage threshold detection. The voltage across R_1 is used to detect the magnitude of the load current.

(continued overleaf)

When the load current is just below the limiting level, current through R₃ plus current through R₂ is just below the threshold point of CR₁. The base-to-emitter voltage of Q₁ is the sum of voltages across CR₁ and CR₂ and the current through R₃ is such that the voltage across CR₂ is about 400 mv. The voltage across CR₁ is at 50 mv and the base-emitter voltage of Q₁ is 450 mv which is not sufficient to turn on Q₁. This is the normal mode of overload curcuit/regulator function.

When the load current causes the peak-point current of CR1 to be exceeded, it causes the base-emitter voltage of Q₁ to turn that transistor on. As a result, current through R₃ now flows into the base of O₁ and the collector current of Q3 flows into Q1 rather than the base of Q2 so that Q2 turns off and limits the current to the regulator, the collector-emitter (saturated) voltage of Q1 being less than the threshold base-emitter voltage of Q₂. The regulator series element being turned off, current through R₁ decreases, allowing current through CR1 to decrease. When the current through CR1 drops below its valley-point current, the overload circuit returns to its original state. If the overload is still present, the cycle is repeated, alternately cutting off Q2 and continuing to limit overload current to the regulator until the fault in the load is corrected. Value of the capacitor controls frequency of the series stage cycle.

Notes:

- Typical changes of the threshold detection current are ±10% over a range from 0° to +70°C. Any change with temperature in the base-emitter voltage threshold of Q₁ is compensated for by a like change in the threshold voltage of CR₂.
- 2. This circuit provides sharp detection of overload currents at very low voltage levels and has limited short circuit currents to less than 10% more than the detector (CR₁) threshold current.
- 3. The circuit shown uses a germanium tunnel diode but will perform satisfactorily with one of silicon.
- 4. Inquiries concerning this innovation may be directed to:

Technology Utilization Officer Goddard Space Flight Center Greenbelt, Maryland 20771 Reference: B66-10292

Patent status:

No patent action is contemplated by NASA.

Source: H. B. Airth of Westinghouse Electric Corporation under contract to Goddard Space Flight Center (GSFC-453)