

and diode CR4 in series. The purpose of the zener diode is to drop the regulator voltage to a value several volts below the regulator output. Diode CR4 prevents power on the logic supply line from flowing into the load during the starting interval. When power is applied, the output of the regulator is zero and the emitter of Q2 is at ground potential. Since the base is then forward biased by CR2, current will flow through Q2 to the logic circuitry. The logic circuitry, now being energized, will sense the lack of regulator voltage output and supply drive power to turn on Q1. The voltage of the output of the regulator will rise. As soon as the regulator output voltage exceeds the sum of CR3, forward drop of CR4, and emitter voltage at Q2, it will start supplying power to the logic circuitry. As the voltage rises, the emitter of Q2 will follow. Since the various voltages have been selected so the normal operating voltage at the logic circuitry and the emitter of Q2 will exceed the base voltage on Q2 as supplied by CR2, Q2 will then be back biased and cut off. The drain on the input power supply, regardless of voltage level, will be just a few milliamperes through CR2. The logic circuit will then be supplied by well-regulated power out of the switching regulator.

Notes:

1. The total power consumed by the logic circuitry is held to a minimum, the circuit is automatically self-starting, and receives the optimum regulated supply power.
2. No further documentation is available.
3. Technical questions may be directed to:
Technology Utilization Officer
Lewis Research Center
21000 Brookpark Road
Cleveland, Ohio 41135
Reference: B69-10128

Patent status:

Inquiries about obtaining rights for the commercial use of this invention may be made to NASA, Code GP, Washington, D. C. 20546.

Source: Gordon Sohl and Eugene H. Schraut
of Electro-Optical Systems, Inc.
under contract to
Lewis Research Center
(LEW-10686)