

September 1970


Brief 70-10414

# NASA TECH BRIEF



NASA Tech Briefs announce new technology derived from the U.S. space program. They are issued to encourage commercial application. Tech Briefs are available on a subscription basis from the Clearinghouse for Federal Scientific and Technical Information, Springfield, Virginia 22151. Requests for individual copies or questions relating to the Tech Brief program may be directed to the Technology Utilization Division, NASA, Code UT, Washington, D.C. 20546.
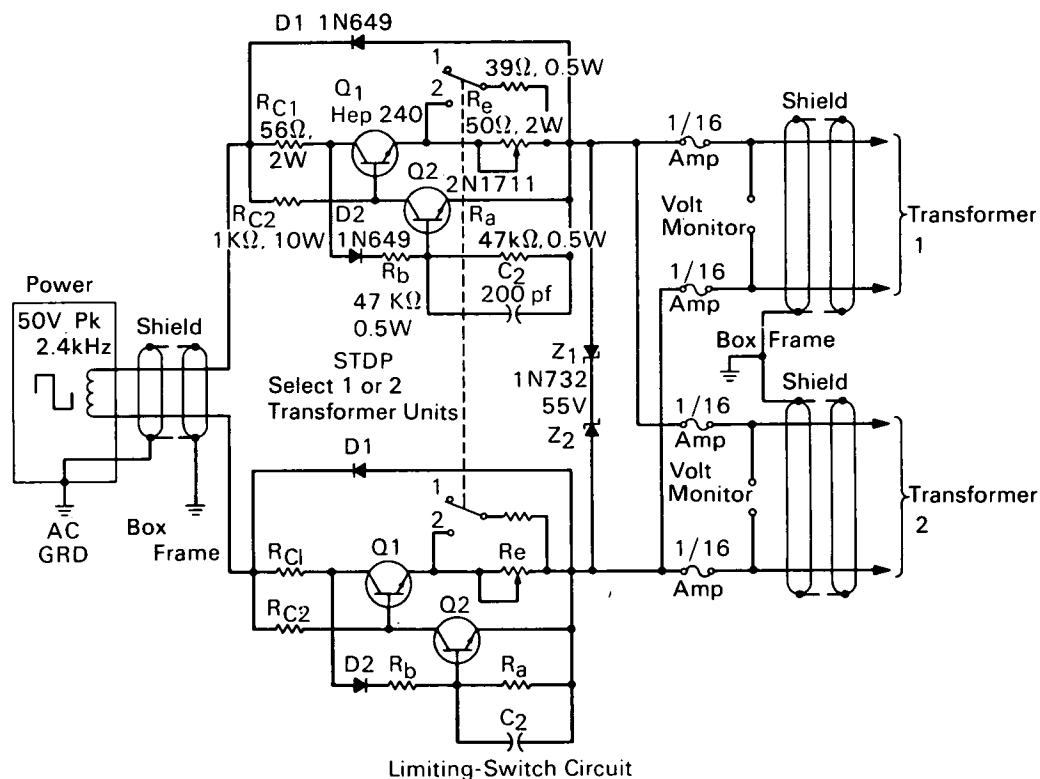
## Transistor Current and Voltage Limiting Switch



Limiting-Switch Circuit

### The problem:

A main power supply, used to power a series of electronic modules undergoing extended life tests, requires an overload circuit to protect the main supply and to limit and control the current drawn by each module in the event of a shortcircuit. The entire sequence must be automated due to the long and unattended nature of the test operation.

### The solution:

A limiting circuit in a balanced configuration that limits current within 1 mA when used with direct

current of either polarity or with pulse or ac power sources from direct current to about 100 kHz.

### How it's done:

For an isolated power supply whose output is a 50-V-peak 2.4-kHz square wave, the circuit (see fig.) consists of two identical stages that alternately perform the limiting operation or bypass the current through diode D1, depending on the polarity of the supply voltage. Resistors  $R_{C1}$  and  $R_{C2}$  are chosen so that, for normal load current,  $Q_1$  is saturated;  $D_2$ ,  $R_b$ , and  $R_a$  form a voltage-divider network that feeds

(continued overleaf)

back part of the voltage across  $Q_1$  and  $R_e$  to the base of  $Q_2$ . When  $Q_1$  is saturated, and with normal load current through  $R_e$ ,  $Q_2$  is biased off. The current limit is controllable within 1 mA by variation of  $R_e$ .

As load current through  $R_e$  increases above the selected safe level, the voltage at the base of  $Q_2$  rises, causing  $Q_2$  to turn on; thus  $Q_1$  is turned off, and regeneration then keeps  $Q_2$  on and  $Q_1$  off. By switching of the high resistance of  $R_{C2}$  in the path of the load current, both load and power supply are protected.

The circuit automatically resets to the on state when the supply voltage is dropped to zero and raised again; capacitor  $C_2$  ensures that  $Q_1$  turns on first when voltage is reapplied. By use of two stages and bypass diodes  $D1$ , this circuit limits current for direct current of either polarity or for a non-dc type of supply.

In this particular case, the load of the transformer's primary is considerably inductive; therefore, zeners  $Z_1$  and  $Z_2$  are used to limit inductive spikes that would occur if the circuit limited. The collector-to-emitter breakdown voltage of  $Q_1$  and power rating of  $R_{C2}$  are chosen so that even with a worst-case power-supply failure, resulting in a supply output of 120 V rms (170-V peak), the transformer is not damaged.

The circuit also protects the power supply and eliminates the chance of fire resulting from direct shorting of the outputs; it is capable of limiting continuously more than 120 V rms supplied to a direct short at the output. The switch's limiting speed for this circuit is about 5  $\mu$ sec; therefore it can be used for supply-voltage frequencies from direct current to about 100 kHz. The frequency range could be increased, if desired, by use of high-frequency transistors if the high collector-to-emitter breakdown voltage were not required.

**Note:**

Requests for further information may be directed to:  
Technology Utilization Officer  
NASA Pasadena Office  
4800 Oak Grove Drive  
Pasadena, California 91103  
Reference: TSP70-10414

**Patent status:**

No patent action is contemplated by NASA.  
Source: E. E. Hilbert of  
Caltech/JPL  
under contract to  
NASA Pasadena Office  
(NPO-11166)