



Introduction to Electromagnetic Compatibility

Second Edition

CLAYTON R. PAUL

*Department of Electrical and Computer Engineering, School of Engineering,
Mercer University, Macon, Georgia and Emeritus Professor of Electrical
Engineering, University of Kentucky, Lexington, Kentucky*

 **WILEY-
INTERSCIENCE**

A JOHN WILEY & SONS, INC. PUBLICATION

Contents

Preface	xvii
1 Introduction to Electromagnetic Compatibility (EMC)	1
1.1 Aspects of EMC	3
1.2 History of EMC	10
1.3 Examples	12
1.4 Electrical Dimensions and Waves	14
1.5 Decibels and Common EMC Units	23
1.5.1 Power Loss in Cables	32
1.5.2 Signal Source Specification	37
Problems	43
References	48
2 EMC Requirements for Electronic Systems	49
2.1 Governmental Requirements	50
2.1.1 Requirements for Commercial Products Marketed in the United States	50
2.1.2 Requirements for Commercial Products Marketed outside the United States	55
2.1.3 Requirements for Military Products Marketed in the United States	60
2.1.4 Measurement of Emissions for Verification of Compliance	62
2.1.4.1 <i>Radiated Emissions</i>	64
2.1.4.2 <i>Conducted Emissions</i>	67
2.1.5 Typical Product Emissions	72
2.1.6 A Simple Example to Illustrate the Difficulty in Meeting the Regulatory Limits	78
	vii

2.2	Additional Product Requirements	79
2.2.1	Radiated Susceptibility (Immunity)	81
2.2.2	Conducted Susceptibility (Immunity)	81
2.2.3	Electrostatic Discharge (ESD)	81
2.2.4	Requirements for Commercial Aircraft	82
2.2.5	Requirements for Commercial Vehicles	82
2.3	Design Constraints for Products	82
2.4	Advantages of EMC Design	84
	Problems	86
	References	89
3	Signal Spectra—the Relationship between the Time Domain and the Frequency Domain	91
3.1	Periodic Signals	91
3.1.1	The Fourier Series Representation of Periodic Signals	94
3.1.2	Response of Linear Systems to Periodic Input Signals	104
3.1.3	Important Computational Techniques	111
3.2	Spectra of Digital Waveforms	118
3.2.1	The Spectrum of Trapezoidal (Clock) Waveforms	118
3.2.2	Spectral Bounds for Trapezoidal Waveforms	122
3.2.2.1	<i>Effect of Rise/Falltime on Spectral Content</i>	123
3.2.2.2	<i>Bandwidth of Digital Waveforms</i>	132
3.2.2.3	<i>Effect of Repetition Rate and Duty Cycle</i>	136
3.2.2.4	<i>Effect of Ringing (Undershoot/Overshoot)</i>	137
3.2.3	Use of Spectral Bounds in Computing Bounds on the Output Spectrum of a Linear System	140
3.3	Spectrum Analyzers	142
3.3.1	Basic Principles	142
3.3.2	Peak versus Quasi-Peak versus Average	146
3.4	Representation of Nonperiodic Waveforms	148
3.4.1	The Fourier Transform	148
3.4.2	Response of Linear Systems to Nonperiodic Inputs	151
3.5	Representation of Random (Data) Signals	151
3.6	Use of SPICE (PSPICE) In Fourier Analysis	155
	Problems	167
	References	175
4	Transmission Lines and Signal Integrity	177
4.1	The Transmission-Line Equations	181
4.2	The Per-Unit-Length Parameters	184
4.2.1	Wire-Type Structures	186

4.2.2	Printed Circuit Board (PCB) Structures	199
4.3	The Time-Domain Solution	204
4.3.1	Graphical Solutions	204
4.3.2	The SPICE Model	218
4.4	High-Speed Digital Interconnects and Signal Integrity	225
4.4.1	Effect of Terminations on the Line Waveforms	230
4.4.1.1	<i>Effect of Capacitive Terminations</i>	233
4.4.1.2	<i>Effect of Inductive Terminations</i>	236
4.4.2	Matching Schemes for Signal Integrity	238
4.4.3	When Does the Line Not Matter, i.e., When is Matching Not Required?	244
4.4.4	Effects of Line Discontinuities	247
4.5	Sinusoidal Excitation of the Line and the Phasor Solution	260
4.5.1	Voltage and Current as Functions of Position	261
4.5.2	Power Flow	269
4.5.3	Inclusion of Losses	270
4.5.4	Effect of Losses on Signal Integrity	273
4.6	Lumped-Circuit Approximate Models	283
	Problems	287
	References	297
5	Nonideal Behavior of Components	299
5.1	Wires	300
5.1.1	Resistance and Internal Inductance of Wires	304
5.1.2	External Inductance and Capacitance of Parallel Wires	308
5.1.3	Lumped Equivalent Circuits of Parallel Wires	309
5.2	Printed Circuit Board (PCB) Lands	312
5.3	Effect of Component Leads	315
5.4	Resistors	317
5.5	Capacitors	325
5.6	Inductors	336
5.7	Ferromagnetic Materials—Saturation and Frequency Response	340
5.8	Ferrite Beads	343
5.9	Common-Mode Chokes	346
5.10	Electromechanical Devices	352
5.10.1	DC Motors	352
5.10.2	Stepper Motors	355
5.10.3	AC Motors	355
5.10.4	Solenoids	356
5.11	Digital Circuit Devices	357
5.12	Effect of Component Variability	358
5.13	Mechanical Switches	359
5.13.1	Arcing at Switch Contacts	360

5.13.2	The Showering Arc	363
5.13.3	Arc Suppression	364
	Problems	369
	References	375
6	Conducted Emissions and Susceptibility	377
6.1	Measurement of Conducted Emissions	378
6.1.1	The Line Impedance Stabilization Network (LISN)	379
6.1.2	Common- and Differential-Mode Currents Again	381
6.2	Power Supply Filters	385
6.2.1	Basic Properties of Filters	385
6.2.2	A Generic Power Supply Filter Topology	388
6.2.3	Effect of Filter Elements on Common- and Differential-Mode Currents	390
6.2.4	Separation of Conducted Emissions into Common- and Differential-Mode Components for Diagnostic Purposes	396
6.3	Power Supplies	401
6.3.1	Linear Power Supplies	405
6.3.2	Switched-Mode Power Supplies (SMPS)	406
6.3.3	Effect of Power Supply Components on Conducted Emissions	409
6.4	Power Supply and Filter Placement	414
6.5	Conducted Susceptibility	416
	Problems	416
	References	419
7	Antennas	421
7.1	Elemental Dipole Antennas	421
7.1.1	The Electric (Hertzian) Dipole	422
7.1.2	The Magnetic Dipole (Loop)	426
7.2	The Half-Wave Dipole and Quarter-Wave Monopole Antennas	429
7.3	Antenna Arrays	440
7.4	Characterization of Antennas	448
7.4.1	Directivity and Gain	448
7.4.2	Effective Aperture	454
7.4.3	Antenna Factor	456
7.4.4	Effects of Balancing and Baluns	460
7.4.5	Impedance Matching and the Use of Pads	463
7.5	The Friis Transmission Equation	466
7.6	Effects of Reflections	470
7.6.1	The Method of Images	470

7.6.2	Normal Incidence of Uniform Plane Waves on Plane, Material Boundaries	470
7.6.3	Multipath Effects	479
7.7	Broadband Measurement Antennas	486
7.7.1	The Biconical Antenna	487
7.7.2	The Log-Periodic Antenna	490
	Problems	494
	References	501
8	Radiated Emissions and Susceptibility	503
8.1	Simple Emission Models for Wires and PCB Lands	504
8.1.1	Differential-Mode versus Common-Mode Currents	504
8.1.2	Differential-Mode Current Emission Model	509
8.1.3	Common-Mode Current Emission Model	514
8.1.4	Current Probes	518
8.1.5	Experimental Results	523
8.2	Simple Susceptibility Models for Wires and PCB Lands	533
8.2.1	Experimental Results	544
8.2.2	Shielded Cables and Surface Transfer Impedance	546
	Problems	550
	References	556
9	Crosstalk	559
9.1	Three-Conductor Transmission Lines and Crosstalk	560
9.2	The Transmission-Line Equations for Lossless Lines	564
9.3	The Per-Unit-Length Parameters	567
9.3.1	Homogeneous versus Inhomogeneous Media	568
9.3.2	Wide-Separation Approximations for Wires	570
9.3.3	Numerical Methods for Other Structures	580
	9.3.3.1 <i>Wires with Dielectric Insulations</i> <i>(Ribbon Cables)</i>	586
	9.3.3.2 <i>Rectangular Cross-Section Conductors</i> <i>(PCB Lands)</i>	590
9.4	The Inductive–Capacitive Coupling Approximate Model	595
9.4.1	Frequency-Domain Inductive–Capacitive Coupling Model	599
	9.4.1.1 <i>Inclusion of Losses: Common-Impedance</i> <i>Coupling</i>	601
	9.4.1.2 <i>Experimental Results</i>	604
9.4.2	Time-Domain Inductive–Capacitive Coupling Model	612
	9.4.2.1 <i>Inclusion of Losses: Common-Impedance Coupling</i>	616
	9.4.2.2 <i>Experimental Results</i>	617

9.5	Lumped-Circuit Approximate Models	624
9.6	An Exact SPICE (PSPICE) Model for Lossless, Coupled Lines	624
9.6.1	Computed versus Experimental Results for Wires	633
9.6.2	Computed versus Experimental Results for PCBs	640
9.7	Shielded Wires	647
9.7.1	Per-Unit-Length Parameters	648
9.7.2	Inductive and Capacitive Coupling	651
9.7.3	Effect of Shield Grounding	658
9.7.4	Effect of Pigtailed	667
9.7.5	Effects of Multiple Shields	669
9.7.6	MTL Model Predictions	675
9.8	Twisted Wires	677
9.8.1	Per-Unit-Length Parameters	681
9.8.2	Inductive and Capacitive Coupling	685
9.8.3	Effects of Twist	689
9.8.4	Effects of Balancing	698
	Problems	701
	References	710
10	Shielding	713
10.1	Shielding Effectiveness	718
10.2	Shielding Effectiveness: Far-Field Sources	721
10.2.1	Exact Solution	721
10.2.2	Approximate Solution	725
	10.2.2.1 Reflection Loss	725
	10.2.2.2 Absorption Loss	728
	10.2.2.3 Multiple-Reflection Loss	729
	10.2.2.4 Total Loss	731
10.3	Shielding Effectiveness: Near-Field Sources	735
10.3.1	Near Field versus Far Field	736
10.3.2	Electric Sources	740
10.3.3	Magnetic Sources	740
10.4	Low-Frequency, Magnetic Field Shielding	742
10.5	Effect of Apertures	745
	Problems	750
	References	751
11	System Design for EMC	753
11.1	Changing the Way We Think about Electrical Phenomena	758
11.1.1	Nonideal Behavior of Components and the Hidden Schematic	758
11.1.2	“Electrons Do Not Read Schematics”	763

11.1.3	What Do We Mean by the Term “Shielding”?	766
11.2	What Do We Mean by the Term “Ground”?	768
11.2.1	Safety Ground	771
11.2.2	Signal Ground	774
11.2.3	Ground Bounce and Partial Inductance	775
11.2.3.1	<i>Partial Inductance of Wires</i>	781
11.2.3.2	<i>Partial Inductance of PCB Lands</i>	786
11.2.4	Currents Return to Their Source on the Paths of Lowest Impedance	787
11.2.5	Utilizing Mutual Inductance and Image Planes to Force Currents to Return on a Desired Path	793
11.2.6	Single-Point Grounding, Multipoint Grounding, and Hybrid Grounding	796
11.2.7	Ground Loops and Subsystem Decoupling	802
11.3	Printed Circuit Board (PCB) Design	805
11.3.1	Component Selection	805
11.3.2	Component Speed and Placement	806
11.3.3	Cable I/O Placement and Filtering	808
11.3.4	The Important Ground Grid	810
11.3.5	Power Distribution and Decoupling Capacitors	812
11.3.6	Reduction of Loop Areas	822
11.3.7	Mixed-Signal PCB Partitioning	823
11.4	System Configuration and Design	827
11.4.1	System Enclosures	827
11.4.2	Power Line Filter Placement	828
11.4.3	Interconnection and Number of Printed Circuit Boards	829
11.4.4	Internal Cable Routing and Connector Placement	831
11.4.5	PCB and Subsystem Placement	832
11.4.6	PCB and Subsystem Decoupling	832
11.4.7	Motor Noise Suppression	832
11.4.8	Electrostatic Discharge (ESD)	834
11.5	Diagnostic Tools	847
11.5.1	The Concept of Dominant Effect in the Diagnosis of EMC Problems	850
	Problem	856
	References	857

Appendix A	The Phasor Solution Method	859
A.1	Solving Differential Equations for Their Sinusoidal, Steady-State Solution	859

	A.2 Solving Electric Circuits for Their Sinusoidal, Steady-State Response	863
Problems		867
References		869
Appendix B	The Electromagnetic Field Equations and Waves	871
B.1	Vector Analysis	872
B.2	Maxwell's Equations	881
	B.2.1 Faraday's Law	881
	B.2.2 Ampere's Law	892
	B.2.3 Gauss' Laws	898
	B.2.4 Conservation of Charge	900
	B.2.5 Constitutive Parameters of the Medium	900
B.3	Boundary Conditions	902
B.4	Sinusoidal Steady State	907
B.5	Power Flow	909
B.6	Uniform Plane Waves	909
	B.6.1 Lossless Media	912
	B.6.2 Lossy Media	918
	B.6.3 Power Flow	922
	B.6.4 Conductors versus Dielectrics	923
	B.6.5 Skin Depth	925
B.7	Static (DC) Electromagnetic Field Relations— a Special Case	927
	B.7.1 Maxwell's Equations for Static (DC) Fields	927
	<i>B.7.1.1 Range of Applicability for Low-Frequency Fields</i>	928
	B.7.2 Two-Dimensional Fields and Laplace's Equation	928
Problems		930
References		939
Appendix C	Computer Codes for Calculating the Per-Unit-Length (PUL) Parameters and Crosstalk of Multiconductor Transmission Lines	941
C.1	WIDSEPF.FOR for Computing the PUL Parameter Matrices of Widely Spaced Wires	942
C.2	RIBBON.FOR for Computing the PUL Parameter Matrices of Ribbon Cables	947
C.3	PCB.FOR for Computing the PUL Parameter Matrices of Printed Circuit Boards	949

C.4	MSTRP.FOR for Computing the PUL Parameter Matrices of Coupled Microstrip Lines	951
C.5	STRPLINE.FOR for Computing the PUL Parameter Matrices of Coupled Striplines	952
C.6	SPICEMTL.FOR for Computing a SPICE (PSPICE) Subcircuit Model of a Lossless, Multiconductor Transmission Line	954
C.7	SPICELPI.FOR For Computing a SPICE (PSPICE) Subcircuit of a Lumped-Pi Model of a Lossless, Multiconductor Transmission Line	956
Appendix D	A SPICE (PSPICE) Tutorial	959
D.1	Creating the SPICE or PSPICE Program	960
D.2	Circuit Description	961
D.3	Execution Statements	966
D.4	Output Statements	968
D.5	Examples	970
References		974
Index		975