

Semiconductor Detector Systems

Helmuth Spieler

Physics Division, Lawrence Berkeley National Laboratory

OXFORD
UNIVERSITY PRESS

CONTENTS

1	Detector systems overview	1
1.1	Sensor	2
1.2	Preamplifier	3
1.3	Pulse shaper	3
1.4	Digitizer	5
1.5	Electro-mechanical integration	6
1.6	Sensor structures I	8
1.6.1	Basic sensor	8
1.6.2	Position sensing	9
1.6.3	Pixel devices	11
1.7	Sensor physics	12
1.7.1	Signal charge	12
1.7.2	Sensor volume	13
1.7.3	Charge collection	16
1.7.4	Energy resolution	19
1.7.5	Position resolution	19
1.8	Sensor structures II – monolithic pixel devices	24
1.8.1	Charge coupled devices	24
1.8.2	Silicon drift chambers	25
1.8.3	Monolithic active pixel sensors	26
1.9	Electronics	29
1.10	Detection limits and resolution	29
1.10.1	Electronic noise	31
1.10.2	Amplitude measurements	33
1.10.3	Timing measurements	35
1.11	Subsystems	36
1.11.1	Circuit integration and bussing	36
1.11.2	Detector modules, services, and supports	38
1.11.3	Data acquisition	40
1.12	Further reading	40
	References	40
2	Signal formation and acquisition	43
2.1	The signal	43
2.2	Detector sensitivity	48
2.2.1	Low energy quanta ($E \approx E_g$)	48
2.2.2	High energy quanta ($E \gg E_g$)	51
2.2.3	Fluctuations in signal charge – the Fano factor	52
2.3	Signal formation	55
2.3.1	Formation of a high-field region	55

2.3.2	Doping	56
2.3.3	The <i>pn</i> -junction	59
2.3.4	The reverse-biased diode	61
2.3.5	Strip and pixel detectors	66
2.4	Charge collection	67
2.5	Time dependence of the signal current	71
2.5.1	Induced charge – Ramo’s theorem	73
2.5.2	Parallel plate geometry with uniform field	75
2.5.3	Double-sided strip detector	78
2.6	Charge collection in the presence of trapping	82
2.7	Semiconductor detector materials	83
2.8	Photodiodes	86
2.9	Signal acquisition	91
2.9.1	Voltage-sensitive amplifier	91
2.9.2	Current-sensitive amplifier	91
2.9.3	Voltage and current mode with capacitive sources	92
2.9.4	Feedback amplifiers – the “charge-sensitive amplifier”	93
2.9.5	Realistic charge-sensitive amplifiers	95
2.9.6	Input impedance of a charge-sensitive amplifier	100
	References	102
3	Electronic noise	105
3.1	Electronic noise and resolution	105
3.2	Electronic noise	107
3.3	Some general properties of noise	107
3.3.1	Thermal (Johnson) noise	109
3.3.2	Shot noise	109
3.3.3	Low frequency (“ $1/f$ ”) noise	109
3.4	Derivation of spectral densities	110
3.4.1	Spectral density of thermal noise	110
3.4.2	Spectral density of shot noise	111
3.4.3	Spectral density of low-frequency noise	113
3.5	“Noiseless” resistances	114
3.5.1	Dynamic resistances	114
3.5.2	Active resistances	114
3.5.3	Radiation resistance of an antenna	114
3.6	Correlated noise	115
3.7	Signal equivalent noise measures	116
3.7.1	Noise equivalent power	116
3.7.2	Equivalent noise charge	116
3.8	Noise in Amplifiers	117
3.8.1	Amplifier noise model	117
3.8.2	Noise bandwidth <i>vs.</i> signal bandwidth	120
3.9	Amplifier noise matching	121

CONTENTS

xi

3.9.1 Resistive sources	121
3.9.2 Noise matching with a transformer	122
3.10 Capacitive sources	123
3.10.1 Noise <i>vs.</i> capacitance in a charge-sensitive amplifier	123
3.10.2 S/N <i>vs.</i> input time constant	125
3.11 Complex sensors	127
3.11.1 Cross-coupled noise	129
3.11.2 Backside readout	131
3.12 Quantum noise limits in amplifiers	132
References	133
4 Signal processing	134
4.1 Simple pulse shapers	134
4.1.1 Effect of relative time constants	135
4.2 Evaluation of equivalent noise charge	138
4.2.1 Experiment	139
4.2.2 Numerical simulation (<i>e.g.</i> SPICE)	141
4.2.3 Analytical simulation	141
4.3 Noise analysis of a detector and front-end amplifier	142
4.3.1 Detector bias current	143
4.3.2 Parallel resistance	144
4.3.3 Series resistance	145
4.3.4 Amplifier input noise	145
4.3.5 Cumulative input noise voltage	145
4.3.6 Equivalent noise charge	146
4.4 Examples	148
4.4.1 Photodiode readout	148
4.4.2 High-rate x-ray spectroscopy	151
4.5 Noise analysis in the time domain	153
4.5.1 Principles of noise analysis in the time domain	154
4.5.2 The weighting function	156
4.5.3 Time-variant shapers	158
4.5.4 Noise analysis of a correlated-double sample pulse shaper	160
4.6 Detector noise summary	166
4.7 Threshold discriminator systems	169
4.7.1 Noise rate	171
4.7.2 Noise occupancy	173
4.7.3 Measurement of noise in a threshold discriminator system	174
4.8 Some other aspects of pulse shaping	175
4.8.1 Baseline restoration	175
4.8.2 Tail (pole-zero) cancellation	177
4.8.3 Bipolar <i>vs.</i> unipolar shaping	178
4.9 Timing measurements	179
4.9.1 Pulse shaping in timing systems	180

4.9.2	Choice of rise time in a timing system	181
4.9.3	Time walk	182
4.9.4	Lowest practical threshold in leading edge triggering	183
4.9.5	Zero-crossing timing	184
4.9.6	Constant fraction timing	185
4.9.7	Fast timing – some results	187
	References	189
5	Elements of digital electronics and signal processing	191
5.1	Digital circuit elements	191
5.1.1	Logic elements	191
5.1.2	Propagation delays and power dissipation	194
5.1.3	Logic arrays	195
5.2	Digitization of pulse height and time	196
5.2.1	ADC parameters	197
5.2.2	Analog-to-digital conversion techniques	203
5.3	Time-to-digital converters (TDCs)	209
5.3.1	Counter	209
5.3.2	Analog ramp	209
5.3.3	Digitizers with clock interpolation	209
5.4	Digital signal processing	210
	References	216
6	Transistors and amplifiers	217
6.1	Bipolar transistors	217
6.1.1	Bipolar transistors in amplifiers	222
6.2	Field effect transistors	229
6.2.1	Junction field effect transistors	230
6.2.2	Metal-oxide-semiconductor field effect transistors	236
6.2.3	MOSFET types	241
6.2.4	MOS Transistors in Amplifiers	242
6.3	Noise in transistors	243
6.3.1	Noise in field effect transistors	243
6.3.2	Low-frequency excess noise (“ $1/f$ noise”)	248
6.3.3	Noise in bipolar transistors	248
6.3.4	Comparison between bipolar and field effect transistors	251
6.3.5	Noise optimization – capacitive matching revisited	252
6.4	Composite amplifiers	256
6.5	Overall noise of a detector module	265
6.6	Optimization for low power	266
6.6.1	Optimum operating current	267
6.6.2	Technology improvements	271
6.7	Power dissipation of an active pixel array <i>vs.</i> strip readout	274
	References	275

7	Radiation effects	277
7.1	Radiation damage mechanisms	278
7.1.1	Displacement damage	279
7.1.2	Ionization damage	282
7.2	Radiation damage in diodes	283
7.2.1	Contributions to N_{eff}	286
7.2.2	Trapping	289
7.2.3	Ionization effects	292
7.3	Radiation damage in transistors and integrated circuits	292
7.3.1	Bipolar transistors	292
7.3.2	Junction field effect transistors (JFETs)	295
7.3.3	Metal-oxide-silicon field effect transistors (MOSFETs)	296
7.3.4	Radiation effects in integrated circuit structures	302
7.4	Dosimetry	303
7.5	Mitigation techniques	304
7.5.1	Detectors	304
7.5.2	Electronics	306
7.5.3	Summary	309
	References	309
8	Detector systems	315
8.1	Conflicts and compromises	315
8.2	Design considerations	316
8.2.1	Detector geometry	316
8.2.2	Efficiency	316
8.2.3	Event rate	316
8.2.4	Readout	317
8.2.5	Support structures, cooling, and cabling	317
8.2.6	Cost	317
8.3	Segmentation	318
8.4	Tracking and vertex detectors at e^+e^- colliders	319
8.4.1	Layout and detector geometry	319
8.4.2	Electronics	323
8.4.3	“Common mode noise”	326
8.4.4	Noise limits in long strip detectors	327
8.4.5	CCD detectors at e^+e^- colliders	330
8.5	Vertex and tracking detectors at hadron colliders	337
8.5.1	CDF and DØ	337
8.6	Silicon trackers at the Large Hadron Collider	342
8.6.1	Coping with high rates	343
8.6.2	Radiation damage	344
8.6.3	Layout	345
8.6.4	Readout electronics	348
8.6.5	Detector modules	353

8.6.6	Pixel detectors	357
8.6.7	ATLAS pixel detector	357
8.7	Monolithic active pixel devices	363
8.7.1	CMOS imagers	363
8.7.2	DEPFET pixel detectors	364
8.8	Astronomical imaging	366
8.9	Emerging applications	367
8.9.1	Space applications	367
8.9.2	X-ray imaging and spectroscopy	369
8.10	Design, assembly and test	372
8.10.1	Design	372
8.10.2	Assembly	374
8.10.3	Testing	375
8.11	Summary	377
	References	378
9	Why things don't work	386
9.1	Reflections on transmission lines	386
9.2	Common pickup mechanisms	389
9.2.1	Noisy detector bias supplies	389
9.2.2	Light pickup	389
9.2.3	Microphonics	390
9.2.4	RF pickup	391
9.3	Pickup reduction techniques	392
9.3.1	Shielding	392
9.3.2	“Field line pinning”	394
9.3.3	“Self-shielding” structures	395
9.3.4	Inductive coupling	396
9.3.5	“Self-shielding” cables	397
9.3.6	Shielding summary	397
9.4	Shared current paths – grounding and the power of myth	398
9.4.1	Shared current paths (“ground loops”)	398
9.4.2	Remedial techniques	400
9.4.3	Potential distribution on ground planes	403
9.4.4	Connections in multi-stage circuits	405
9.5	Breaking parasitic current paths	405
9.5.1	Isolate sensitive loops	406
9.5.2	Differential signal transmission	406
9.5.3	Blocking Common Mode Currents	408
9.5.4	Isolating parasitic ground connections by series resistors	409
9.5.5	Directing the current flow away from sensitive nodes	410
9.5.6	The folded cascode	412
9.6	Capacitors	414
9.7	System considerations	415

9.7.1	Choice of shaper	415
9.7.2	Local referencing	416
A	Semiconductor device technology	418
A.1	Bulk material	418
A.2	Introduction of dopants	419
A.3	Deposition	420
A.4	Patterning	421
A.5	Surface passivation	422
A.6	Detector fabrication	422
A.7	Detector process flow	423
A.8	Strip detector structures	426
A.9	CMOS devices	428
	References	429
B	Phasors and complex algebra in electrical circuits	432
C	Equivalent circuits	434
D	Feedback amplifiers	438
D.1	Gain of a feedback amplifier	438
D.2	Linearity	439
D.3	Bandwidth	439
D.4	Series and shunt feedback	440
D.5	Input and output impedance	440
D.5.1	Series feedback	441
D.5.2	Shunt feedback	441
D.5.3	Output impedance	442
D.6	Loop gain	443
D.7	Stability	444
	References	446
E	The diode equation	447
E.1	Carrier concentrations in pure semiconductors	447
E.2	Carrier concentrations in doped crystals	450
E.3	<i>pn</i> -junctions	451
E.4	The forward-biased <i>pn</i> -junction	453
	References	458
F	Electrical effects of impurities and defects	459
F.1	Emission and capture processes	459
F.1.1	Electron capture	460
F.1.2	Electron emission	460
F.1.3	Hole capture and emission	460
F.1.4	Emission probabilities	461
F.2	Recombination	462
F.2.1	Band-to-band recombination	462

F.2.2	Recombination via intermediate states	463
F.3	Carrier generation	465
F.3.1	Generation in the depletion region	465
F.3.2	Generation in the neutral region	466
F.4	The origin of recombination and generation centers	467
F.5	The diode equation revisited	468
F.5.1	Reverse Current	468
F.5.2	Forward current	470
F.5.3	Comments	470
	References	471
G	Bipolar transistor equations	472
	References	477
	Index	478