

Total Dose Effects on Single Event Transients in Digital CMOS and Linear Bipolar Circuits

S. Buchner, *MEI/NASA-GSFC*

D. McMorrow, *NRL*

M. Sibley, P. Eaton, D. Mavis, *Micro-RDC*

L. Dusseau, N. J-H. Roche, M. Bernard, *Univ. of Montpellier*



Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009


Introduction

- Exposure of ICs to ionizing radiation **changes electrical parameters**.
- TID effect observed in both CMOS and bipolar circuits:
 - In bipolar circuits, transistors exhibit gain degradation
 - In CMOS circuits, transistors exhibit threshold voltage shifts
- Changes in electrical parameters can cause **changes in SEU/SET rates**. Depending on effect, rates may increase or decrease.
- Therefore, measures taken for SEU/SET mitigation might work at the beginning of a mission but not at the end following TID exposure.

Introduction

TID concerns arise during proton testing of circuits with small SEU cross-sections


- At 60 MeV, a fluence of 7×10^{11} p/cm² gives a TID of 100 krad(Si).
- For 10% statistics require 100 upsets or 3×10^{11} p/cm².
- Assume 50% charge yield in presence of electric field.
- Equivalent TID(e⁻) = 20 krad.
- **If part has a hardness of 50 krad, can measure 2 points before electrical parameters exceed manufacturer's specifications and part must be changed.**
- Schwank et al have investigated proton-induced TID effects in SRAMs (2004)

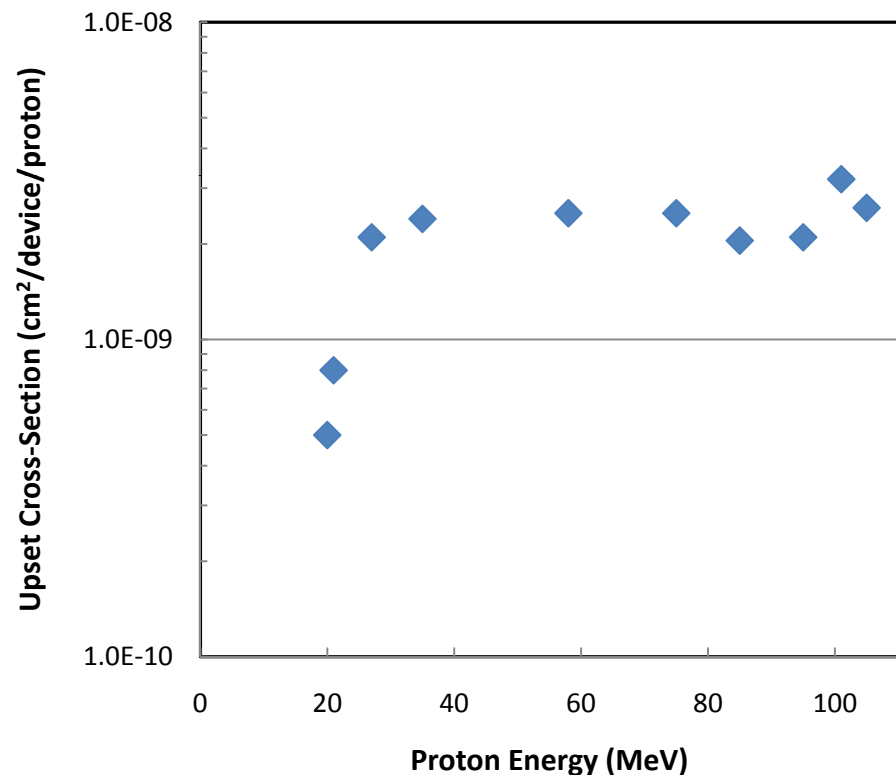


N.J.Buchanan et al. MAPLD 2000

Introduction – Bipolar Transistors

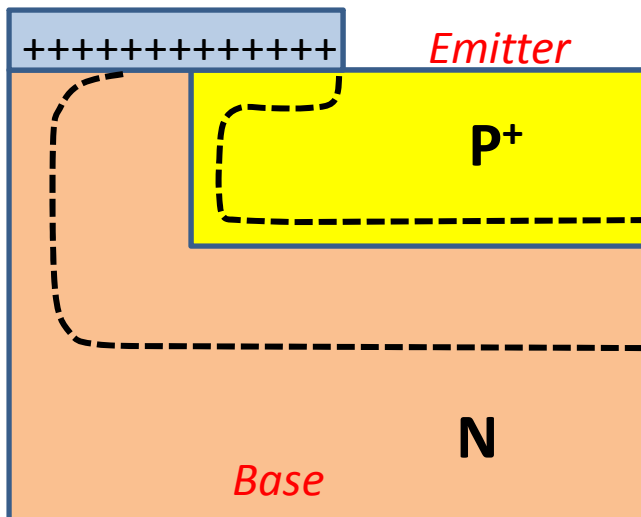TID causes charge buildup that distorts emitter/base junction field and degrades gain.



Schmidt et al, IEEE TNS 1996


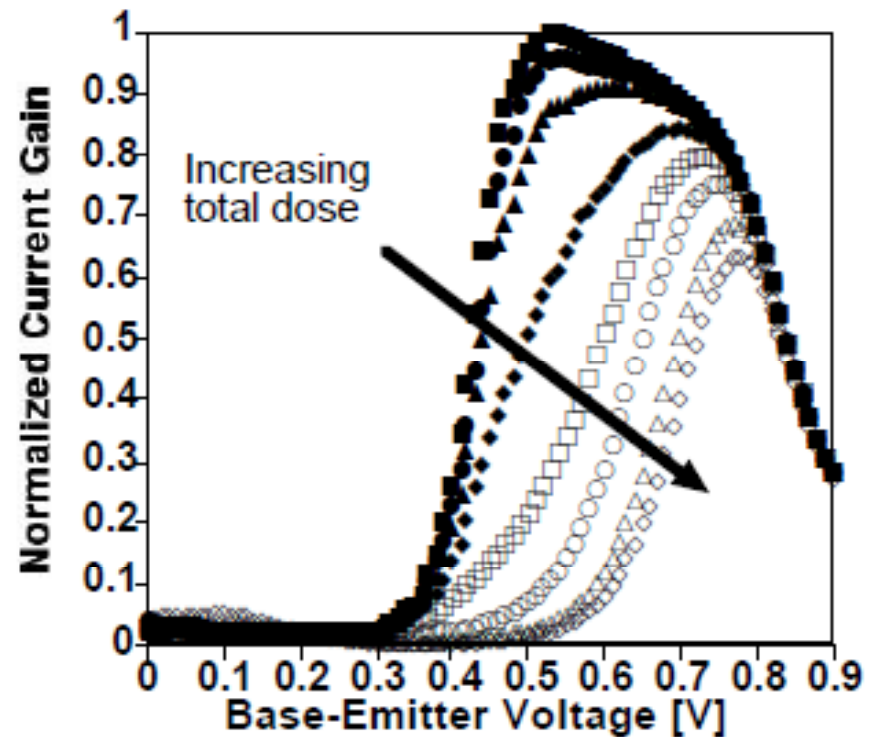


Schrimpf, NSREC 2001 Short Course

Introduction – MOS transistors

TID causes charge buildup that shifts threshold Voltage and increases leakage currents.

N-channel MOSFET

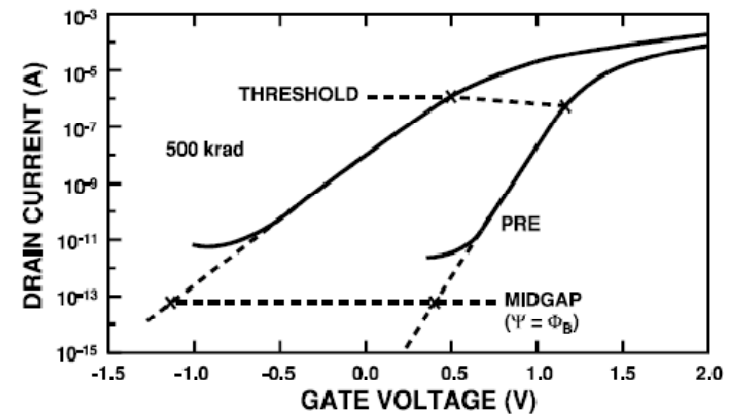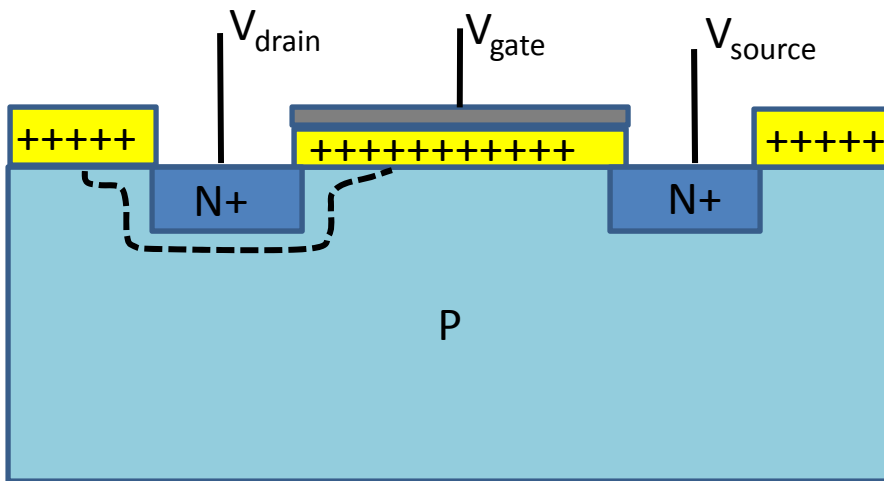

J. Schwank, NSREC Short Course 2002



LINEAR BIPOLAR CIRCUIT

VOLTAGE COMPARATOR – LM139

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Voltage Comparator – LM139

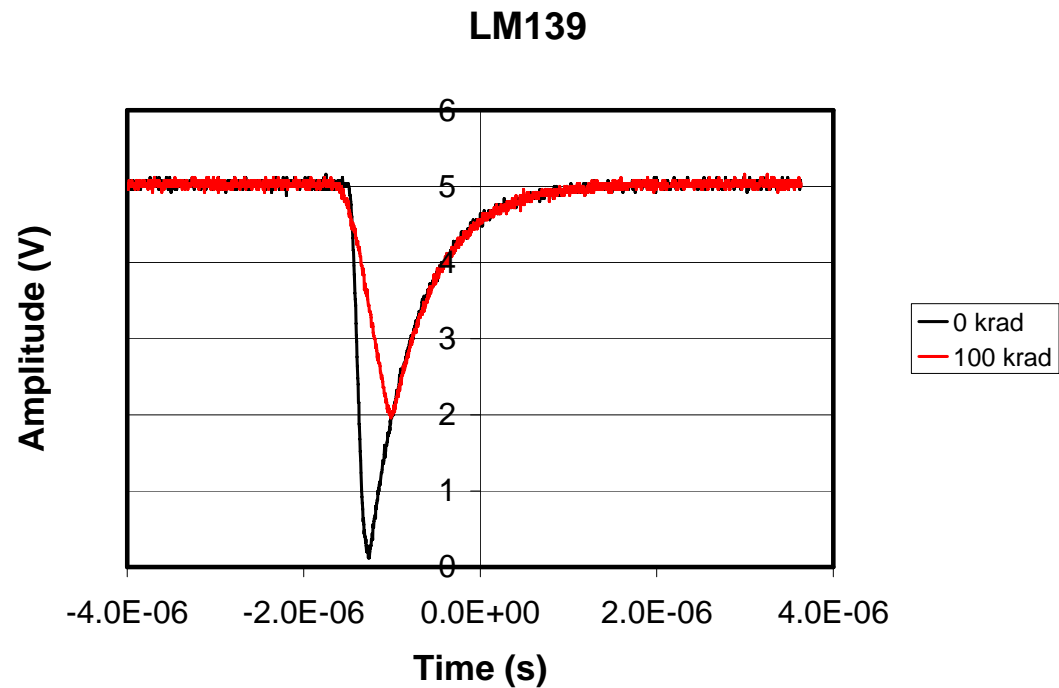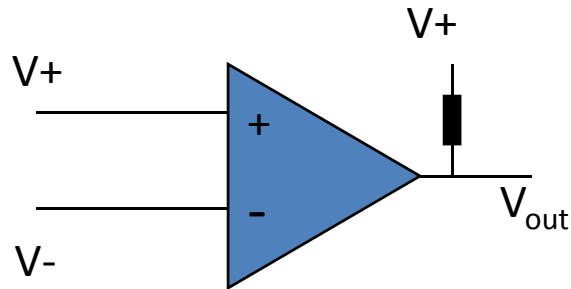- **LM139** - SETs become smaller with TID





LINEAR BIPOLAR CIRCUIT

Operational Amplifier – LM124



Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Operational Amplifier – LM124

- Used focused pulsed laser to inject charge into Q9 and R.

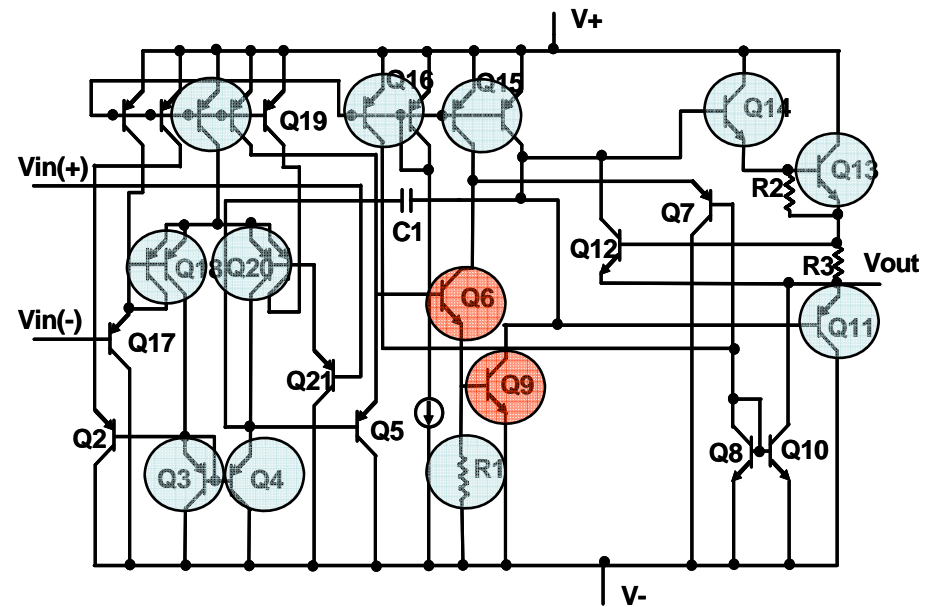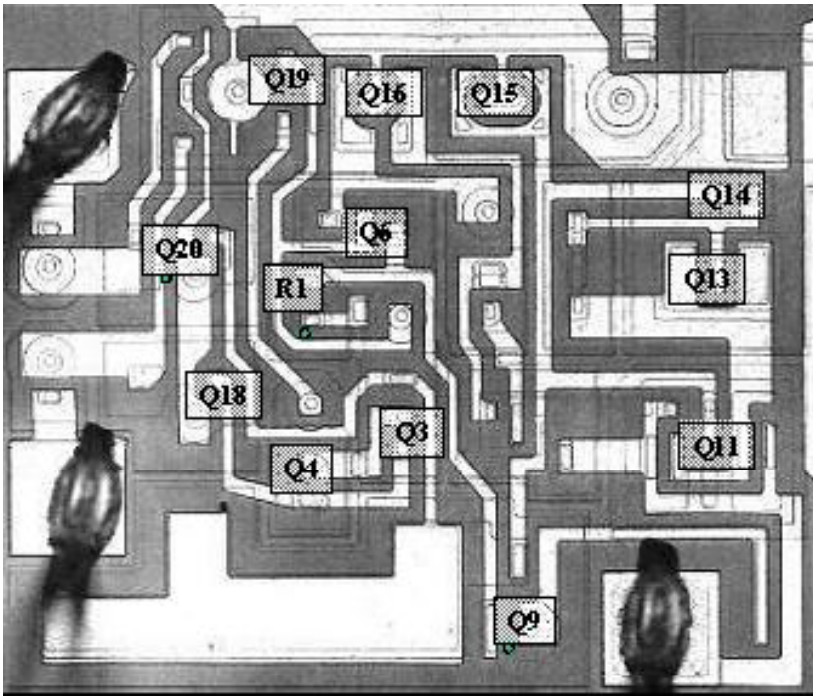



LM124 – Q9 VF

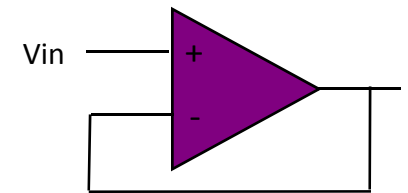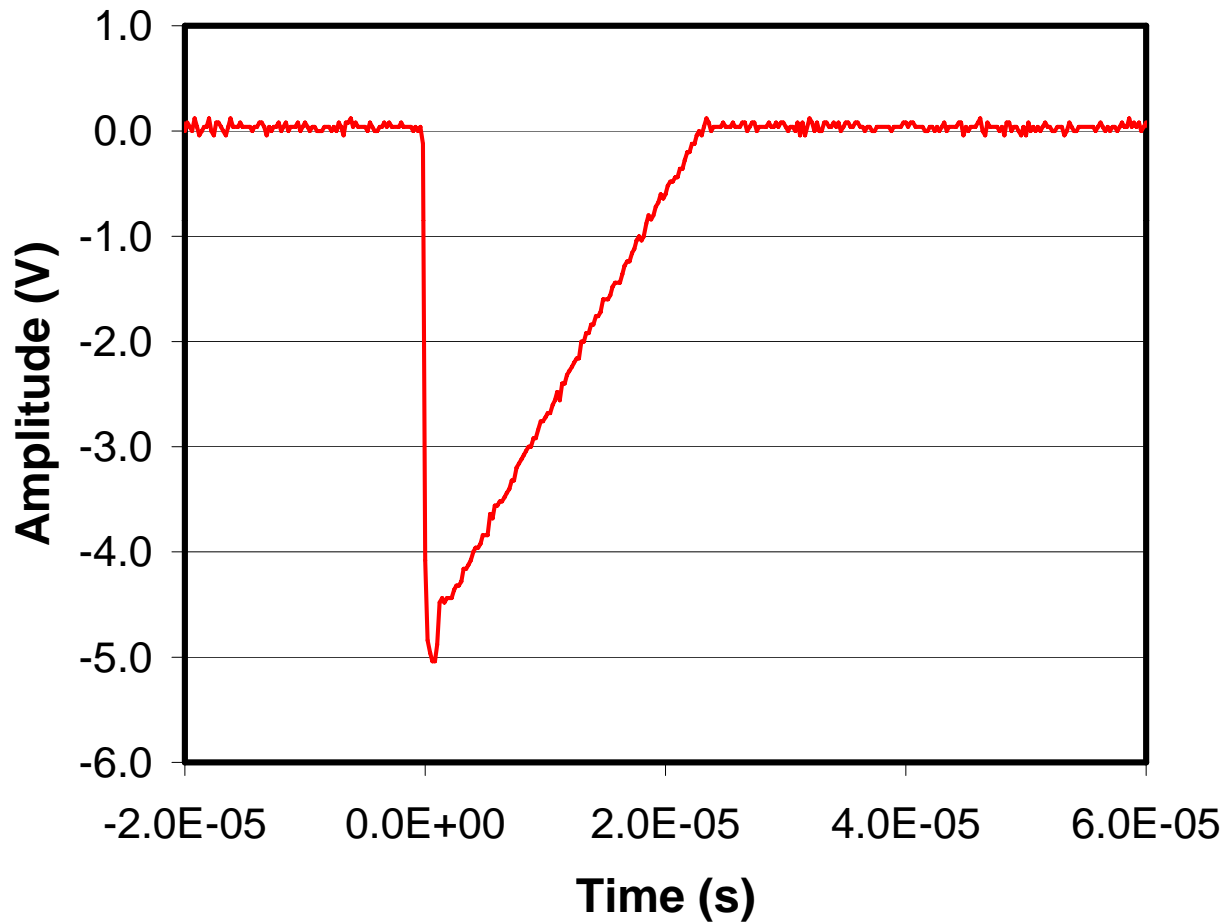

— 0 krad



Presented by S. Buchner at SEE Symposium,
San Diego, CA April 2009.

LM124 – Q9 VF

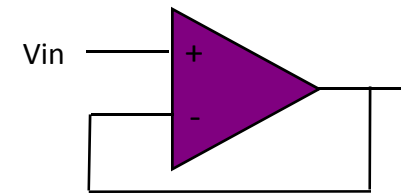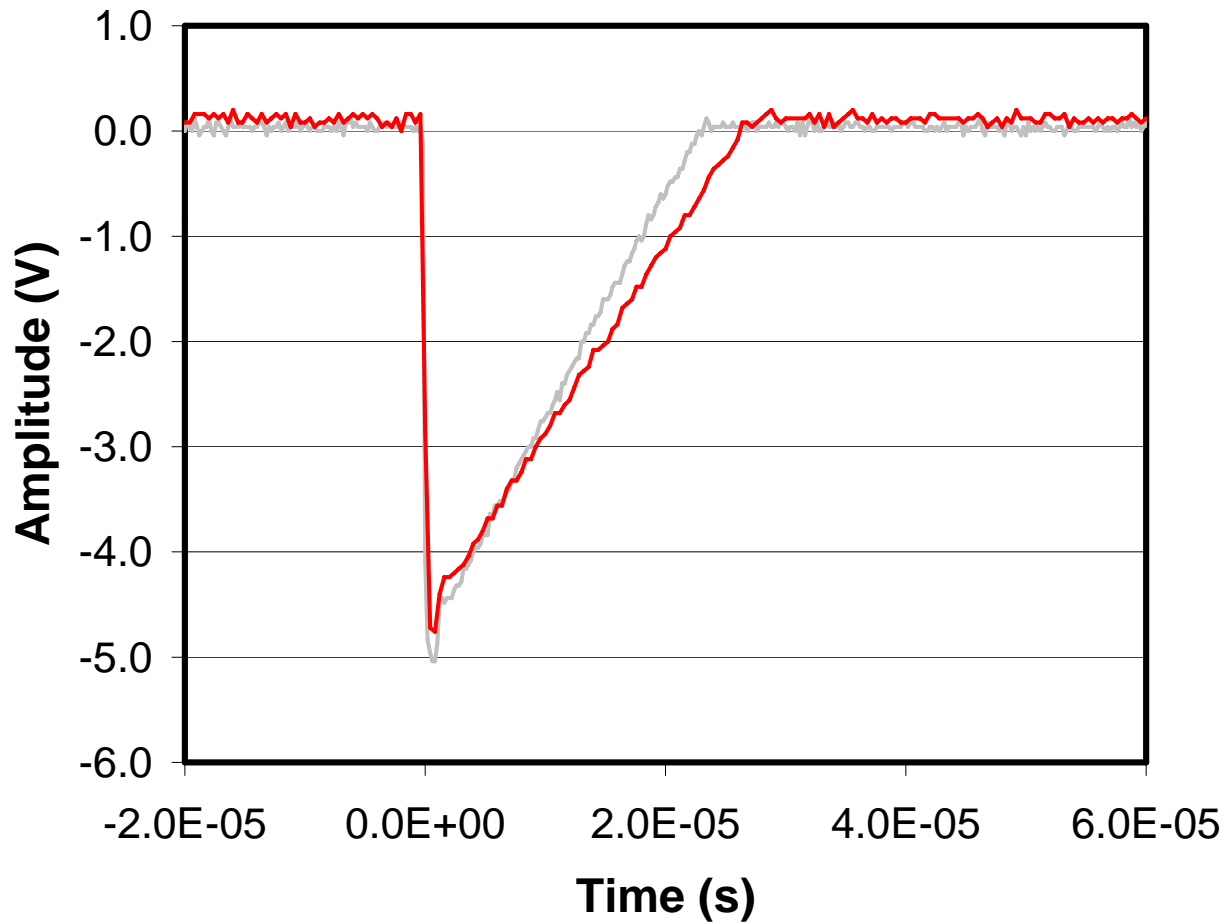

— 0 krad
— 5 krad



LM124 – Q9 VF

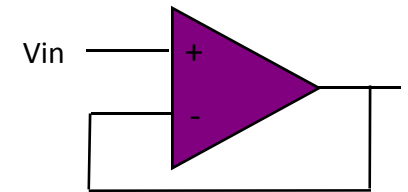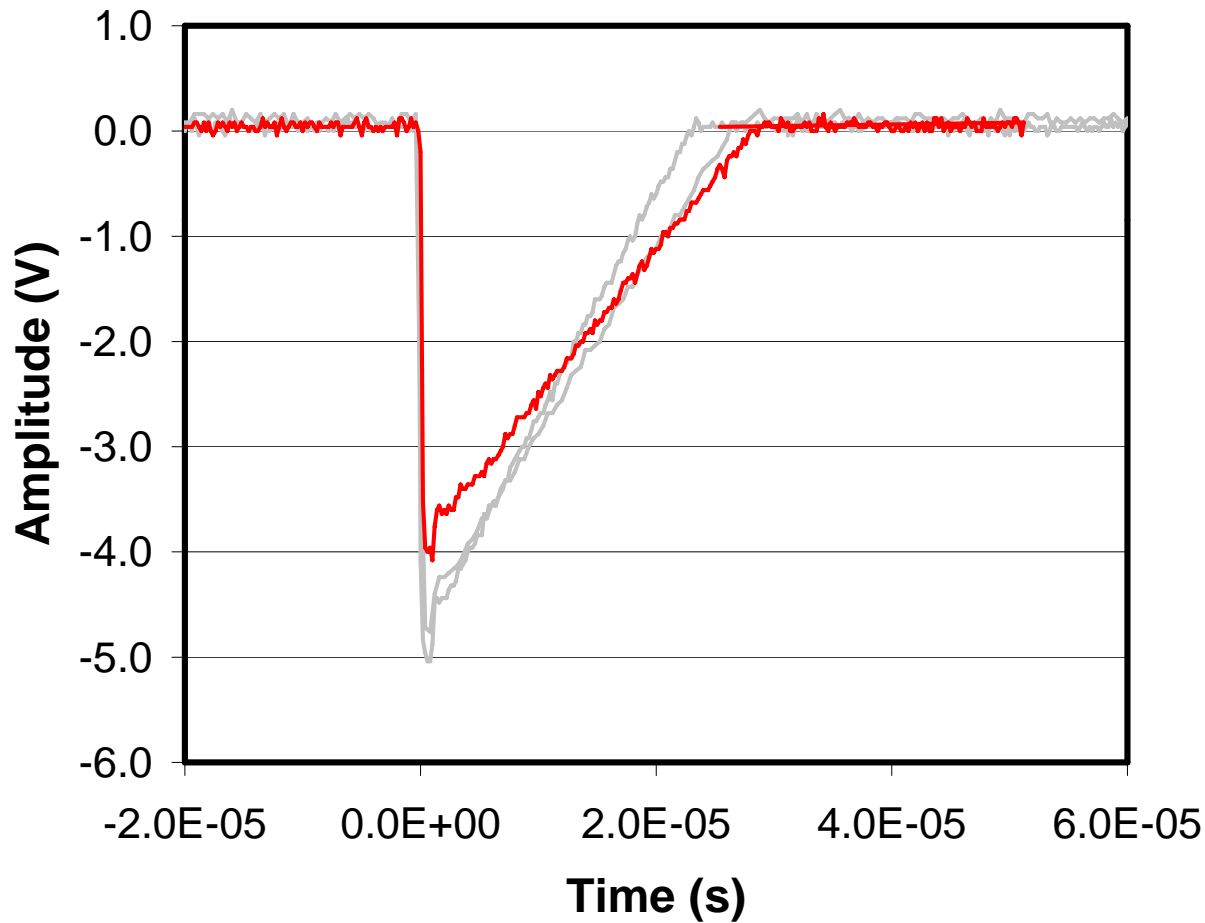

- 0 krad
- 5 krad
- 10 krad

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009



LM124 – Q9 VF

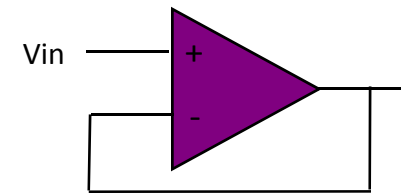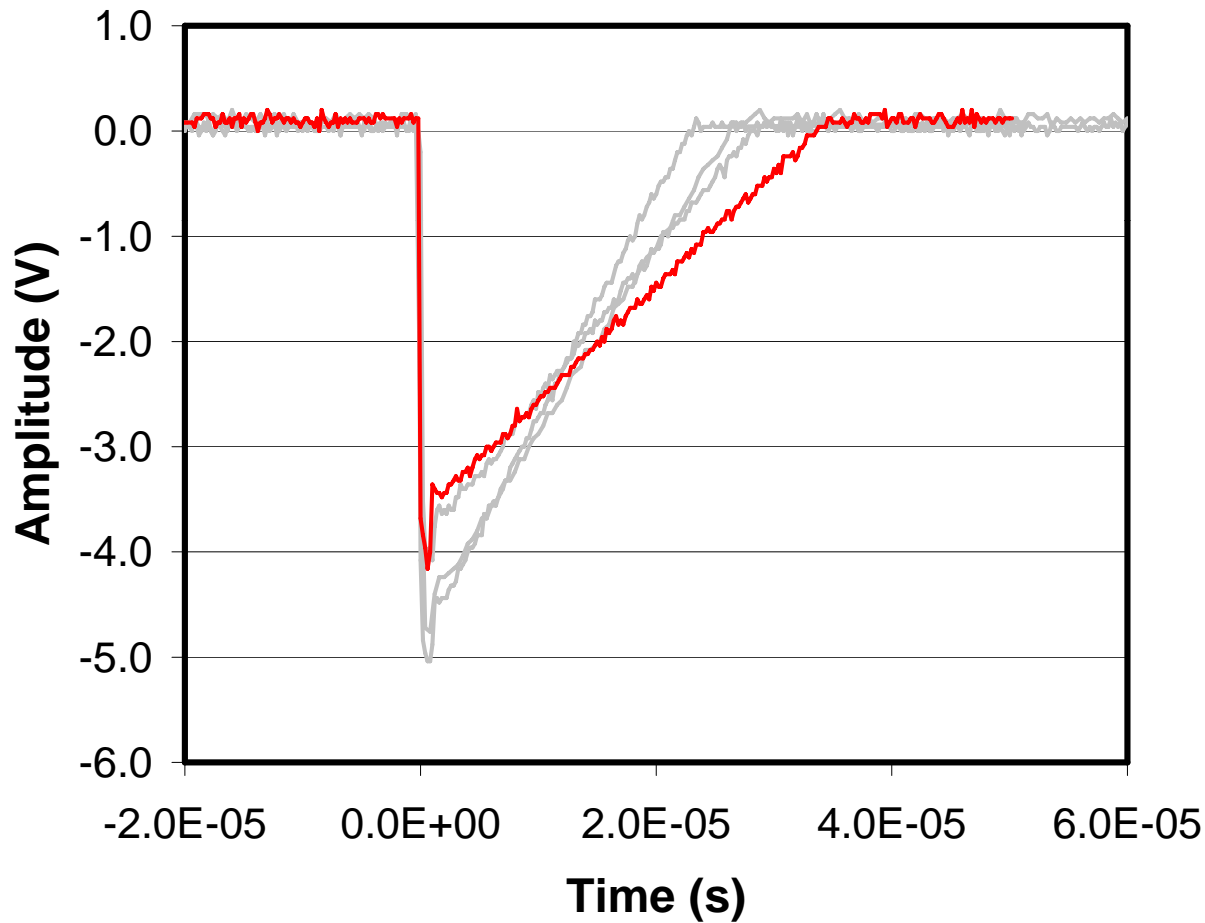

- 0 krad
- 5 krad
- 10 krad
- 18 krad

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009



LM124 – Q9 VF

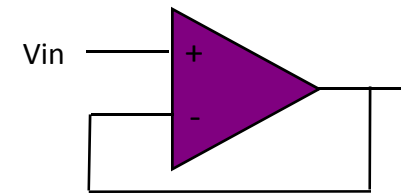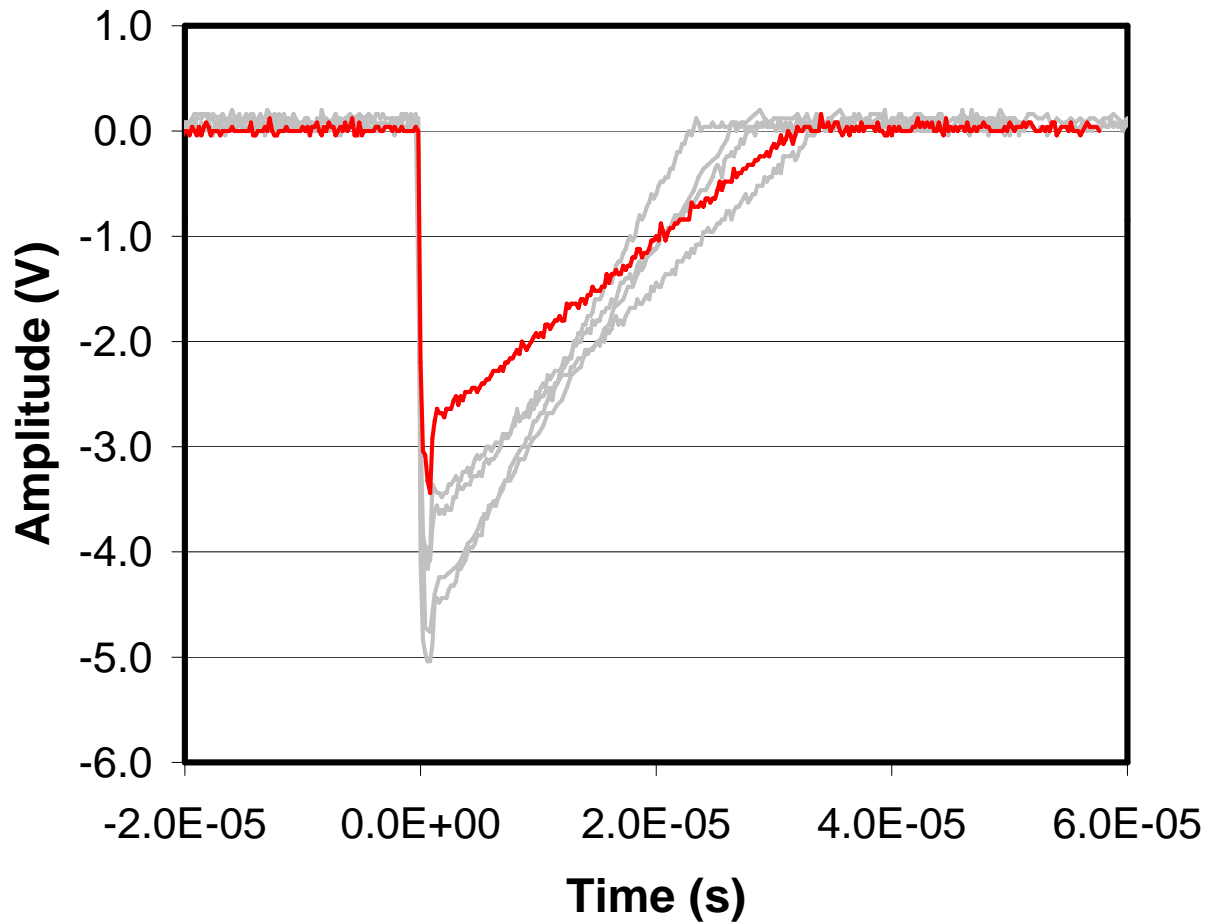

- 0 krad
- 5 krad
- 10 krad
- 18 krad
- 28 krad

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009



LM124 – Q9 VF

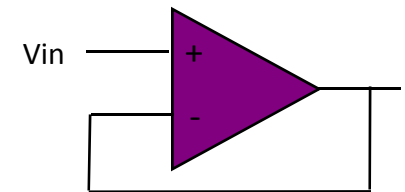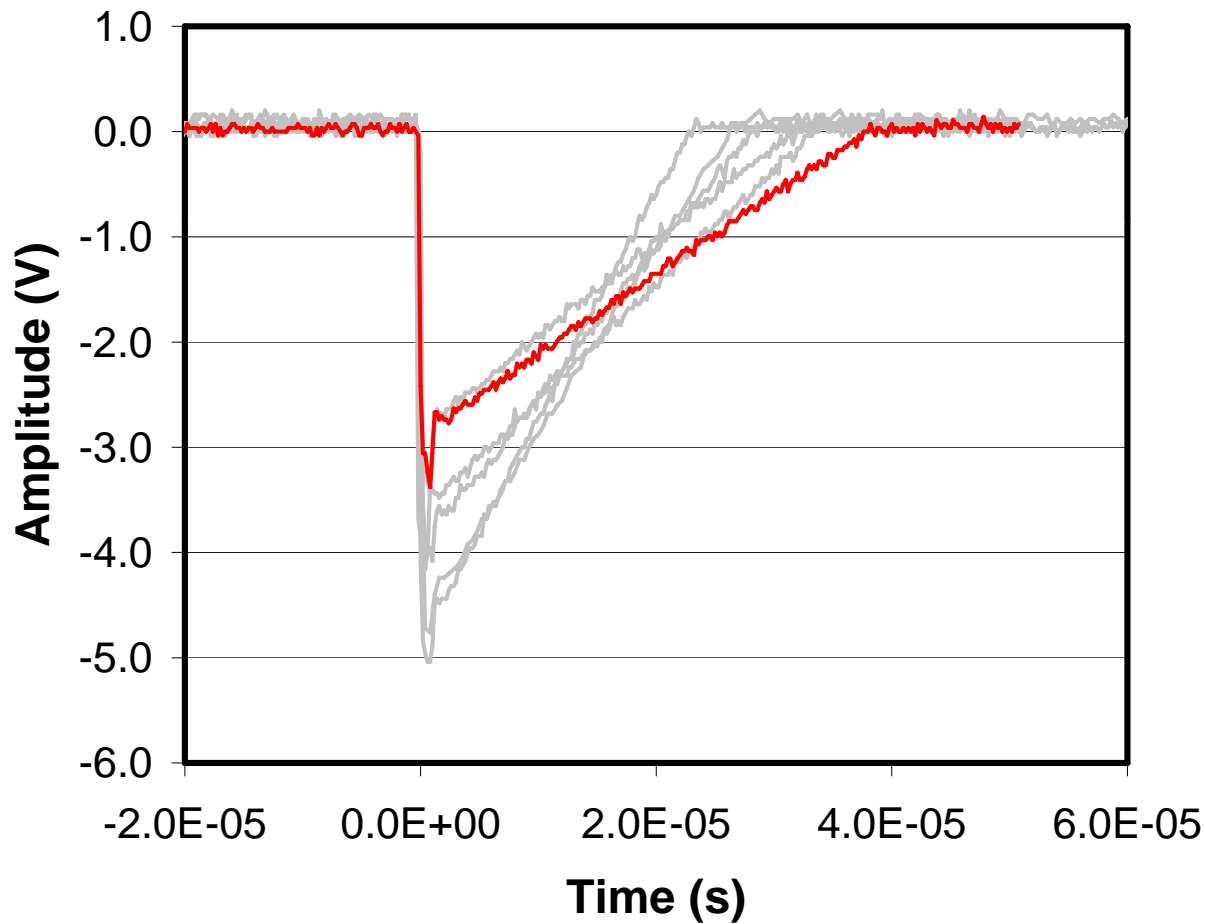

- 0 krad
- 5 krad
- 10 krad
- 18 krad
- 28 krad
- 35 krad

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009


LM124 – Q9 VF

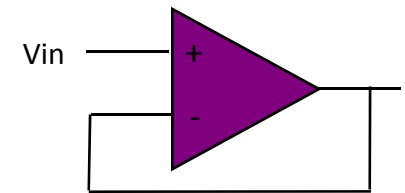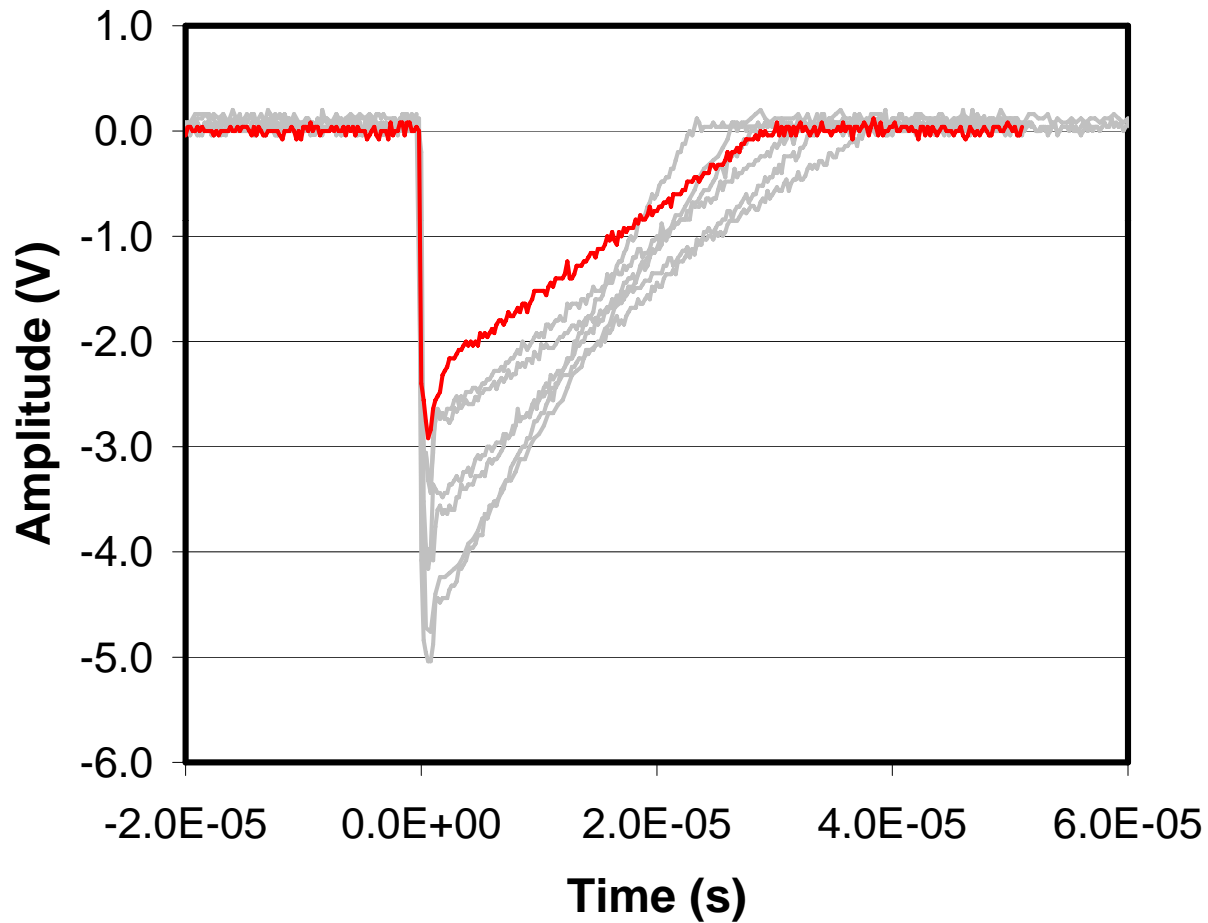

- 0 krad
- 5 krad
- 10 krad
- 18 krad
- 28 krad
- 35 krad
- 50 krad


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – Slew Rate

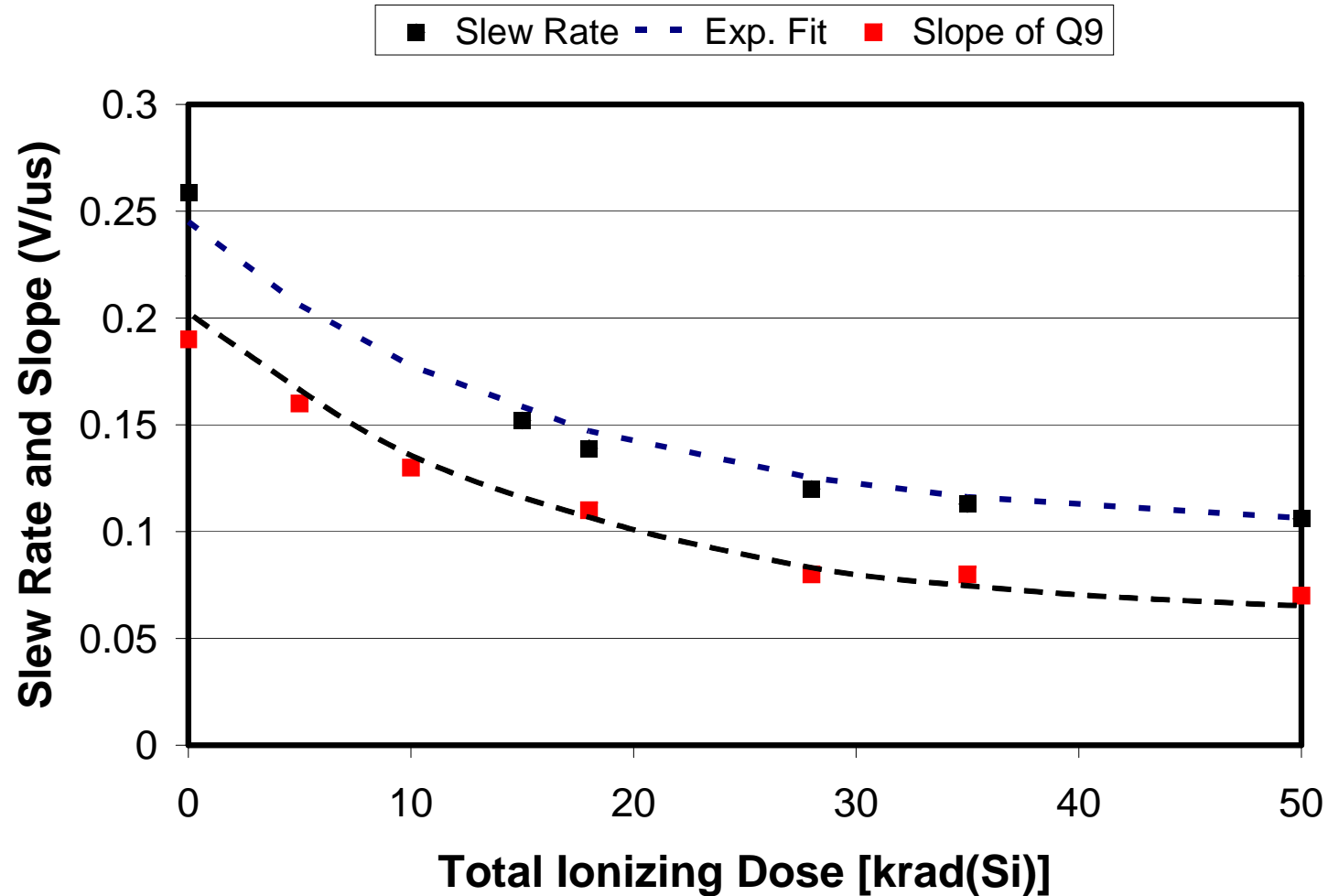


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

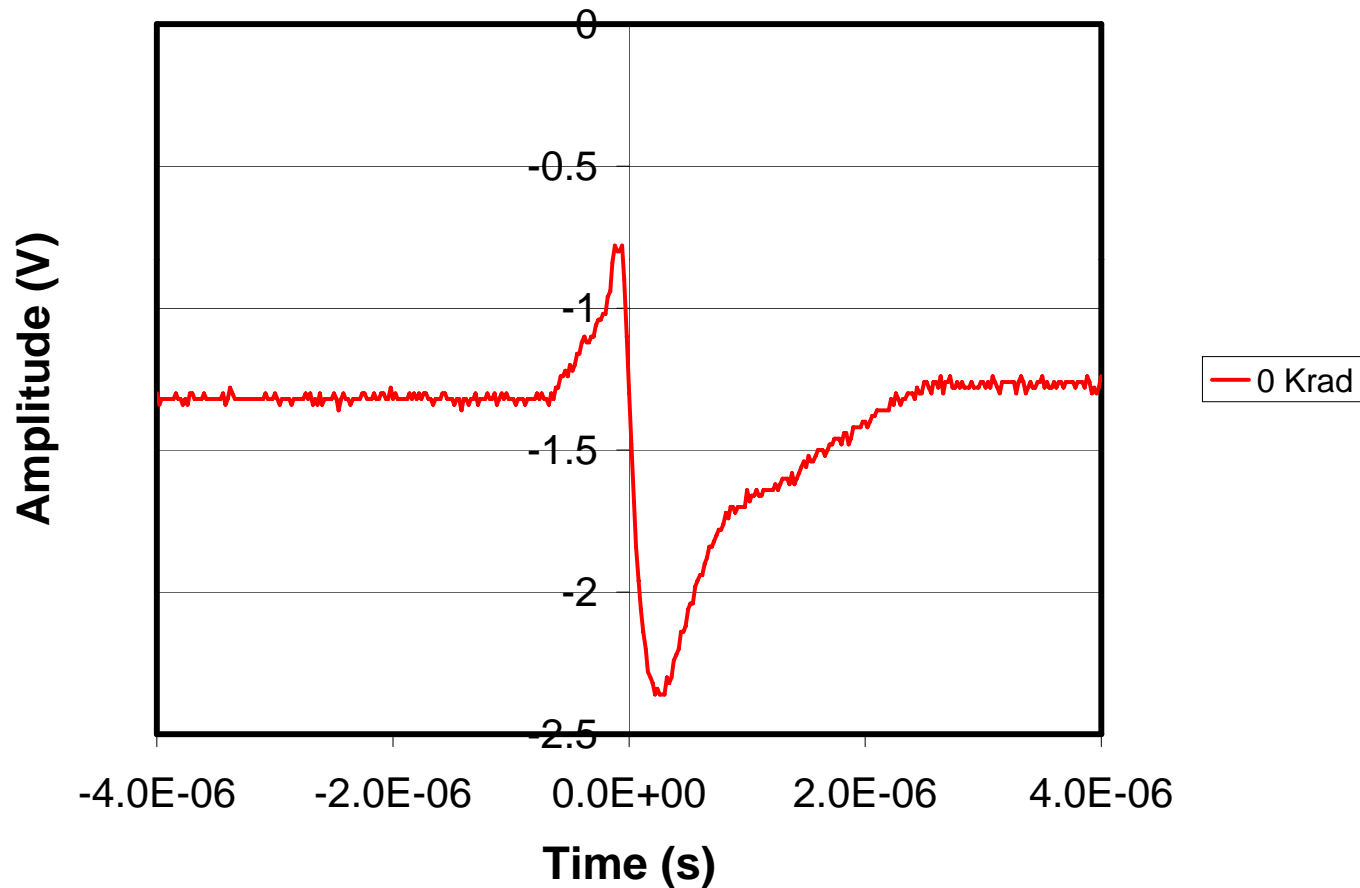


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

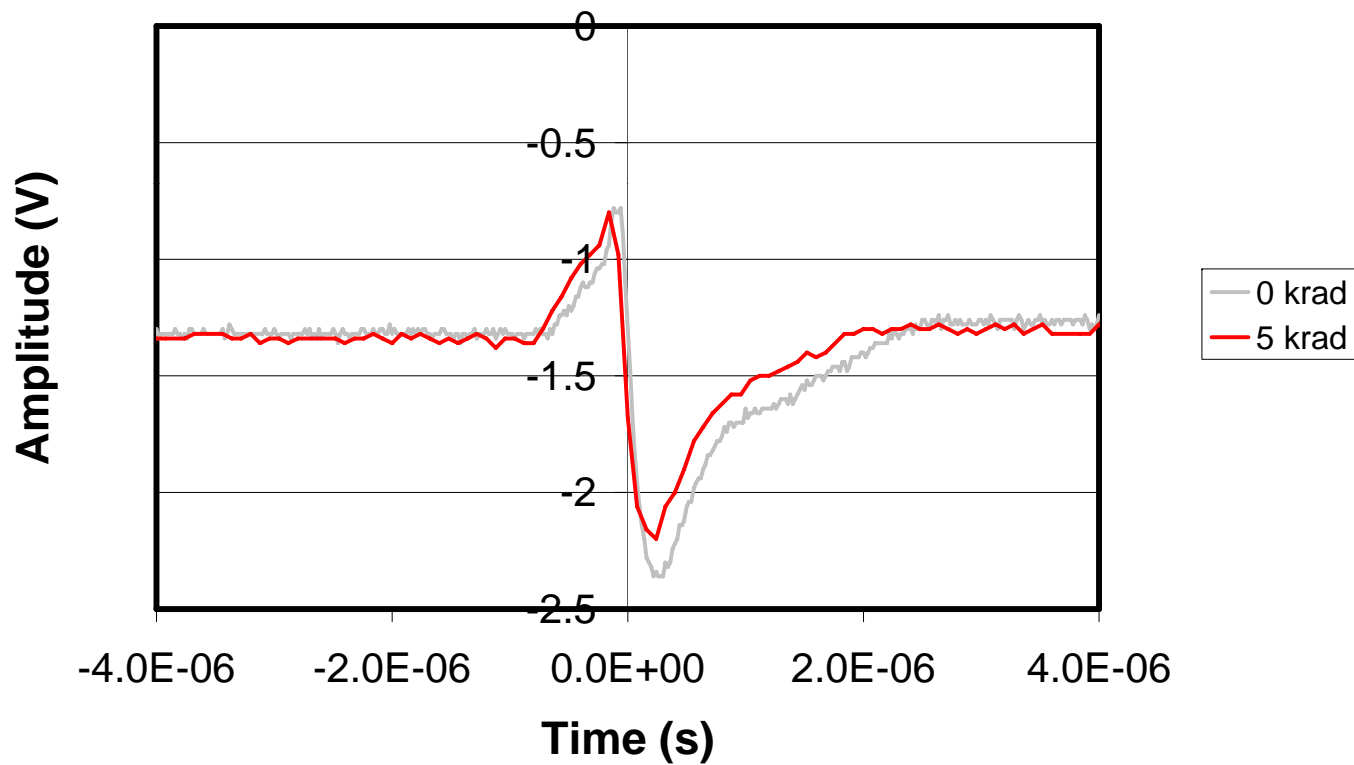


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

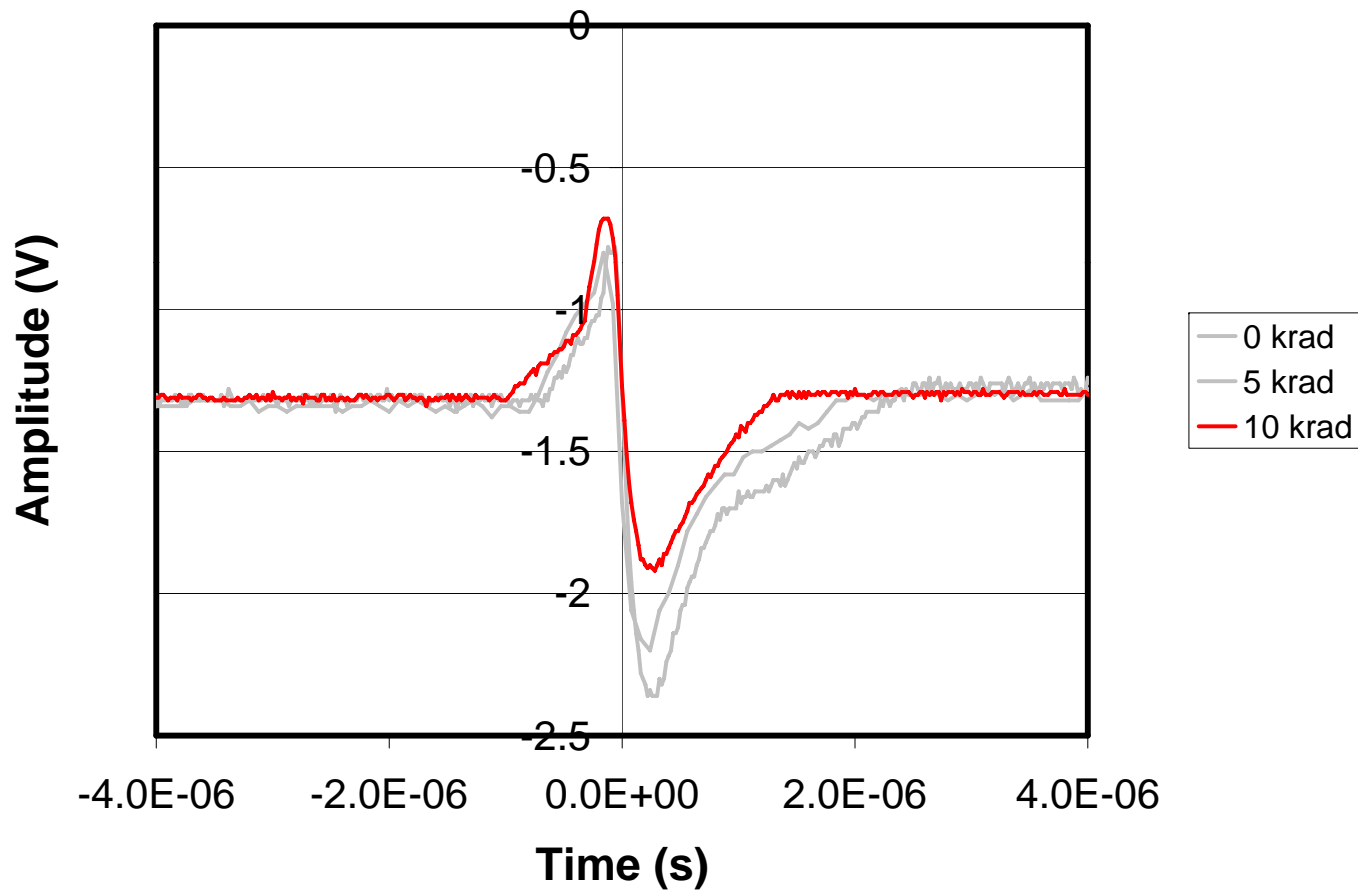


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

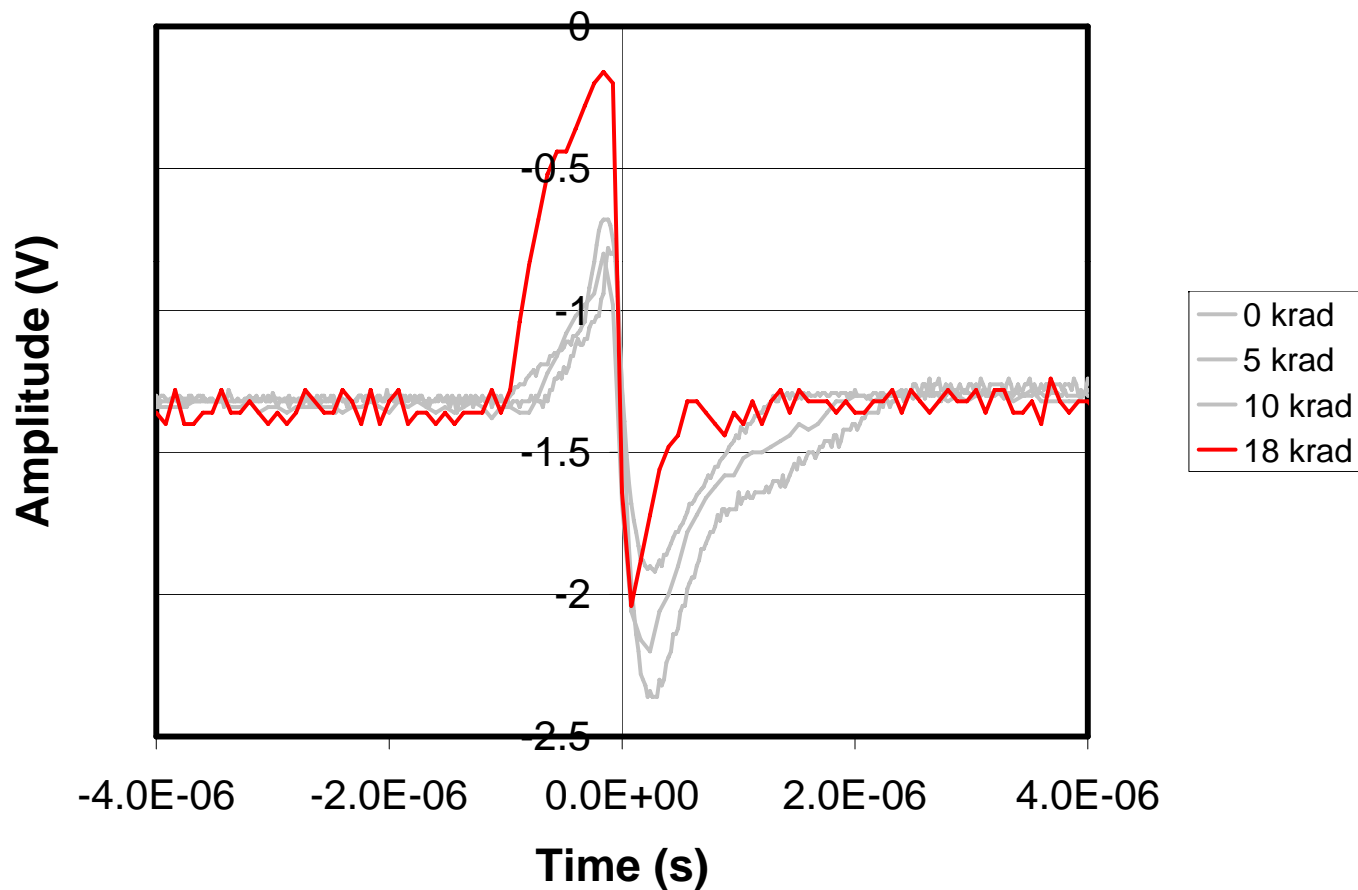


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

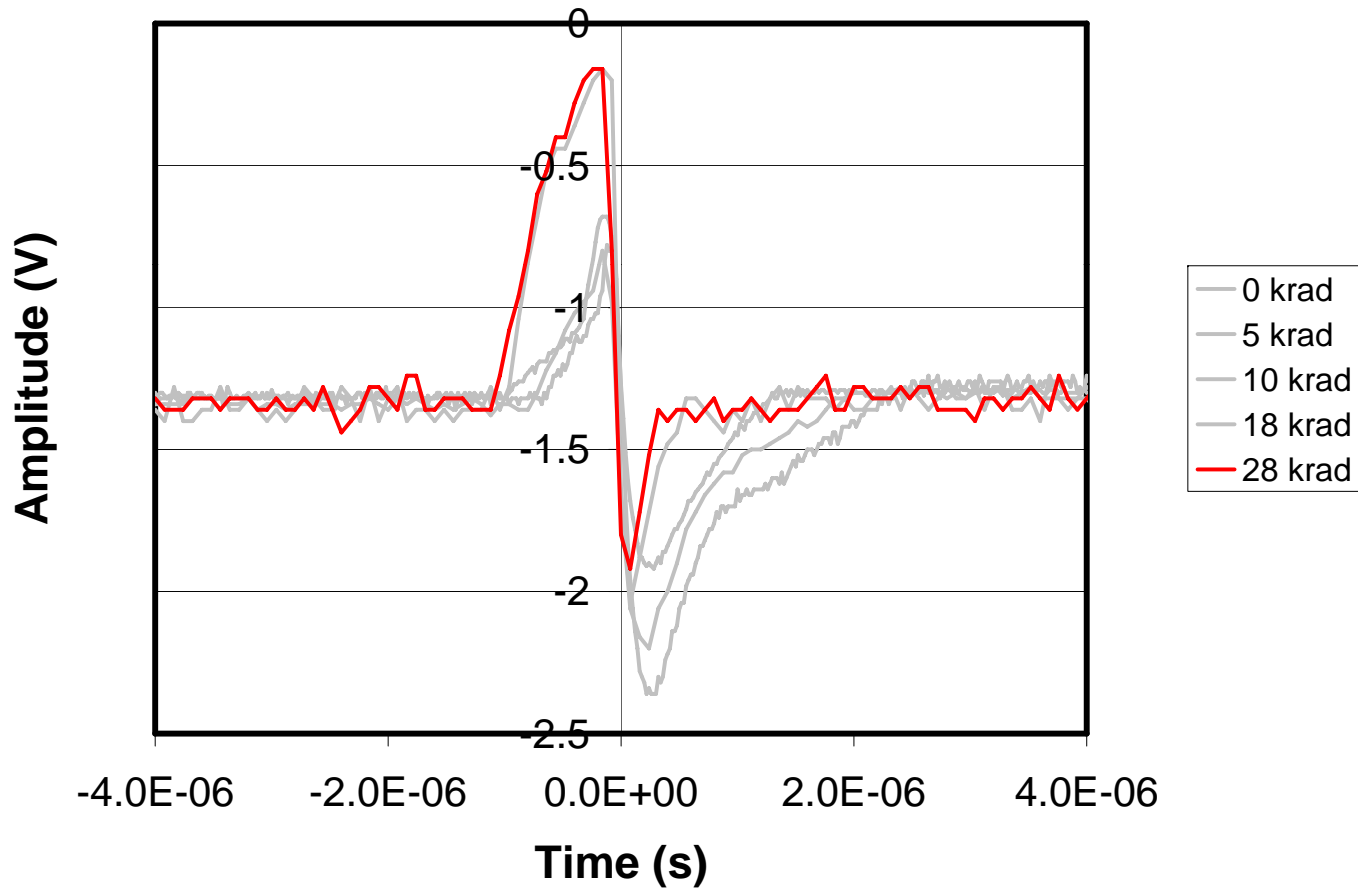


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

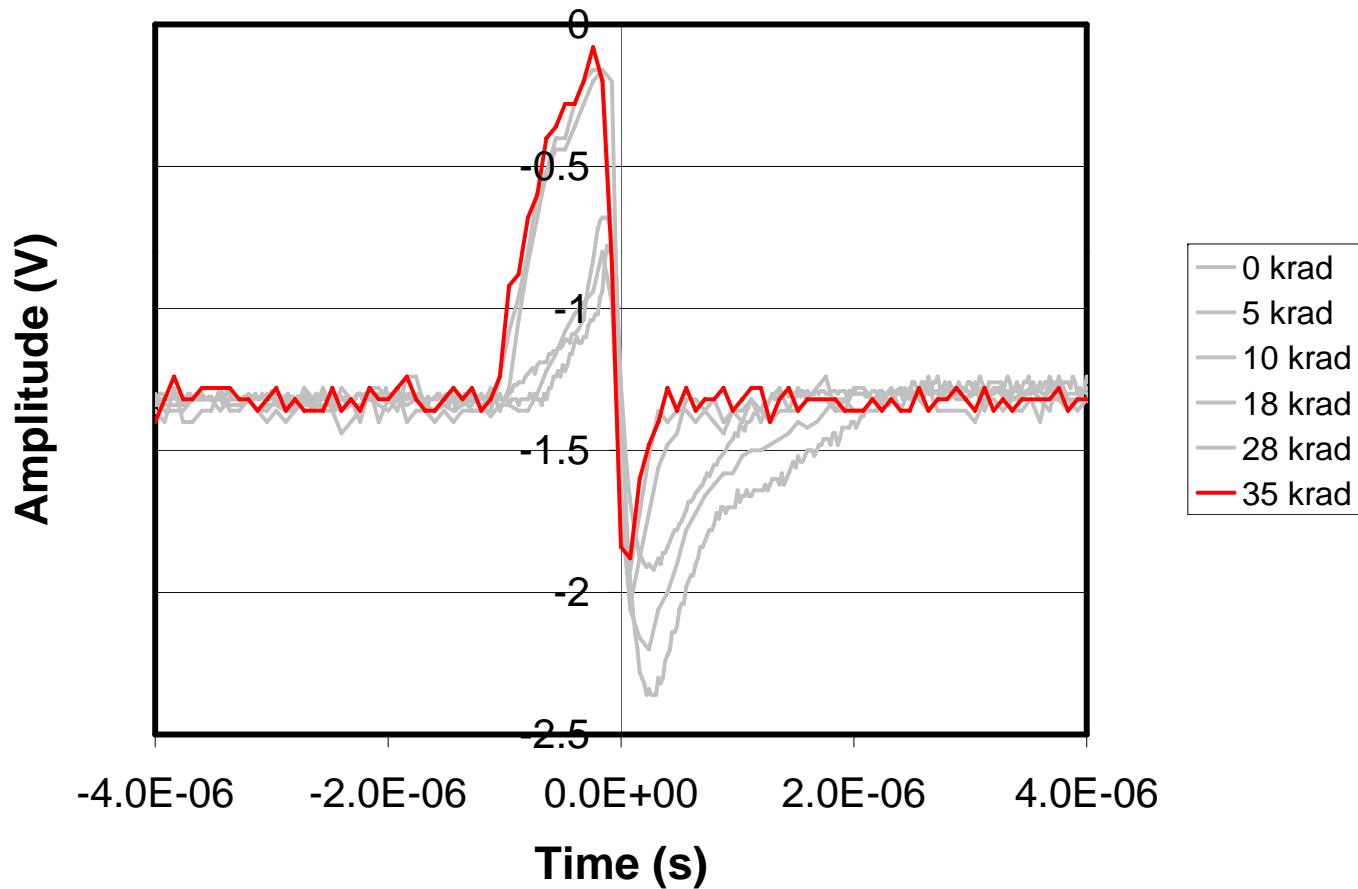

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

LM124 – R1 (Inverter Mode)

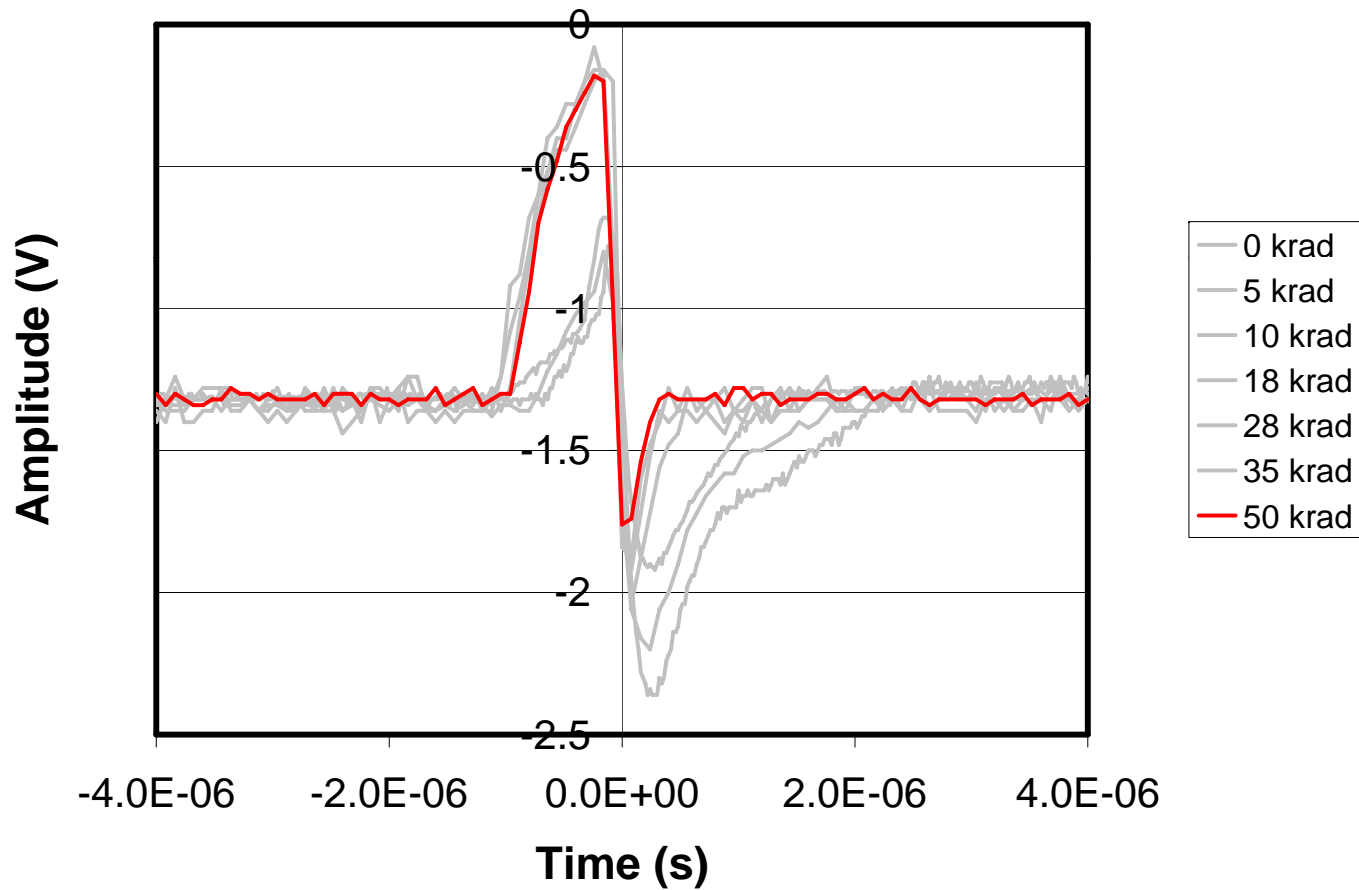

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009



DIGITAL CMOS CIRCUIT

Test Circuit from Micro-RDC

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Digital Test Circuit

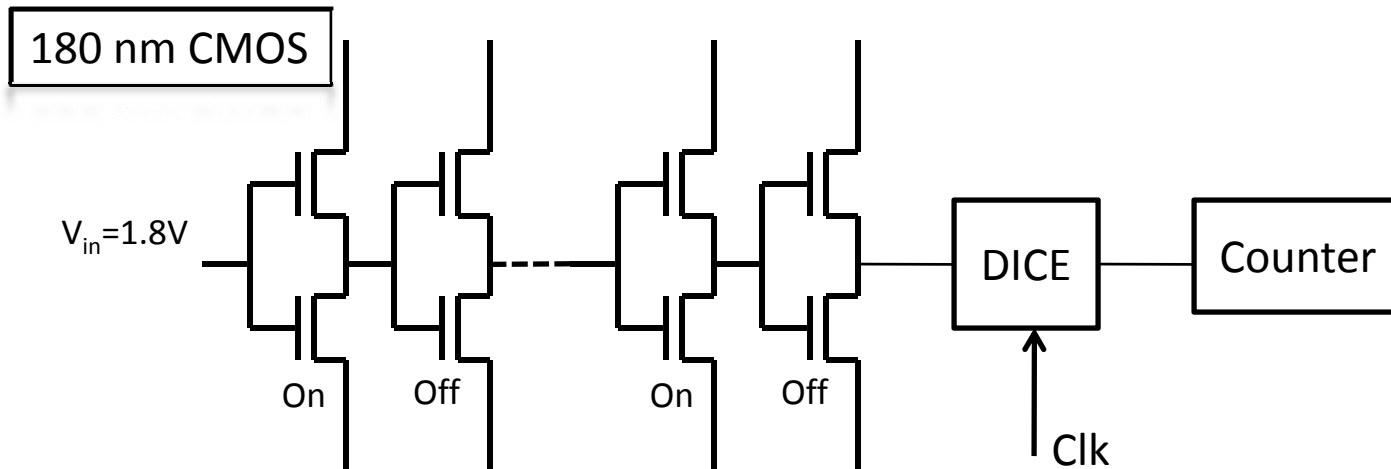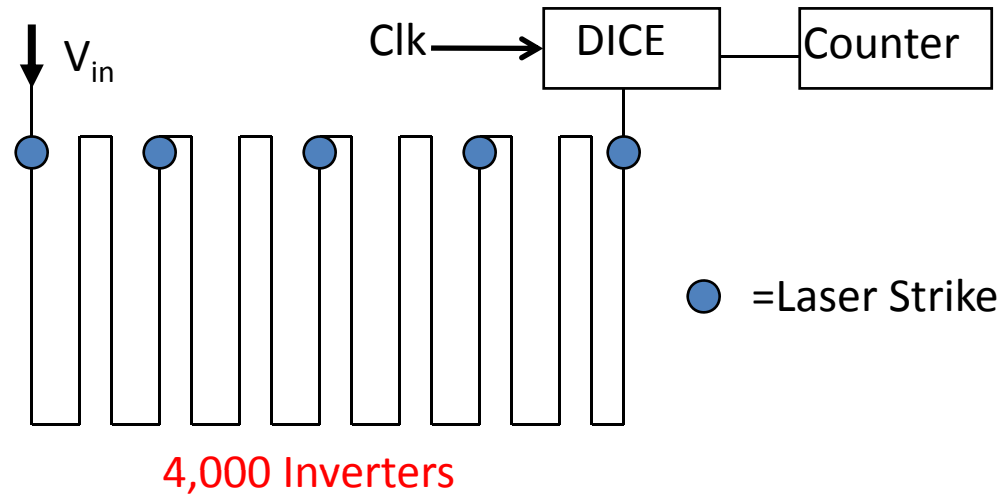- Use pulsed laser to measure transient width




Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Digital Test Circuit


$$R = (\tau_{pw} - T_{s-h}) \cdot f_{clk} \cdot f_{laser}$$
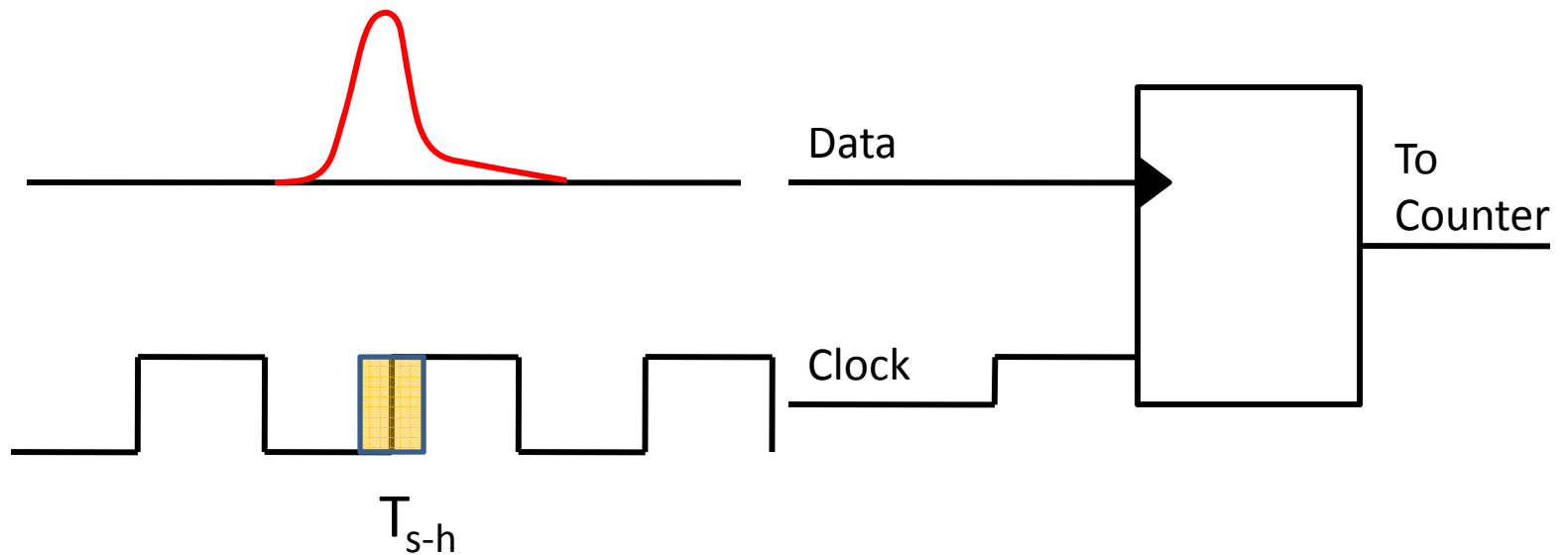
$$\text{Pulse-width} = \tau_{pw} = T_{s-h} + \frac{R}{f_{clk} \cdot f_{laser}}$$




Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Test Results

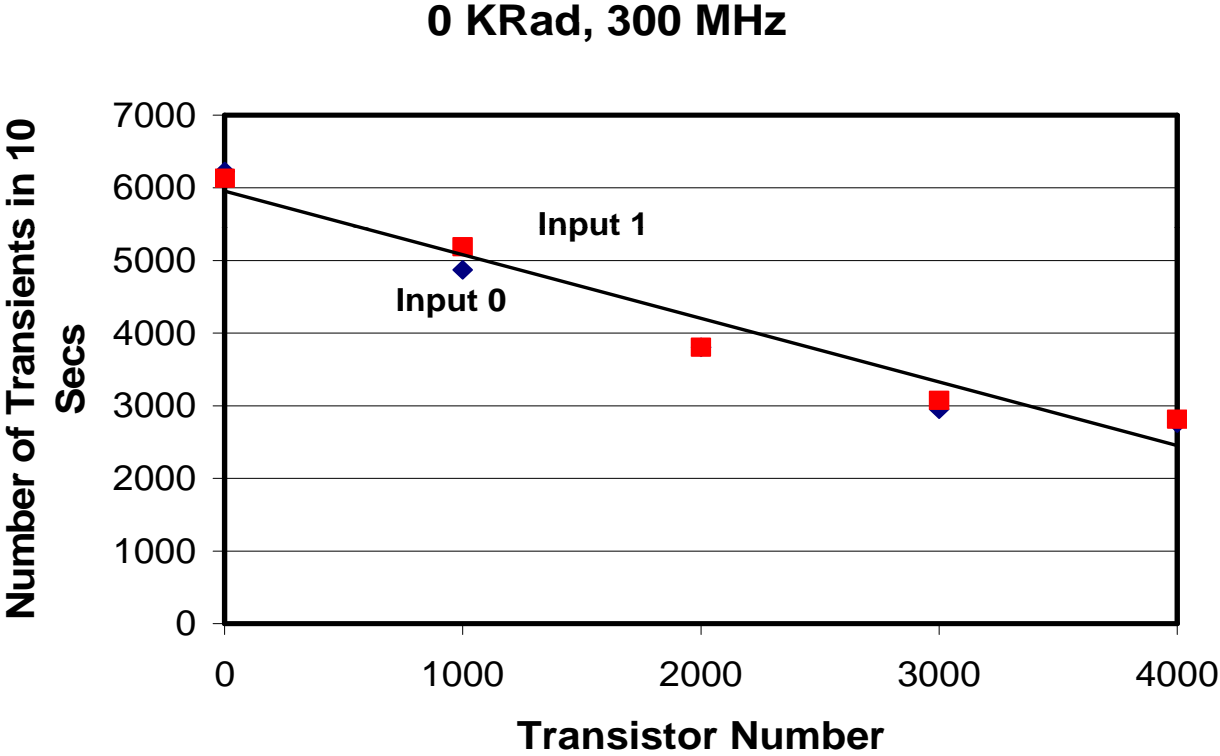


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Test Results

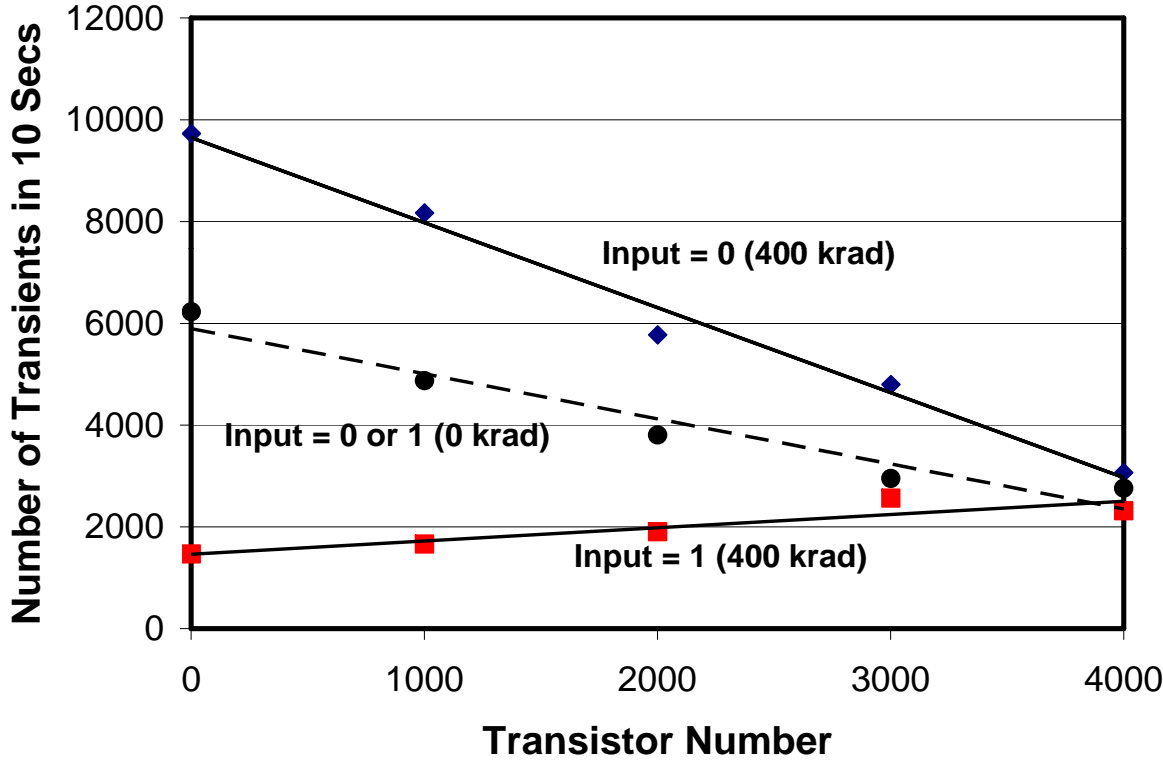


Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Explanation

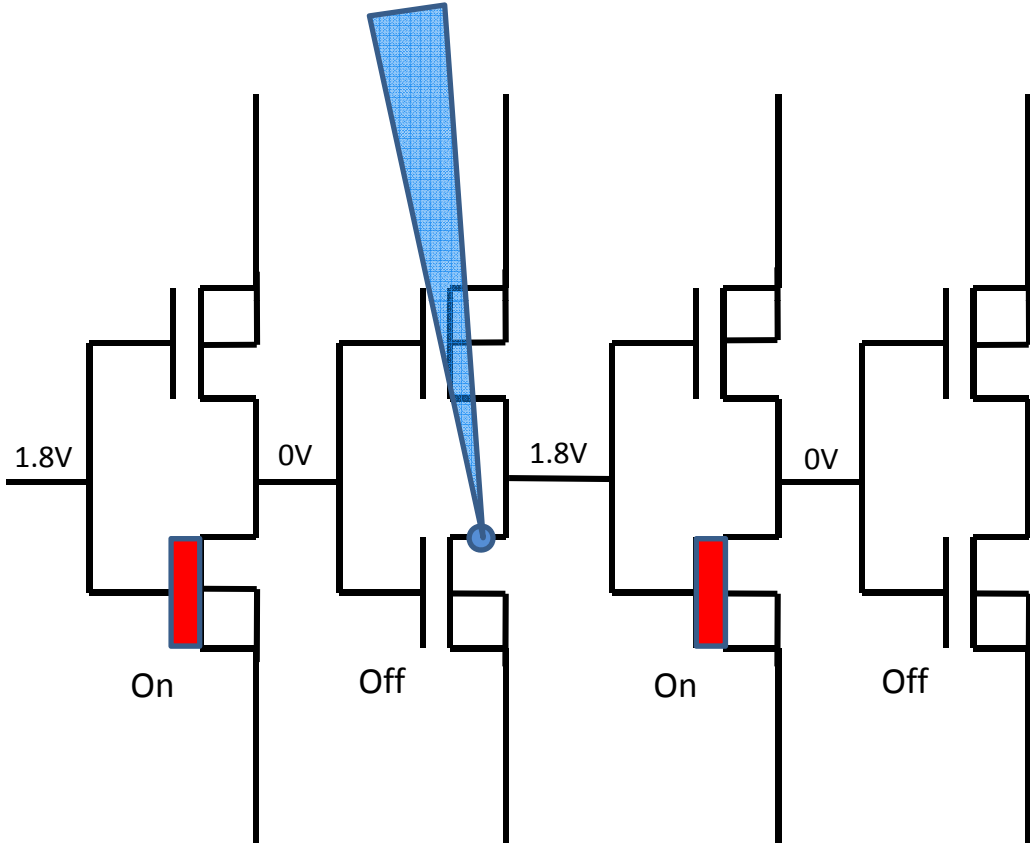

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Explanation

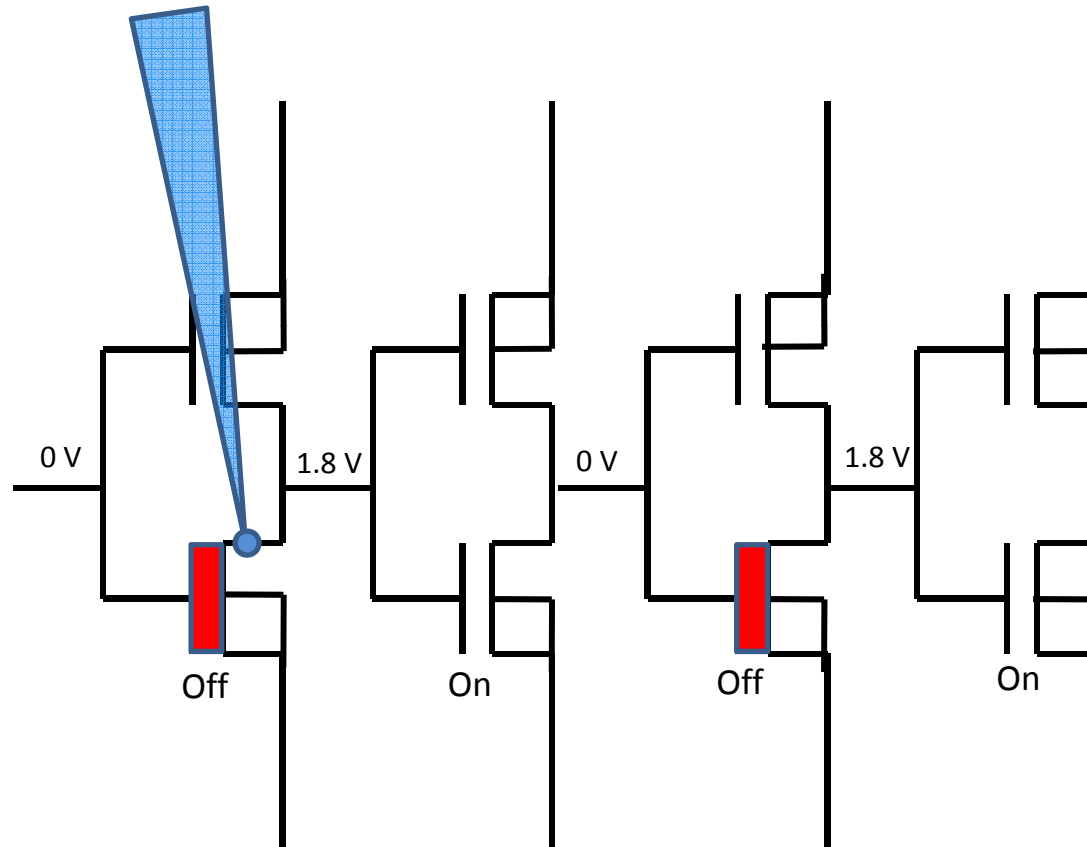

Presented by S. Buchner at SEE Symposium,
San Diego, CA, April 2009

Summary

- Exposure of ICs to ionizing radiation alters their electrical parameters and therefore their SET shapes and sensitivities.
- The effect occurs in both CMOS and bipolar circuits.
- Depending on effect, rates may increase or decrease.
- Effect of TID on SET rates should be considered if SETs cannot be tolerated.
- This work is being extended to other ICs such as a phase locked loop and memories.